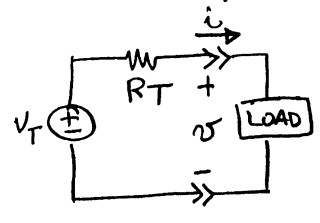




Application to non-linear loads

Thevenin




$$i = \frac{V_T - v}{R_T}$$

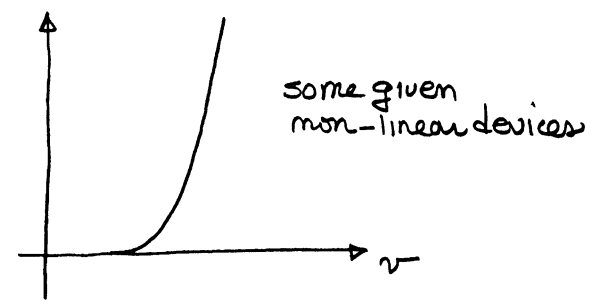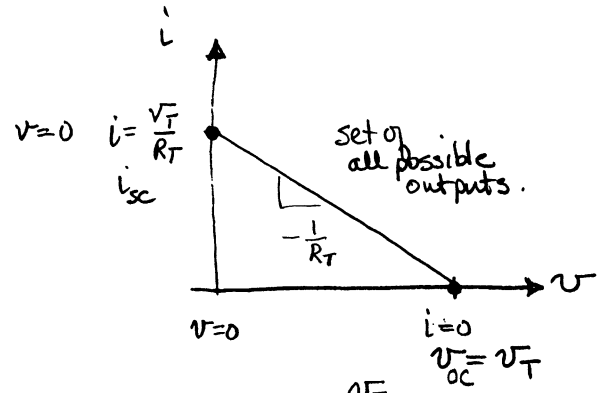
$$i = -\frac{1}{R_T} v + \frac{V_T}{R_T}$$



$$i = -\frac{1}{R_T} v + \frac{V_T}{R_T}$$

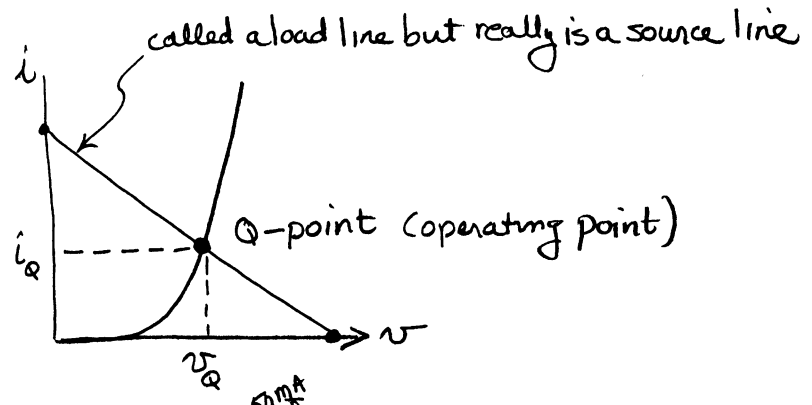

Example 3-18

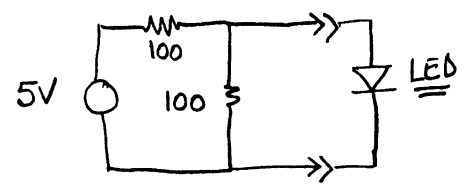


$$V_T = V_{oc} = \frac{100}{100+100} \cdot 5 = 2.5V$$

$$R_T = 100 \parallel 100 = 50$$

$$i_N = i_{sc} = \frac{V_T}{R_T} = \frac{2.5}{50}$$


$$= 50 \text{ mA}$$

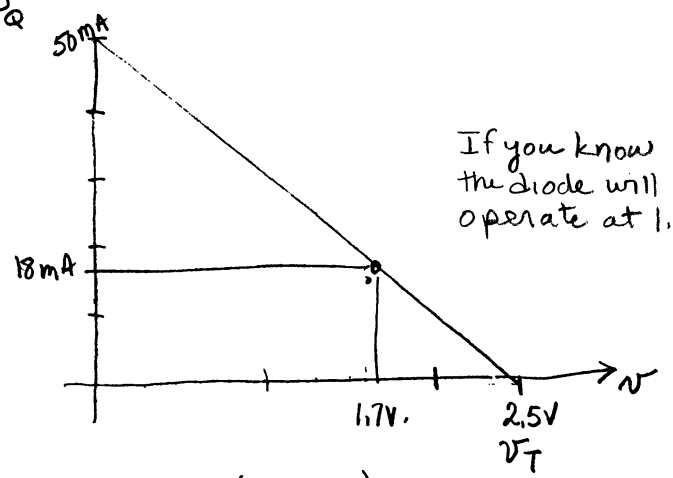

If you know the diode will operate at 1.7 volts.

$$P_D = v_i = (1.7)(.018) = 30.6 \text{ mW}$$


3.5 Maximum signal transfer

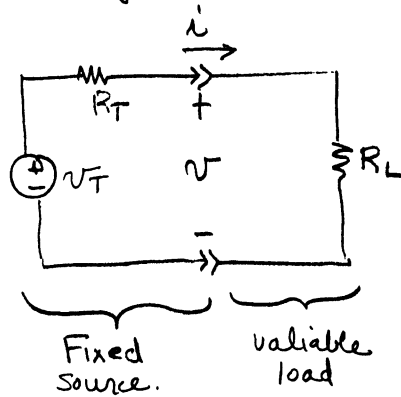

max output voltage when $R_L = \infty$

max output current when $R_L = 0$

Where is maximum power?

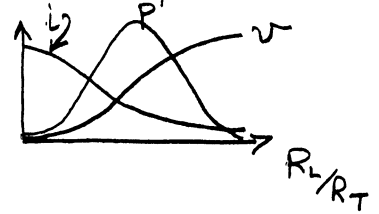

Consider the power being delivered to the load.

At the interface

$$v = \frac{R_L}{R_L + R_T} V_T$$

$$i = \frac{V_T}{R_L + R_T}$$

$$P = vi = \frac{R_L V_T}{R_L + R_T} \cdot \frac{V_T}{R_L + R_T} = \frac{R_L V_T^2}{(R_L + R_T)^2}$$

When do we get maximum power to the load, i.e., the value of R_L

$$\frac{\partial P}{\partial R_L} = \frac{V_T^2}{(R_L + R_T)^2} + \frac{R_L V_T^2 (-2)}{(R_L + R_T)^3} = 0.$$



$$\frac{(R_L + R_T) - 2R_L}{(R_L + R_T)^3} V_T^2 = 0$$

$$R_L + R_T - 2R_L = 0$$

$$R_T - R_L = 0$$

Example 3-19

given measurements find max output.

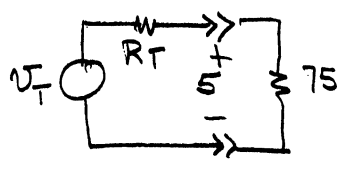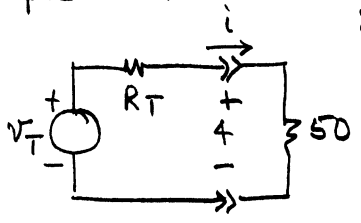

$$4 = \frac{50}{50 + R_T} v_T$$

$$5 = \frac{75}{75 + R_T} v_T$$

$$\frac{200 + 4R_T}{50} = v_T$$

$$v_T = \frac{375 + 5R_T}{75}$$

$$\frac{200 + 4R_T}{50} = \frac{375 + 5R_T}{75}$$

$$(200)(75) + (75)(4)R_T = (375)(50) + (50)(5R_T)$$

$$(75)(4)R_T - (50)(5)R_T = (375)(50) - (200)(75)$$

$$300R_T - 250R_T = 18750 - 15000$$

$$50R_T = 3750$$

$$R_T = 75\Omega$$

$$4 = \frac{50}{50 + 75} v_T$$

$$\frac{(125)(4)}{50} = v_T = 10$$

max voltage out = $v_{oc} = 10$ volts

max current out = $i_{sc} = \frac{10V}{75\Omega} = 133mA$


max power out occurs at $R_L = 75\Omega$.

@ $R_L = 75\Omega$





$$V_{out} = \frac{75}{75 + 75} \cdot 10 = 5 \text{ volts.}$$

$$P_{out} = \frac{(V_{out})^2}{R_L} = \frac{(5)^2}{75} = \frac{25}{75} = 333mW.$$

3-6 Interface Circuit Design

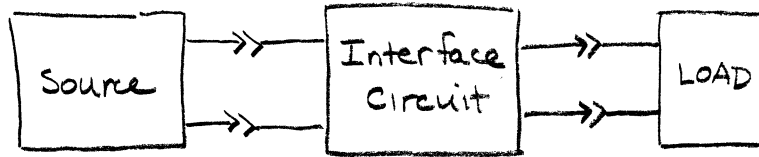


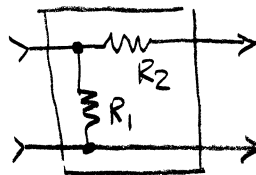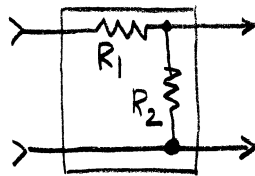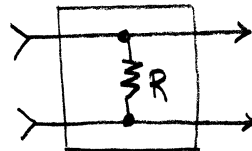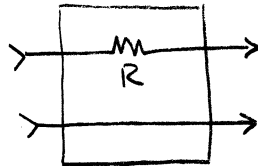At this point resistors are the only elements we can use to design interface circuits.







Examples of interface circuits. These are often called two-port circuits.

Design Example 3-23

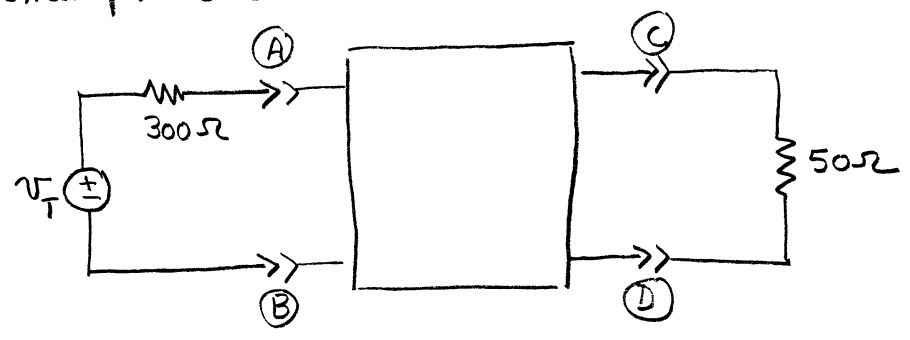


Design the two-port interface circuit so the load "sees" a Thevenin resistance of 50Ω between terminals C and D, while simultaneously the source "sees" a load resistance of 300Ω between A and B

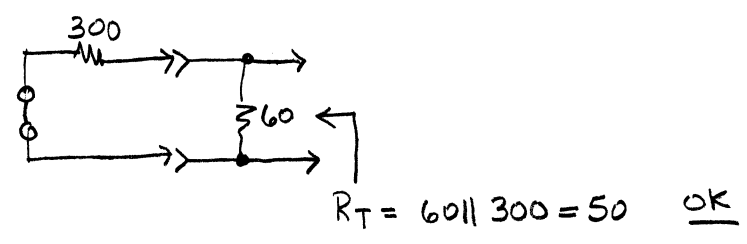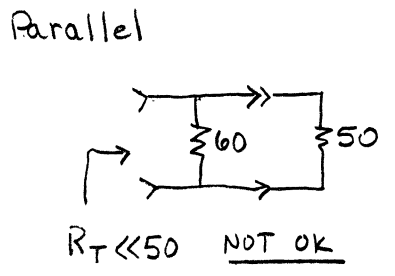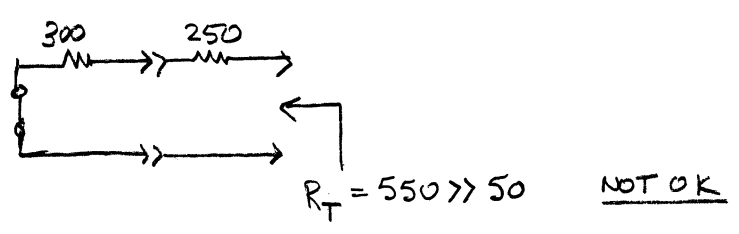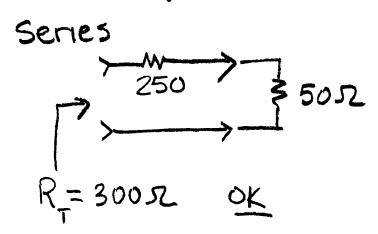
Design We can try different interface circuits



Try two resistor circuits

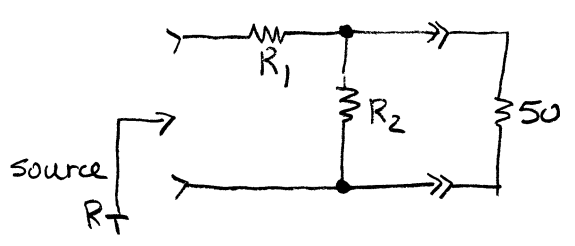

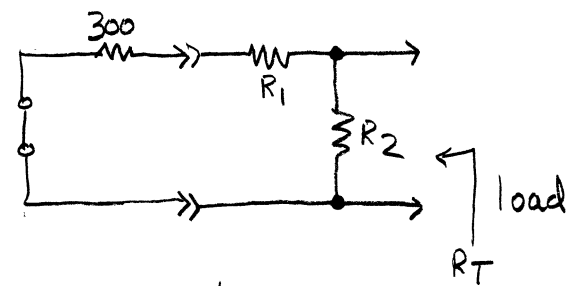Want source to see larger resistance than 50 so this requires a series R.



Want load to see a R_T smaller than source so there has to be a parallel resistance.

Design $R_1 + \frac{50 R_2}{R_2 + 50} = 300$

$\frac{(R_1 + 300) R_2}{R_1 + 300 + R_2} = 50$

Non-linear equations with solutions $R_1 = 273.9$ and $R_2 = 54.8 \Omega$.