

Instrumentation Systems




can be filtering, linearization, etc.

converts analog to digital

need amplification to get signal up to useful level.

Possible amplifier solution

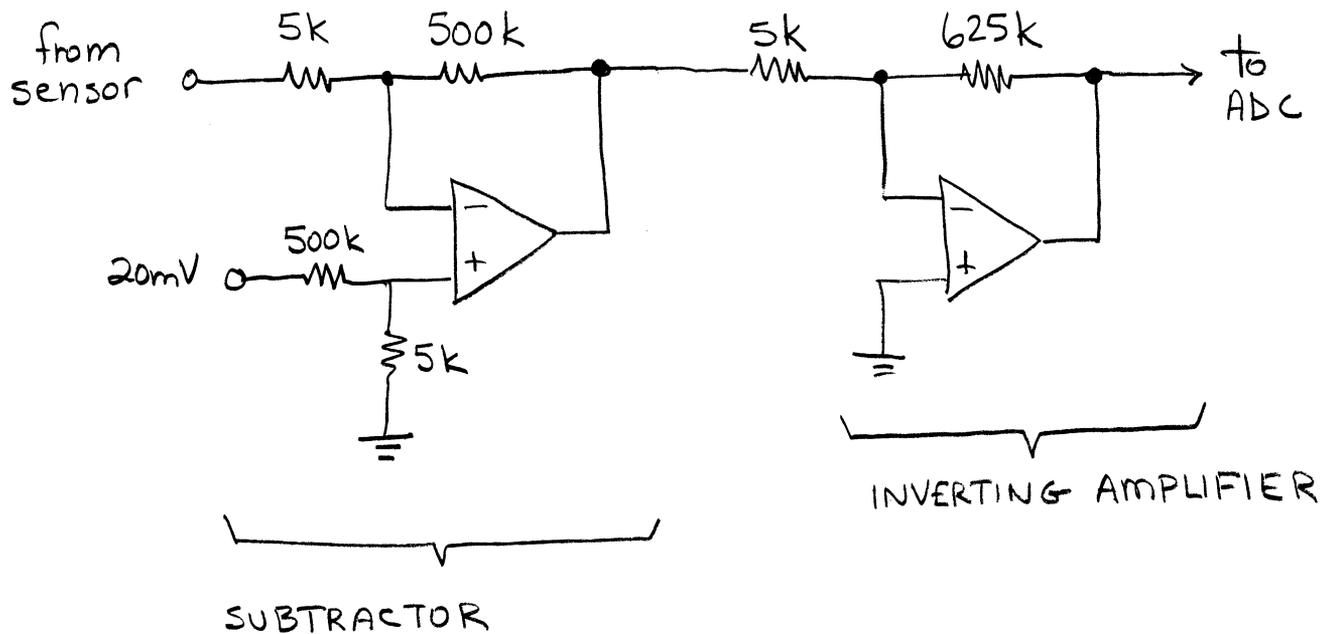


$$K_1 = -\frac{R_2}{R_1} = \frac{-500k}{5k} = -100$$

$$K_2 = \left(\frac{R_1 + R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) = \frac{(5k + 500k)}{5k} \left(\frac{5k}{5k + 500k}\right) = 1$$

Design Exercise 4-16

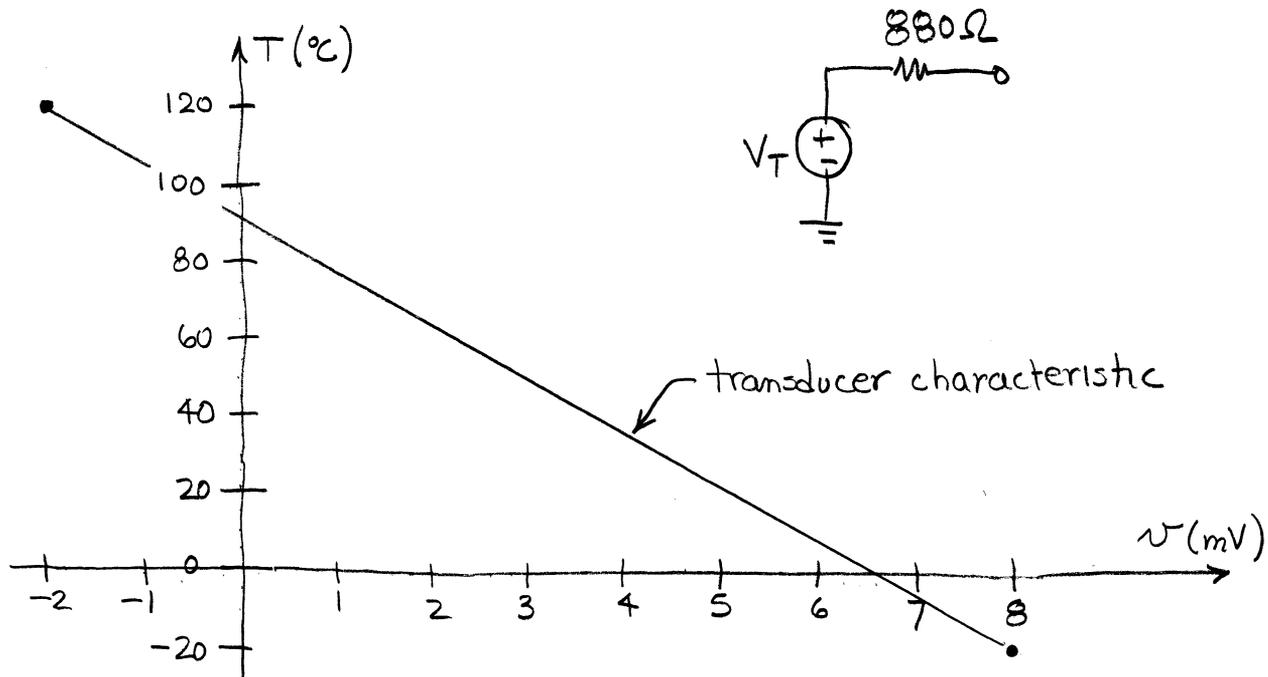
Design an OP AMP circuit to translate the temperature range -20°C to $+120^{\circ}\text{C}$ to a 0-1 volt signal using the following sensor characteristics. The transducer has a Thevenin resistance of 880Ω .



The required gain is

$$K = \frac{\text{output range}}{\text{input range}} = \frac{1 - 0}{8 - (-2) \times 10^{-3}} = 100$$

The ranges are

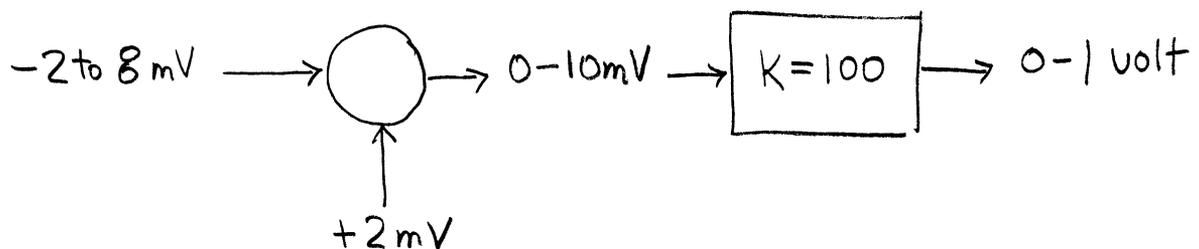


There are many ways to implement this

But we have a consideration other than gain

$$R_{\text{TRANSDUCER}} = 880\Omega$$

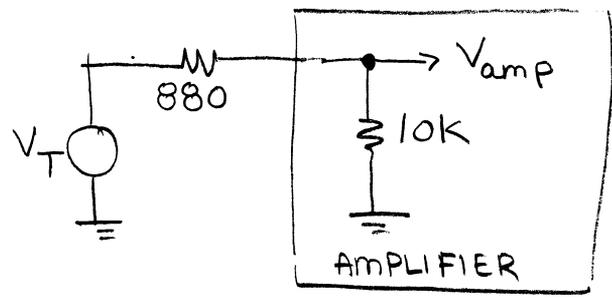We need R_{IN} for the amplifier to be at least 10x time to prevent loading - a voltage divider which would lead to only a fraction of the transducer signal being properly amplified,



Pick R_{IN} for amplifier to be 10k. Then


$$V_{\text{amp}} = \frac{10k}{880 + 10k} V_T \approx .92$$

We can use a subtractor circuit as shown below

-2mV to 8mV.

$$K_1 V_T = +200\text{mV to } -800\text{mV}$$

$$K_2(1.5) = -202\text{mV}$$

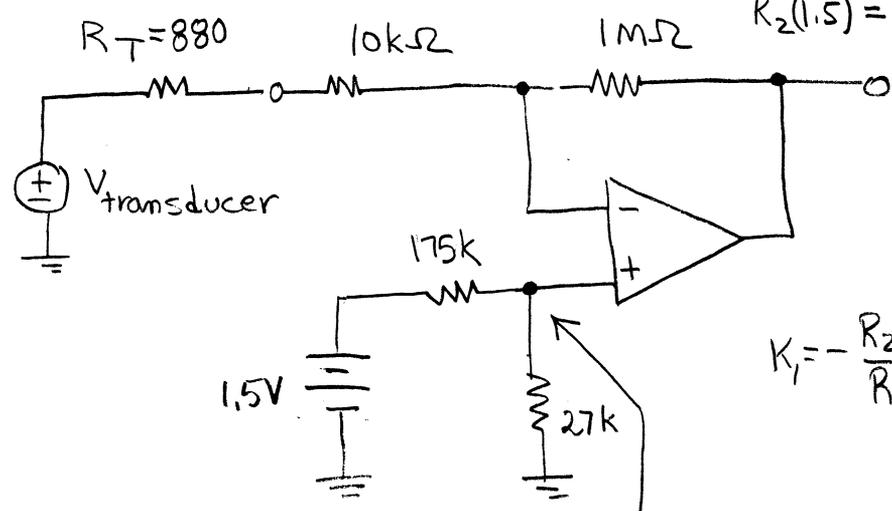

$$K_1 = -\frac{R_2}{R_1} = -\frac{1M\Omega}{10k\Omega} = -100$$

voltage divider

$$V_P = \frac{27k}{27k + 175k} (1.5) = 0.200 \text{ volts}$$

$$K_2 = \left(\frac{10^6 + 10^4}{10^6}\right) \left(\frac{27k}{175k + 27k}\right) = .135$$