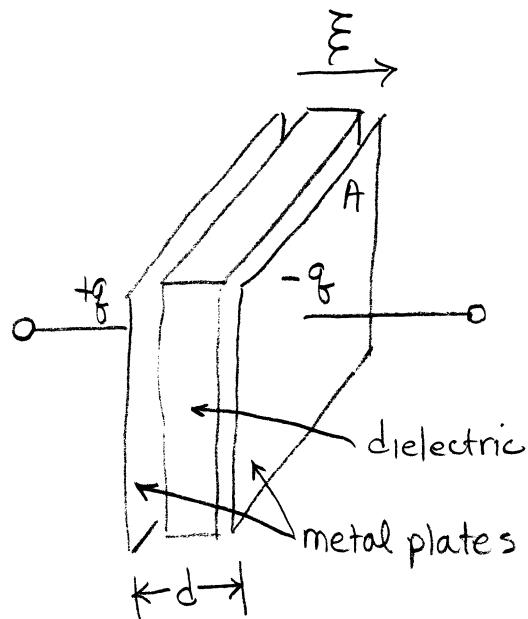


## Chapter 6 Capacitance and Inductance



For small  $d$  the electric field is given by

$$\mathbf{E}(t) = \frac{\mathbf{q}(t)}{\epsilon A}$$

$$\text{but } \mathbf{E}(t) = \frac{V_c(t)}{d}$$

Solving for  $q_f$


$$q_f(t) = \epsilon A \mathbf{E}(t) = \underbrace{\frac{\epsilon A}{d}}_{C} V_c(t)$$

This is a constant dependent upon the physical construction called the capacitance.  $C$

$$q_f(t) = C V_c(t)$$

Differentiating
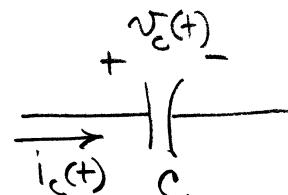
$$i_c(t) = \frac{dq_f(t)}{dt} = C \frac{dV_c}{dt}$$



This is the i-v characteristic of the capacitor.

Consider what this means

- ① When  $V_c = \text{constant (dc)}$  the current is zero
- ② discontinuous voltage like  $\delta(t)$  would require an infinite current. Because of this voltage across a capacitor must be continuous.

Integrate  $i_c(t) = C \frac{dV_c}{dt}$

$$\frac{1}{C} \int i_c(t) dt = dV_c$$


$$\frac{1}{C} \int_{t_0}^t i_c(x) dx = \int_{V_c(t_0)}^{V_c(t)} dV_c = V_c(t) - V_c(t_0)$$

$$\therefore V_c(t) = V_c(t_0) + \frac{1}{C} \int_{t_0}^t i_c(x) dx$$

In most of our problems we will

① define  $t_0 = 0$

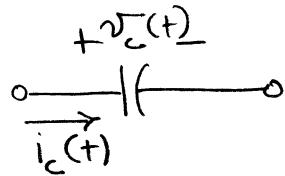② recognize  $V_c(t_0)$  as the initial voltage on the capacitor.



Consider the power  $P_c(t) = i_c(t) V_c(t)$

$$= \left[ C \frac{dV_c}{dt} \right] V_c(t)$$

$$P_c(t) = \frac{d}{dt} \left[ \frac{1}{2} C V_c^2(t) \right]$$

This is VERY interesting.

$P_c(t) > 0$  capacitor absorbing power

$P_c(t) < 0$  capacitor releasing stored power

Since  $P_c(t) = \frac{d}{dt} \left[ \underset{\text{energy in the capacitor}}{\uparrow} W_c(t) \right]$


energy in the capacitor

$$\therefore \text{energy in capacitor } W_c(t) = \frac{1}{2} C V_c^2(t) + \text{constant}$$


$\nearrow 0$   
since  $\xi = 0$  when  $V_c = 0$
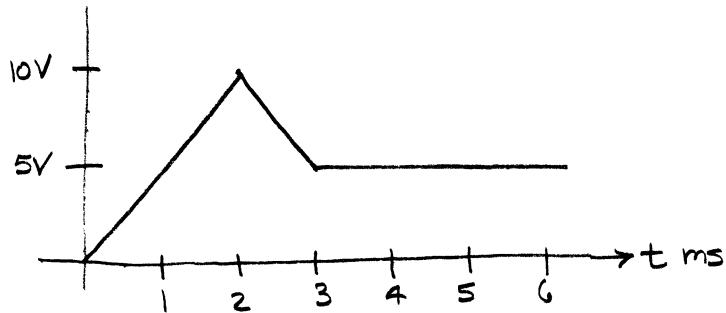
## Example 6-1

If the capacitor voltage is as shown across a  $\frac{1}{2}\mu\text{F}$  capacitor. What is the corresponding current?



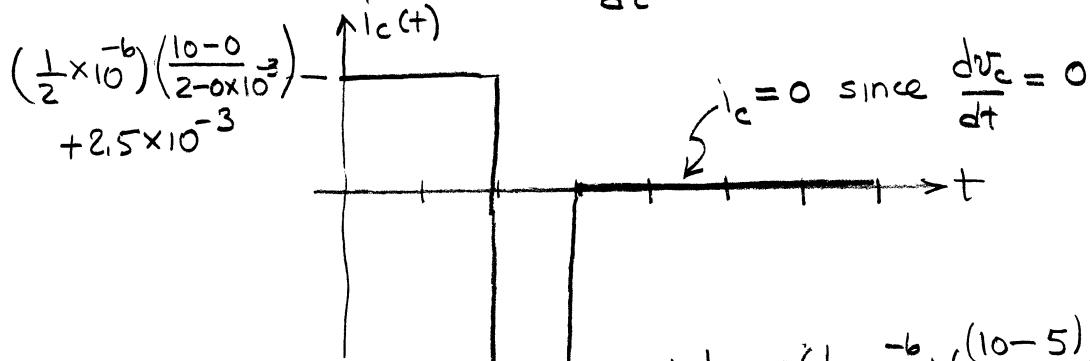Solution: since  $i_c = C \frac{dV_c}{dt}$



$$i_c = -2.5 \times 10^{-3} \text{ A} = -2.5 \text{ mA}$$

## Example 6-2



If  $i_c(t) = I_0 e^{-\frac{t}{T_c}} u(t)$  find  $V_c(t)$  if  $V_c(t=0) = 0$ .

$$i_c = C \frac{dV_c}{dt}$$

$$\frac{1}{C} i_c dt = dV_c$$


$$V_c(t) = V_c(t=0) + \frac{1}{C} \int_0^t I_0 e^{-\frac{x}{T_c}} dx$$
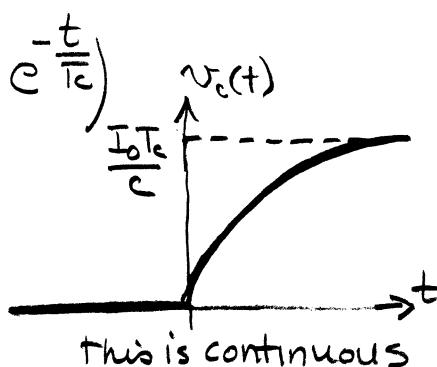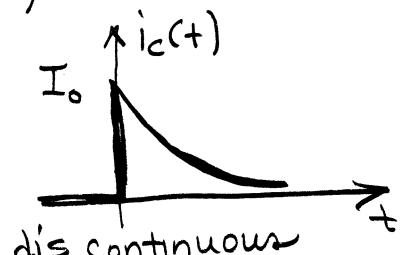
$$V_c(t) = 0 + \frac{I_0}{C} \left[ e^{-\frac{x}{T_c}} \right]_0^t = \frac{I_0 T_c}{C} \left( 1 - e^{-\frac{t}{T_c}} \right)$$



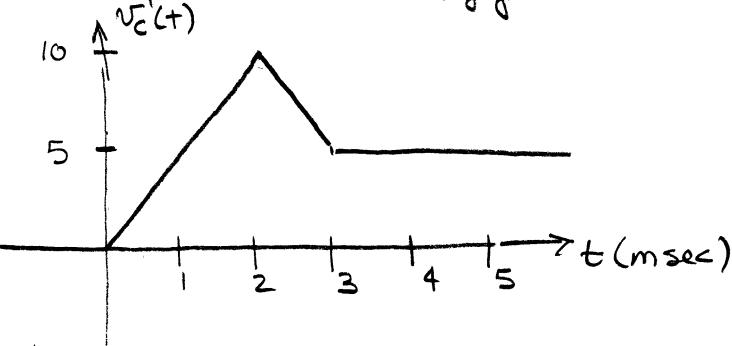
### Example 6-3

The voltage across a capacitor is given below. Find the capacitor's power and energy.




Solution:

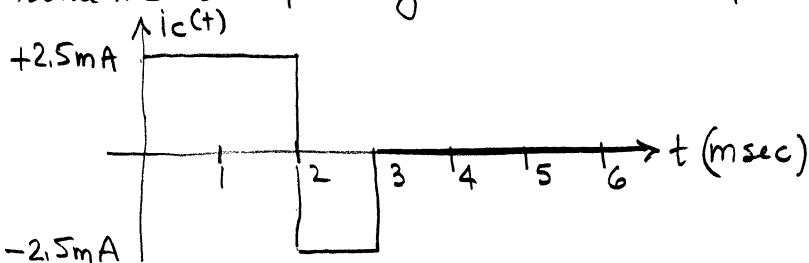We found the corresponding current in Example 6-1.



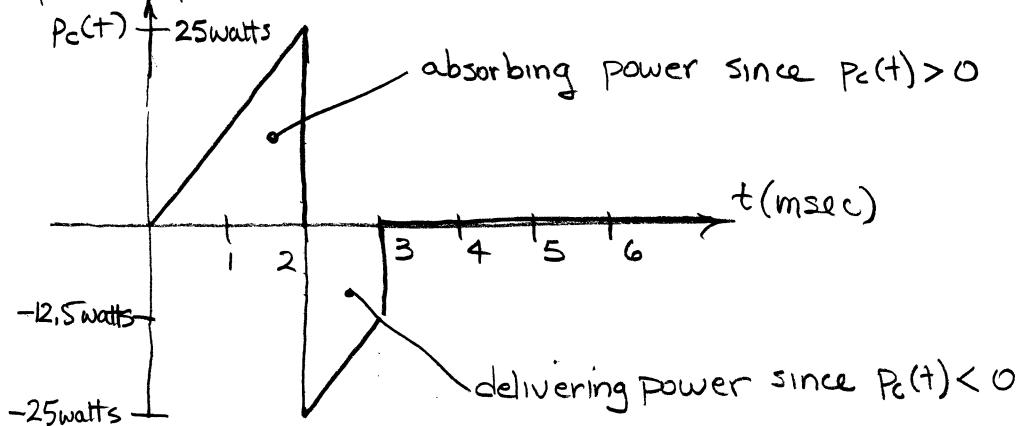
The power  $P_c(t)$  is the product of these waveforms.



$$\text{The energy } W_c = \frac{1}{2} C V^2$$

$$W_c(t=2) = \frac{1}{2} \left(\frac{1}{2} \times 10^{-6}\right) (10)^2 = 25 \times 10^{-6} \text{ J}$$
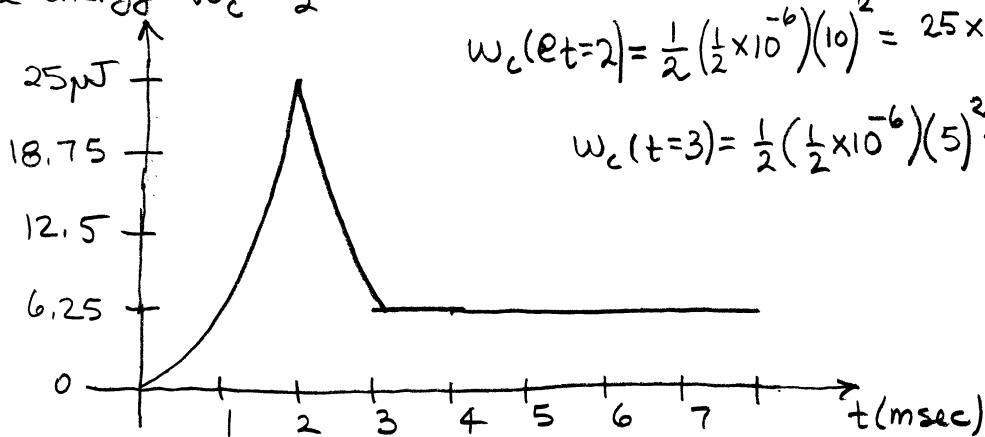
$$W_c(t=3) = \frac{1}{2} \left(\frac{1}{2} \times 10^{-6}\right) (5)^2 = 6.25 \times 10^{-6} \text{ J}$$



### Example 6-4


The current through a capacitor is given by

$$i_c(t) = I_0 e^{-\frac{t}{T_c}} u(t)$$

Find the capacitor's energy and power.

The voltage was found in Example 6-2 to be

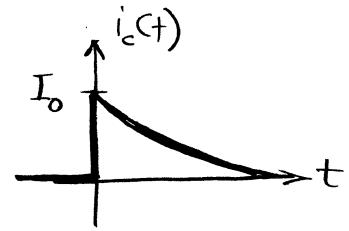
$$v_c(t) = \frac{I_0 T_c}{C} \left[ 1 - e^{-\frac{t}{T_c}} \right]$$



The power is given by  $P_c(t) = i_c(t) v_c(t)$


$$P_c(t) = \left[ I_0 e^{-\frac{t}{T_c}} \right] \left[ \frac{I_0 T_c}{C} \left( 1 - e^{-\frac{t}{T_c}} \right) \right]$$
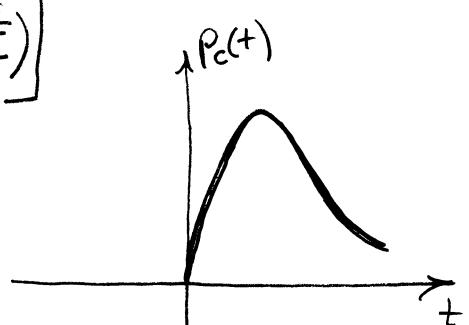
$$P_c(t) = \frac{I_0^2 T_c}{C} \left[ e^{-\frac{t}{T_c}} - e^{-\frac{2t}{T_c}} \right]$$



The energy is most easily calculated as  $w_c(t) = \frac{1}{2} C v_c^2(t)$
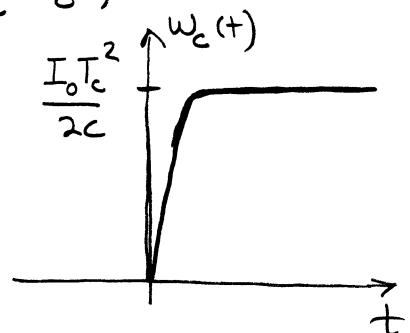
$$w_c(t) = \frac{1}{2} C \left[ \frac{I_0 T_c}{C} \left( 1 - e^{-\frac{t}{T_c}} \right) \right]^2$$




## 6-2 The Inductor

From magneto statics

$$\phi(t) = k_1 N i_L(t)$$

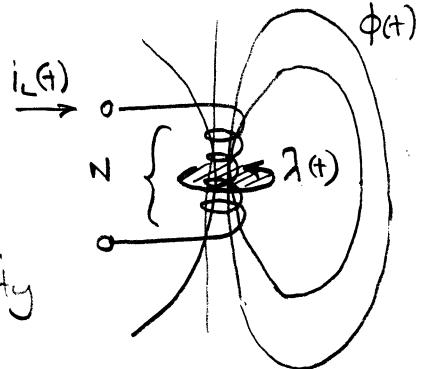↑      ↑      ↑  
 # of turns      constant of proportionality  
 magnetic flux (webers)



$$\lambda(t) = N\phi(t)$$

↑      ↑  
 magnetic flux      # of turns  
 flux linkage, flux/unitarea.

Substituting

$$\lambda(t) = N\phi(t) = N k_1 N i_L(t) = [N^2 k_1] i_L(t)$$

↑  
this is the inductance  $L$

$$\lambda(t) = L i_L(t)$$

Differentiate this to get the  $i$ - $v$  relationship

$$\frac{d\lambda(t)}{dt} = L \frac{di_L(t)}{dt}$$

↑  
by Faraday's Law  $v_L(t) = \frac{d\lambda(t)}{dt}$

$$\therefore v_L(t) = L \frac{di_L(t)}{dt}$$

Observations

- ① If  $i_L(t)$  is constant,  $v_L = 0$  and the inductor looks like a short
- ② A discontinuity  $w(t)$  or  $\delta(t)$  in  $i_L$  would create an infinite voltage so  $i_L(t)$  must be continuous.

We often want  $i_L$  in terms of voltage

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$di_L(t) = \frac{1}{L} v_L(t) dt$$

Assuming  $i_L(t_0)$  is known we can integrate this to get

$$\int_{i_L(t_0)}^{i_L(t)} di_L = \frac{1}{L} \int_{t_0}^t v_L(x) dx$$

$$i_L(t) - i_L(t_0) = \frac{1}{L} \int_{t_0}^t v_L(x) dx$$

$$i_L(t) = i_L(t_0) + \frac{1}{L} \int_0^t v_L(x) dx$$

### Power & energy

$$P_L(t) = i_L(t) v_L(t)$$

$$P_L(t) = i_L(t) L \frac{di_L(t)}{dt}$$

$$P_L(t) = \underbrace{\frac{d}{dt} \left[ \frac{1}{2} L i_L^2(t) \right]}_{\text{recognize this as the energy } w_L \text{ stored in the inductor}}$$

recognize this as the energy  $w_L$  stored in the inductor

$$w_L(t) = \frac{1}{2} L i_L^2(t) + \text{constant}$$


since it is the energy stored when  $i_L = 0$

## Example 6-6

The current through a 2-mH inductor is  $i_L(t) = 4 \sin 1000t + \sin 3000t$   
 Find the corresponding  $v_L(t)$ .

$$\begin{aligned} v_L(t) &= L \frac{di_L}{dt} = L \frac{d}{dt} (4 \sin 1000t + \sin 3000t) \\ &= (.002) [4(1000) \cos 1000t + 3000 \cos 3000t] \end{aligned}$$


$$v_L(t) = 8 \cos 1000t + 6 \cos 3000t$$

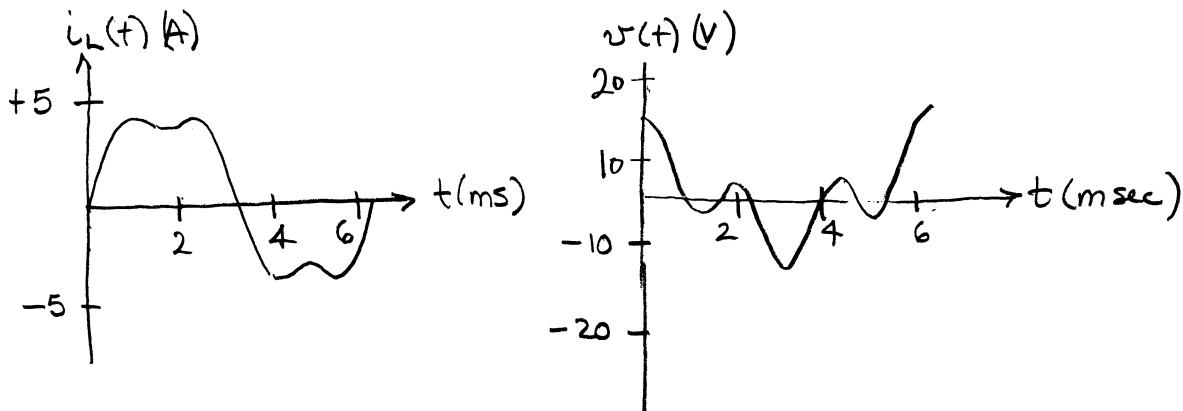

## Example 6-7

The following figures show the current and voltage across an unknown energy storage element.

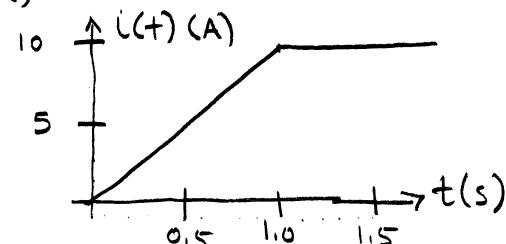(a) What is the element and its numerical value?




This is an inductor since  $v=0$  when  $i = \text{constant}$ .

$$\text{Since } v = L \frac{di}{dt} \text{ for } 0 < t < 1$$

$$0.1 = L \left( \frac{10-0}{1-0} \right) = 10L$$

$$L = .01 \text{ H} = 10 \text{ mH}$$

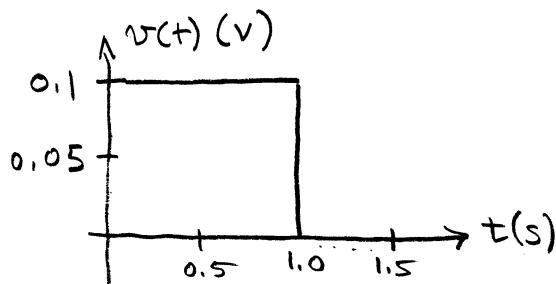

$$\omega_L = \frac{1}{2} L i^2 = \frac{1}{2} (.01)(10)^2 = \frac{1}{2} \text{ J.}$$

(b) What is the energy stored at  $t=1 \text{ sec}$ ?