
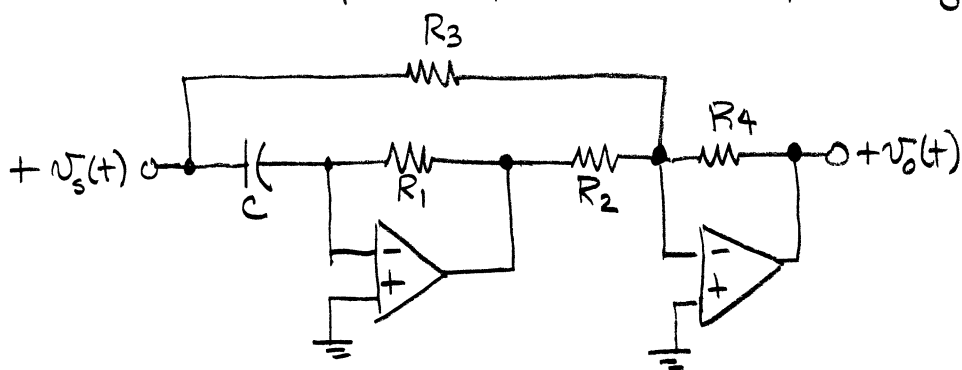


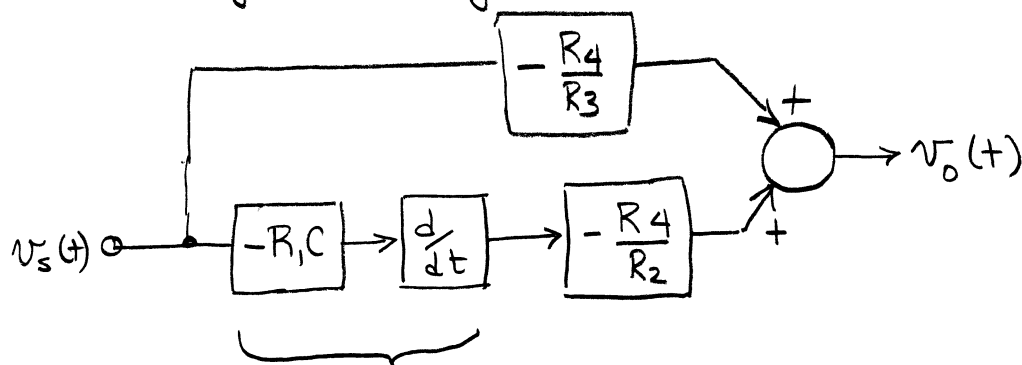Example 6-11

Determine the input-output relationship of the given circuit.



Drawing a block diagram



this is the gain
of the differentiator

we separate it into a gain and a derivative.


The sum of the gains along each path gives

$$\begin{aligned} v_o(t) &= -\frac{R_4}{R_3} v_s(t) + (-R_1 C) \frac{d}{dt} \left[\left(-\frac{R_4}{R_2} \right) v_s(t) \right] \\ &= -\frac{R_4}{R_3} v_s(t) + R_1 C \frac{R_4}{R_2} \frac{d v_s(t)}{dt} \end{aligned}$$

Assuming OP AMPS do not saturate

6-4 Equivalent capacitance & Inductance

N capacitors in parallel

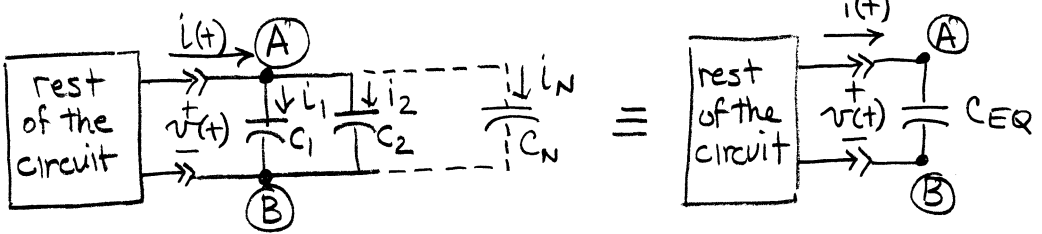

KCL @ A gives

$$i(t) = i_1(t) + i_2(t) + \dots + i_N(t)$$

since the capacitors are in parallel


$$v_1(t) = v_2(t) = \dots = v_N(t) = v(t)$$

$$i(t) = C_1 \frac{dv(t)}{dt} + C_2 \frac{dv(t)}{dt} + \dots + C_N \frac{dv(t)}{dt}$$

$$i(t) = (C_1 + C_2 + \dots + C_N) \frac{dv(t)}{dt} = C_{EQ} \frac{dv(t)}{dt}$$

$$\therefore C_{EQ} = C_1 + C_2 + \dots + C_N$$

N capacitors in series

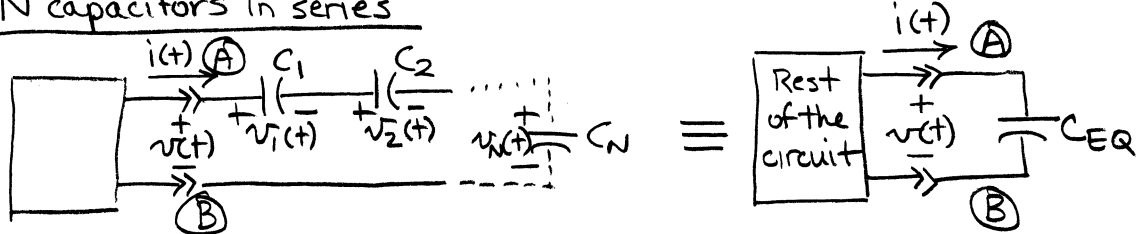

Do KVL around loop $v(t) = v_1(t) + v_2(t) + \dots + v_N(t)$

KCL requires that $i_1(t) = i_2(t) = \dots = i_N(t) = i(t)$

$$v(t) = v_1(0) + \frac{1}{C_1} \int_0^t i(x) dx + v_2(0) + \frac{1}{C_2} \int_0^t i(x) dx + \dots + v_N(0) + \frac{1}{C_N} \int_0^t i(x) dx$$

$$v(t) = [v_1(0) + v_2(0) + \dots + v_N(0)] + \underbrace{\left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right)}_{\frac{1}{C_{EQ}}} \int_0^t i(x) dx$$

$$\therefore \frac{1}{C_{EQ}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

Inductors are the dual of capacitors.

$$L_{EQ} = L_1 + L_2 + \dots + L_N \quad (\text{series connection})$$

$$\frac{1}{L_{EQ}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \quad (\text{parallel connection})$$


DC Equivalent Circuits

Under dc (steady state) conditions



- capacitor acts like an open circuit
- inductor acts like a short circuit

The resulting circuit typically only contains resistors.

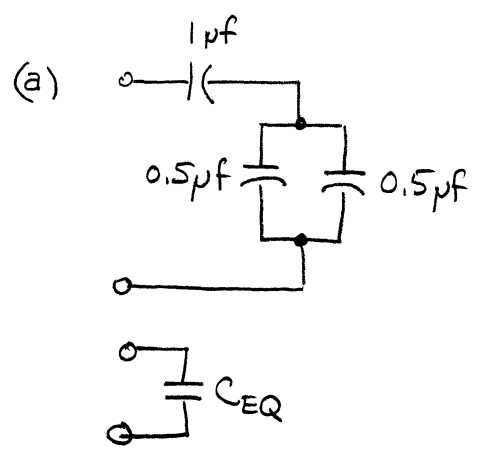
Example 6-14 Find the equivalent capacitances and inductances for the given circuits.



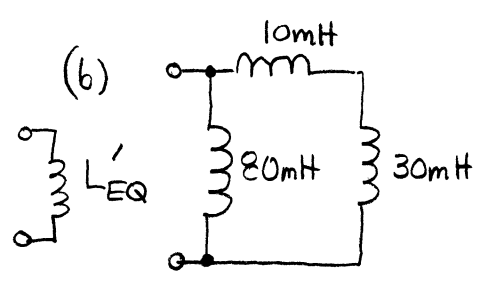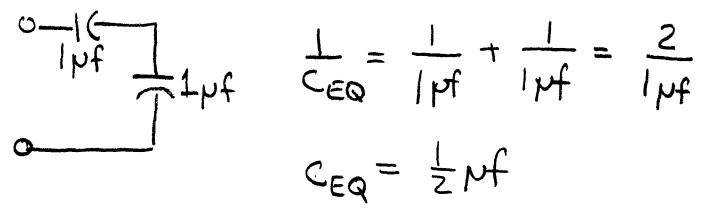The two capacitors in parallel add.
 $0.5 \mu\text{f} + 0.5 \mu\text{f} = 1 \mu\text{f}$.
 This gives the circuit of two capacitors in series.



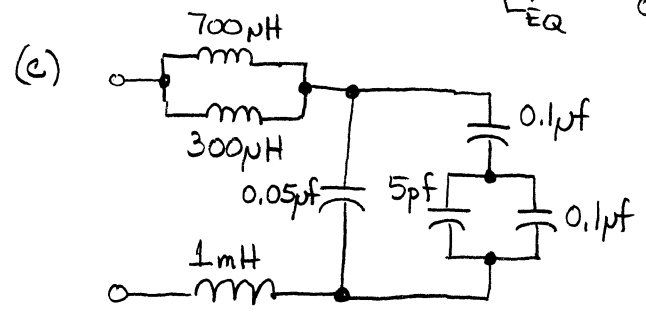The 10 mH and 30 mH are in series and add.
 $L_{EQ} = 10 \text{ mH} + 30 \text{ mH} = 40 \text{ mH}$
 This result is in parallel with the 80 mH inductor.
 $\frac{1}{L'_{EQ}} = \frac{1}{80} + \frac{1}{40} = \frac{3}{80}$ $L'_{EQ} = \frac{80}{3} = 26.67 \text{ mH}$



The inductors and capacitors must be combined separately.
 For the capacitors:
 $5 \text{ pf} \parallel 0.1 \mu\text{f}$ add $0.1 \mu\text{f} + .000005 \mu\text{f} = 0.100005 \mu\text{f}$

This capacitor is in series with the 0.1 pf capacitor,
 $\frac{1}{C_{EQ}} = \frac{1}{0.1 \mu\text{f}} + \frac{1}{0.100005 \mu\text{f}}$ $C_{EQ} \cong 0.050001$


This is in parallel with the 0.05 pf capacitor
 $C'_{EQ} = 0.05 \mu\text{f} + 0.0500001 \mu\text{f} \cong 0.1 \mu\text{f}$.

This completes the capacitance. Proceeding to the inductors.

$700 \text{ pH} \parallel 300 \text{ pH}$ $\frac{1}{L_{EQ}} = \frac{1}{700 \text{ pH}} + \frac{1}{300 \text{ pH}}$ $L_{EQ} = 210 \text{ pH}$


This inductance is essentially in series with the 1 mH inductor

$L'_{EQ} = 1 \text{ mH} + L_{EQ} = 1 \text{ mH} + 210 \text{ pH} = 1210 \text{ pH}$

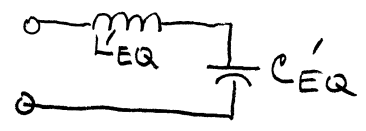


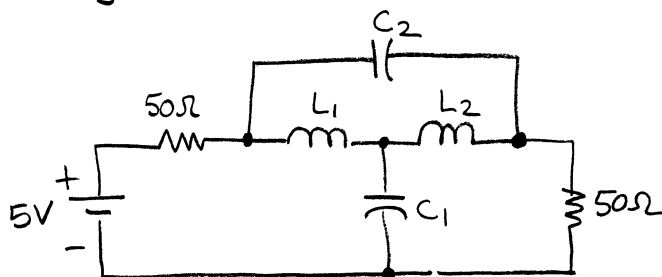Example 6-15


Determine the voltage across the capacitors and current through the inductors in the circuit given below.



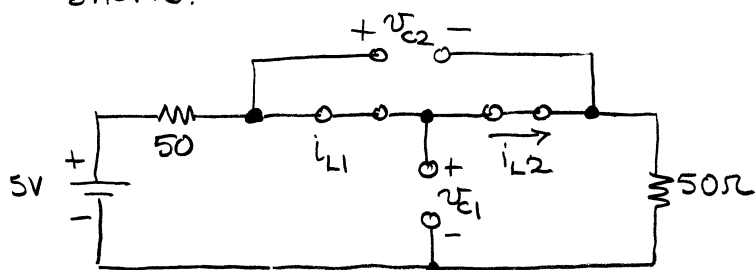This is a DC circuit analysis. The capacitors are opens since they are fully charged. The inductors are correspondingly shorts.



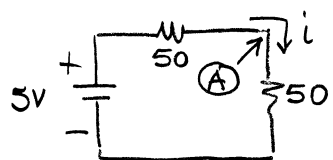
This is basically a two resistor series circuit.



$$i = \frac{5V}{50+50} = 0.050 \text{ A}$$


The voltage at (A) is $v_A = iR$
 $v_A = (0.05)(50) = 2.5V$

The circuit values are then

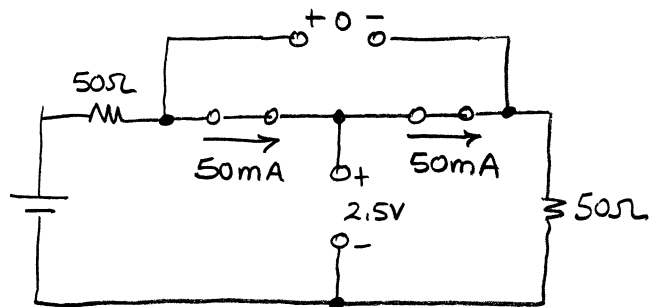


Exercise 6-11

Find the OP AMP output voltage.

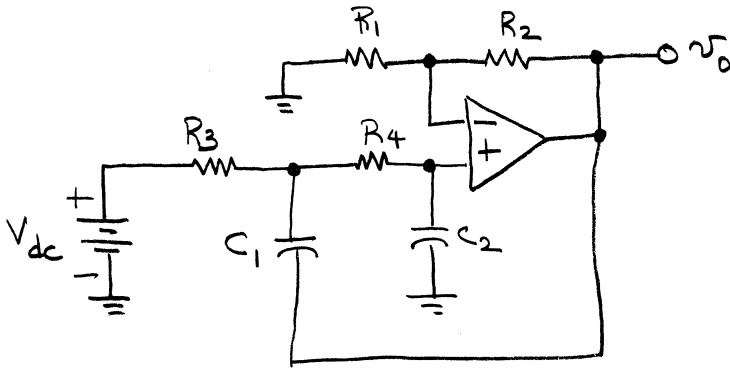


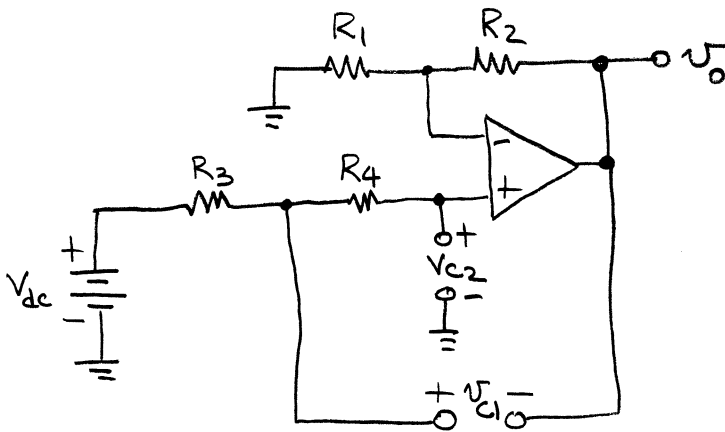Since this is a dc circuit we replace the capacitors by open circuits and solve.



There is no current i_p into the OP AMP so there are no voltage drops across either R_3 or R_4 . $\Rightarrow V_p = V_{dc}$

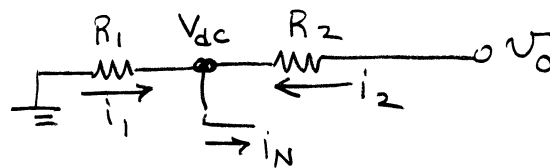Since $V_p = V_{dc} = V_n$ we can analyze the inverting side of the OP AMP.



Using KCL $\sum i = 0$

$$i_1 - i_n + i_2 = 0$$

$$\frac{0 - V_{dc}}{R_1} + \frac{v_o - V_{dc}}{R_2} = 0$$

$$\therefore \frac{v_o}{R_2} = V_{dc} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$v_o = \frac{R_1 + R_2}{R_1 R_2} V_{dc}$$

Note that: $V_{c2} = V_{dc} - 0 = V_{dc}$

$$V_{c1} = V_{dc} - \frac{R_1 + R_2}{R_2} V_{dc} = \frac{2R_2 - R_1}{R_2} V_{dc}$$