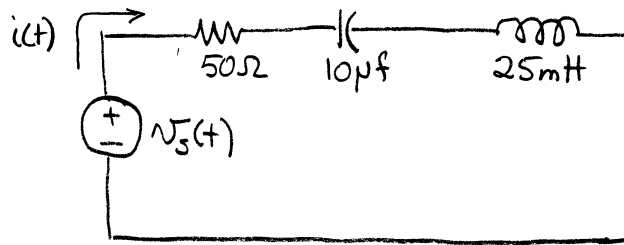


## Example 8-6

The circuit shown below is operating in the sinusoidal steady state with  $v_s(t) = 35 \cos 1000t$ .




(a) Transform the circuit into the phasor domain.

$$Z_R = R = 50$$

$$Z_L = j\omega L = j(1000)(25 \times 10^{-3}) = j25$$
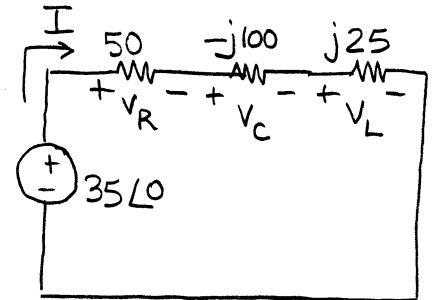
$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(1000)(10 \times 10^{-6})} = -j100$$



(b) Solve for the phasor current  $\underline{I}$ .

$$Z_{EQ} = Z_R + Z_L + Z_C = 50 + j25 - j100 = 50 - j75 = 90.14 \angle -56.3^\circ$$

$$\underline{I} = \frac{\underline{V}}{\underline{Z}} = \frac{35 \angle 0^\circ}{90.14 \angle -56.3^\circ} = \frac{35}{50 - j75} = 0.215 + j0.323 = 0.388 \angle 56.3^\circ$$

(c) Solve for the phasor voltage across each element

$$\underline{V}_R = Z_R \underline{I} = 50 (0.215 + j0.323) = 10.75 + j16.15 = 19.4 \angle +56.4^\circ$$

$$\underline{V}_C = Z_C \underline{I} = (-j100)(0.215 + j0.323) = +32.3 - j21.5 = 38.8 \angle +146.4^\circ$$

$$\underline{V}_L = Z_L \underline{I} = (j25)(0.215 + j0.323) = -8.075 + j5.375 = 9.70 \angle -33.65^\circ$$

(d) Construct the waveforms corresponding to the phasors found in (a) and (b)

$$i(t) = 0.388 \cos(1000t + 56.3^\circ)$$


$$v_R(t) = 19.4 \cos(1000t + 56.4^\circ)$$

$$v_C(t) = 38.8 \cos(1000t + 146.4^\circ)$$

$$v_L(t) = 9.70 \cos(1000t - 33.65^\circ)$$
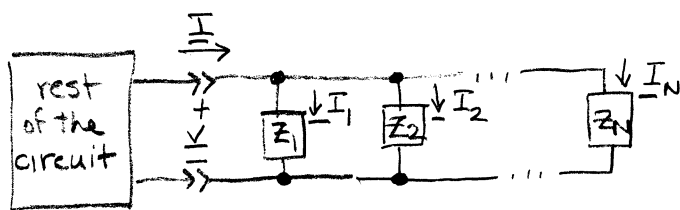
## Parallel equivalence and current division

When impedances are connected in parallel as shown below we may use KCL to compute an equivalent impedance



$$I = I_1 + I_2 + \dots + I_N$$

$$= \frac{V}{Z_1} + \frac{V}{Z_2} + \dots + \frac{V}{Z_N} = \left( \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \right) V$$

$$\frac{1}{Z_{EQ}} = \frac{I}{V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}$$


We often use the admittance  $Y$

$$Y = \frac{1}{Z} = G + jB$$

↑ conductance
 ↑ susceptance
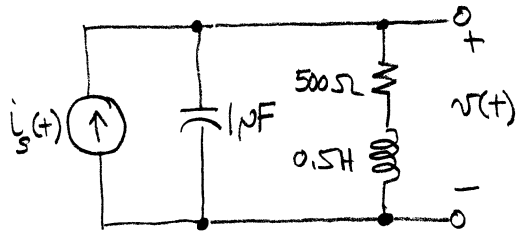
## Example 8-9

The circuit shown below is operating in sinusoidal steady state with  $i_s(t) = 50 \cos 2000t$  mA.




(a) Transform the circuit into the phasor domain.

$$Z_R = R = 500 \Omega$$

$$Z_L = j\omega L = j(2000)(0.5) = j1000$$
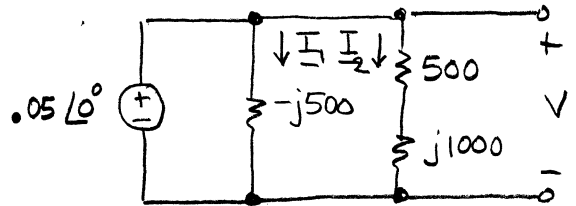
$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(2000)(1 \times 10^{-6})} = -j500$$



(b) Solve for the phasor voltage  $\underline{V}$

$$Z_{EQ} = (-j500) \parallel (500 + j1000) = \frac{(-j500)(500 + j1000)}{-j500 + 500 + j1000} = 250 - j750$$

$$\underline{V} = \underline{I} Z_{EQ} = (0.05 \angle 0^\circ)(250 - j750) = 12.5 - j37.5 = 39.5 \angle -71.6^\circ$$

(c) Solve for the phasor current through each branch.

$$\underline{I}_1 = \frac{\underline{V}}{-j500} = \frac{12.5 - j37.5}{-j500} = 0.075 + j0.025 = 0.079 \angle 18.4^\circ$$

$$\underline{I}_2 = \frac{\underline{V}}{500 + j1000} = \frac{12.5 - j37.5}{500 + j1000} = -0.025 - j0.025 = 0.035 \angle -135^\circ$$

(d) Construct the wave forms corresponding to the phasors found in (b) and (c),


$$v(t) = \text{Re} [39.5 e^{-j71.6^\circ} e^{j2000t}] = 39.5 \cos(2000t - 71.6^\circ)$$

$$i_1(t) = \text{Re} [0.079 e^{j18.4^\circ} e^{j2000t}] = 0.079 \cos(2000t - 18.4^\circ)$$

$$i_2(t) = \text{Re} [0.035 e^{-j135^\circ} e^{j2000t}] = 0.035 \cos(2000t - 135^\circ)$$
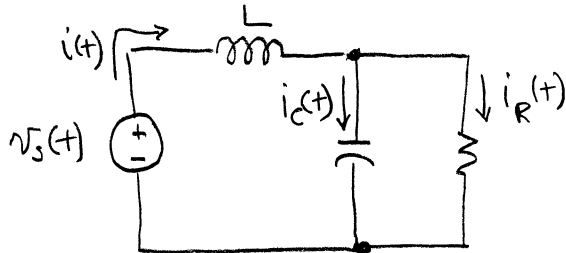
## Example 8-10

Find the steady-state currents  $i(t)$ ,  $i_C(t)$  and  $i_R(t)$  in the circuit below for  $v_s(t) = 100 \cos 2000t$ ,  $L = 250 \text{ mH}$ ,  $C = 0.05 \mu\text{F}$ , and  $R = 3 \text{ k}\Omega$ .




Converting to phasors.

$$Z_L = j\omega L = j(2000)(250 \times 10^{-3}) = j500$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(2000)(0.05 \times 10^{-6})} = -j1000$$

$$Z_R = 3000$$

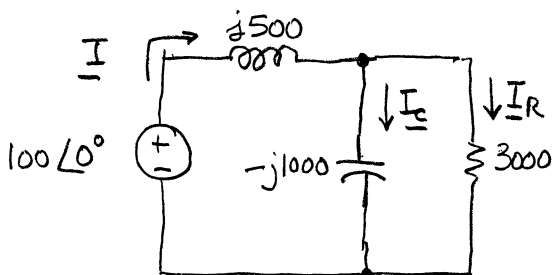

$$Z_{EQ} = j500 + (3000) \parallel (-j1000)$$

$$= j500 + \frac{(3000)(-j1000)}{3000 - j1000}$$

$$= j500 + 300 - j900$$

$$Z_{EQ} = 300 - j400$$

$$\underline{I} = \frac{\underline{V}}{Z_{EQ}} = \frac{100 \angle 0^\circ}{300 - j400} = 0.12 + j0.16 = 0.2 \angle 53.1^\circ$$

We can now use current division to find  $\underline{I}_C$  and  $\underline{I}_R$

$$\underline{I}_C = \frac{3000}{3000 - j1000} (0.12 + j0.16) = 0.06 + j0.18 = 0.190 \angle 71.56^\circ$$

$$\underline{I}_R = \frac{-j1000}{3000 - j1000} (0.12 + j0.16) = 0.06 - j0.02 = 0.063 \angle -18.43^\circ$$


$$i(t) = \text{Re} \{ 0.2 e^{j53.1^\circ} e^{j2000t} \} = 0.2 \cos(2000t + 53.1^\circ)$$

$$i_C(t) = \text{Re} \{ 0.190 e^{j71.56^\circ} e^{j2000t} \} = 0.190 \cos(2000t + 71.56^\circ)$$

$$i_R(t) = \text{Re} \{ 0.063 e^{-j18.43^\circ} e^{j2000t} \} = 0.063 \cos(2000t - 18.43^\circ)$$
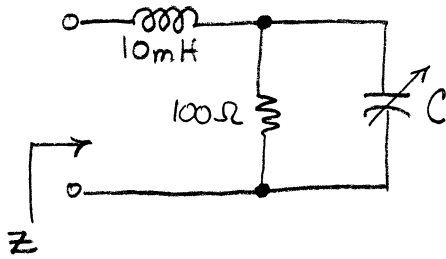
## Example 8-12

The circuit shown below is operating in the sinusoidal steady state with  $\omega = 5000$ .



- (a) Find the value of  $C$  that causes the input impedance  $Z$  to be purely resistive.

$$Z_R = 100 \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(5000)C} = \frac{1}{j5000C}$$

$$Z_L = j\omega L = j(5000)(10 \times 10^{-3}) = j50$$

$$Z = j50 + \frac{1}{\frac{1}{j5000C} \parallel 100} = j50 + \frac{\frac{1}{j5000C} \cdot 100}{\frac{1}{j5000C} + 100} = j50 + \frac{100}{1 + j5 \times 10^5 C}$$

$$Z = j50 + \frac{100(1 - j5 \times 10^5 C)}{(1 + j5 \times 10^5 C)(1 - j5 \times 10^5 C)} = j50 + \frac{100 - j5 \times 10^7 C}{1 + (5 \times 10^5 C)^2}$$

$$Z = j50 + \frac{100}{1 + (5 \times 10^5 C)^2} - j \frac{5 \times 10^7 C}{1 + (5 \times 10^5 C)^2}$$

$$\text{Set } 50 - \frac{5 \times 10^7 C}{1 + (5 \times 10^5 C)^2} = 0$$

$$\cancel{50} + \cancel{50}(5 \times 10^5 C)^2 - \cancel{5} \times 10^7 C = 0$$

$$25 \times 10^{11} C^2 - 10^7 C + 10 = 0$$

$$25 \times 10^{10} C^2 - 10^6 C + 10 = 0$$

$$C = \frac{+10^6 \pm \sqrt{(10^6)^2 - 4(25 \times 10^{10})(10)}}{2(25 \times 10^{10})} = 2 \times 10^{-6} \text{ F}$$

- (b) Find the real part of the input impedance for this value of  $C$


$$Z_{\text{real}} = \frac{100}{1 + ((5 \times 10^5)(2 \times 10^{-6}))^2} = \frac{100}{1 + 1} = 50 \Omega$$

# Chapter 12 - Frequency Response

frequency response - frequency dependent relationship (including both magnitude and phase) between a sinusoidal input and the resulting sinusoidal steady-state output

Bode diagram - plots of magnitude and phase versus logarithmic frequency

## 12-1 Frequency Response descriptors

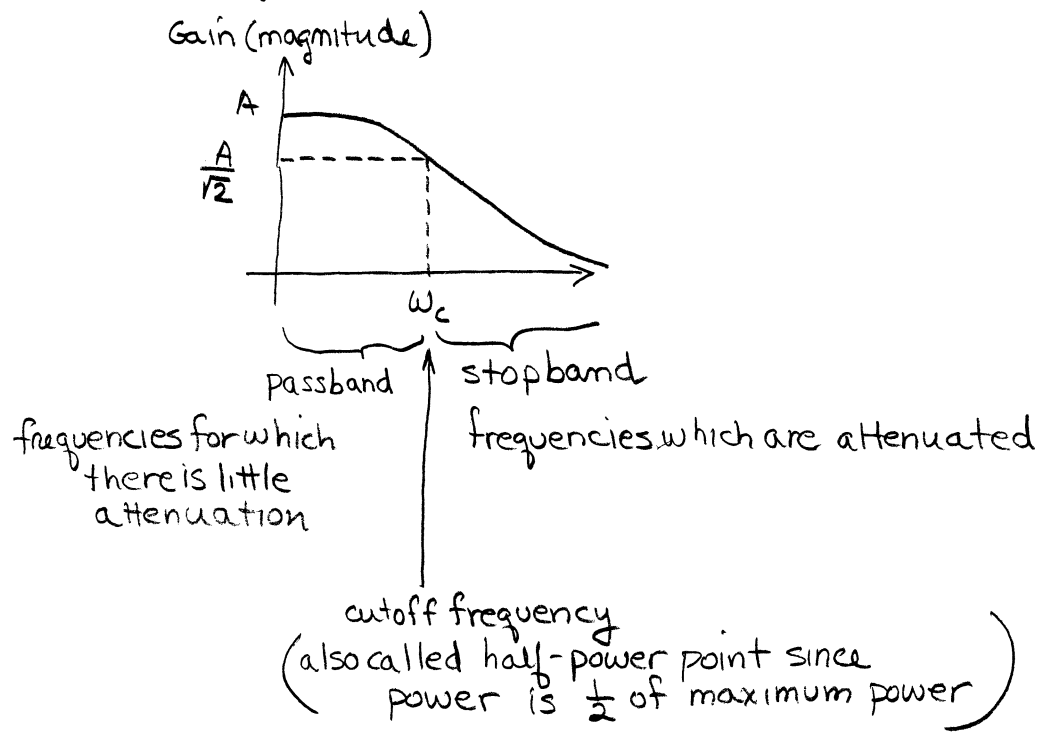

### Different types of responses

