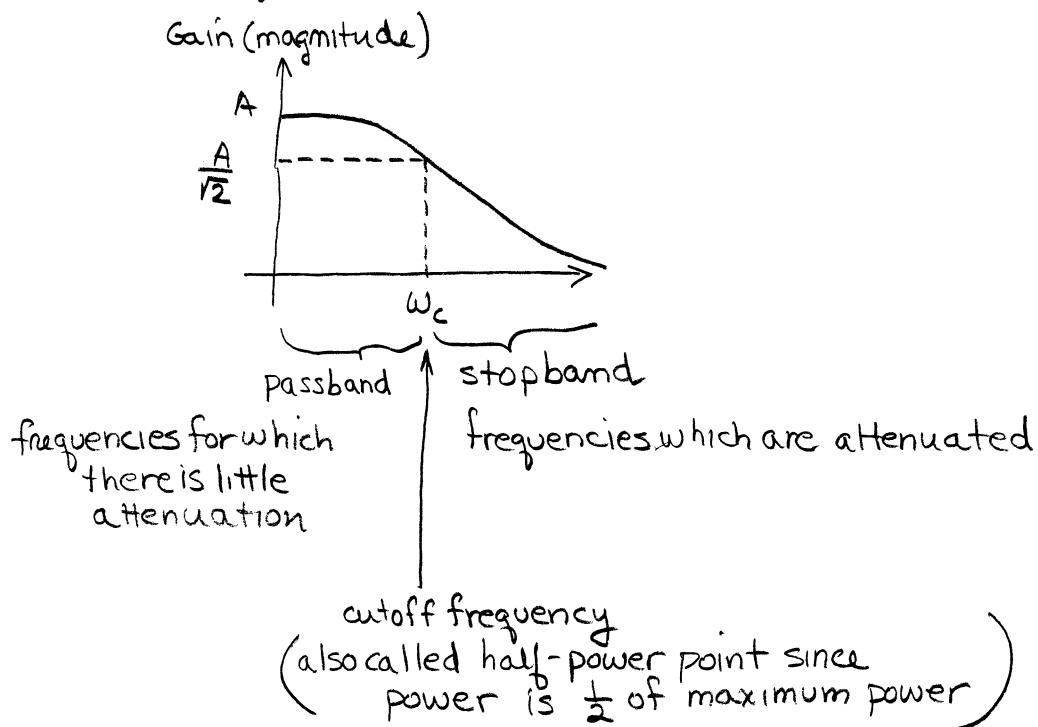


Chapter 12 - Frequency Response


frequency response — frequency dependent relationship (including both magnitude and phase) between a sinusoidal input and the resulting sinusoidal steady-state output

Bode diagram — plots of magnitude and phase versus logarithmic frequency

12-1 Frequency Response descriptors



Different types of responses

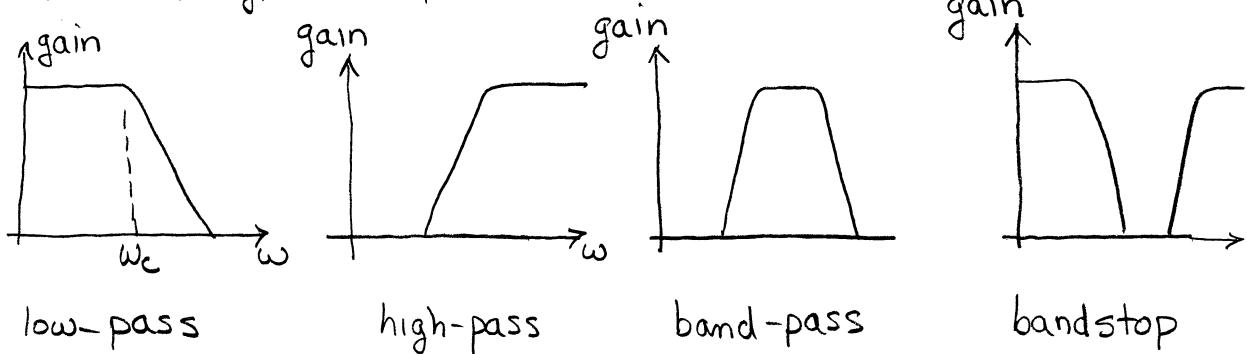

The sinusoidal steady-state output is given by the gain function $|T(j\omega)|$ and the phase function $\Theta(\omega)$.

$$\text{Output amplitude} = |T(j\omega)| \times \text{Input amplitude}$$

$$\text{Output phase} = \text{Input phase} + \Theta(\omega)$$

octave: 2:1 range of frequencies

decade: 10:1 range of frequencies

In Bode plots the gain $|T(j\omega)|$ is usually expressed in decibels

$$|T(j\omega)|_{\text{dB}} = 20 \log_{10} |T(j\omega)|$$

Since the cutoff frequency occurs for the gain reduced to $\frac{1}{\sqrt{2}}$
this is a gain reduction of

$$\begin{aligned} 20 \log_{10} \left(\frac{1}{\sqrt{2}} |T_{\text{MAX}}| \right) &= 20 \log_{10} |T_{\text{MAX}}| - 20 \log_{10} \sqrt{2} \\ &= |T_{\text{MAX}}|_{\text{dB}} - 3 \text{dB} \end{aligned}$$

∴ cutoff frequency is often called the 3-dB down frequency

We will concentrate on the gain (magnitude) response.

12-2 First Order Circuit Frequency Response

Consider the first-order low-pass transfer function

$$T(j\omega) = \frac{K}{\alpha + j\omega} = \frac{|K| e^{jLK}}{\sqrt{\alpha^2 + \omega^2} e^{j\tan^{-1}(\frac{\omega}{\alpha})}}$$


$$|T(j\omega)| = \frac{|K|}{\sqrt{\alpha^2 + \omega^2}}$$

↑
simple magnitude division of the numerator by the denominator

$$\theta(\omega) = LK - \tan^{-1}\left(\frac{\omega}{\alpha}\right)$$

↑
this is simply the phase of the numerator minus the phase of the denominator

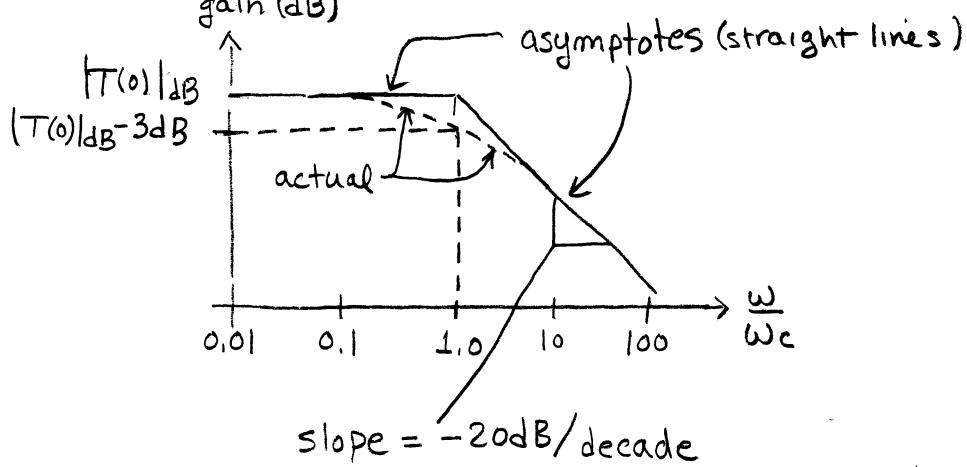We can plot the magnitude response by approximating it as straight lines.



Typical response is $T(j\omega) = \frac{K/\alpha}{1 + j\omega/\alpha}$

write as sum of log terms $20 \log_{10} |T(j\omega)| = \underbrace{20 \log_{10} \left| \frac{K}{\alpha} \right|}_{\text{plot as a straight line}} - \underbrace{20 \log_{10} \left| 1 + j\frac{\omega}{\alpha} \right|}_{\text{also plot as a straight line}}$

this just a constant

for $\omega < \alpha$ $j\frac{\omega}{\alpha} \ll 1$ and we approximate $1 + j\frac{\omega}{\alpha}$ as simply 1

for $\omega > \alpha$ $j\frac{\omega}{\alpha} \gg 1$ and we approximate $1 + j\frac{\omega}{\alpha}$ as $\frac{\omega}{\alpha}$


As ω increases by a factor of 10 (a decade)

$20 \log_{10} \left| \frac{\omega}{\alpha} \right|$ increases by 20 since $\frac{\omega}{\alpha}$ increased by 10¹

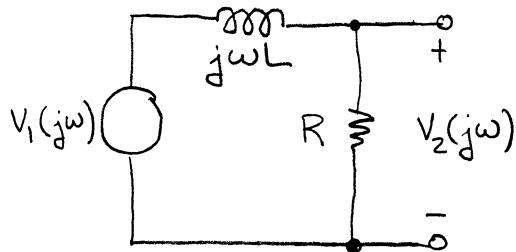Example 12-2


Consider the circuit shown below. Find the transfer function

$T(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)}$ and construct the straight line approximations to the gain response.



$$\text{Using voltage division } T(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{R}{R+j\omega L} = \frac{1}{1+j\frac{\omega L}{R}}$$

$$20 \log |T(j\omega)| = 20 \log(1) - 20 \log |1+j\frac{\omega L}{R}|$$

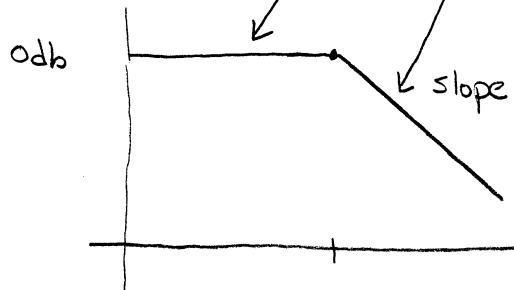

want all terms
to be in terms
of $1 + (\)\omega$

because of the minus sign due
to denominator

cutoff for each term $\omega_c \frac{L}{R} = 1$

$$\text{or } \omega_c = \frac{R}{L}$$