
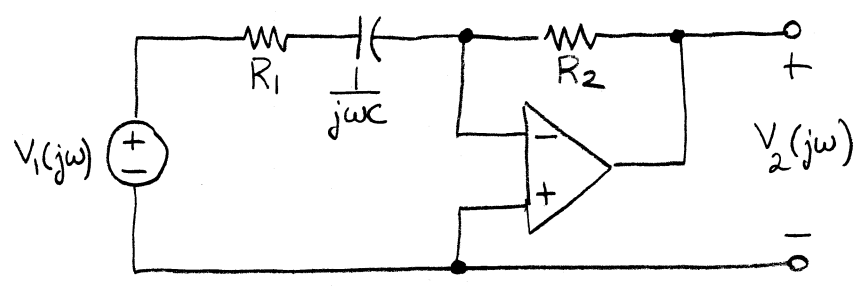


Design Example 12-6

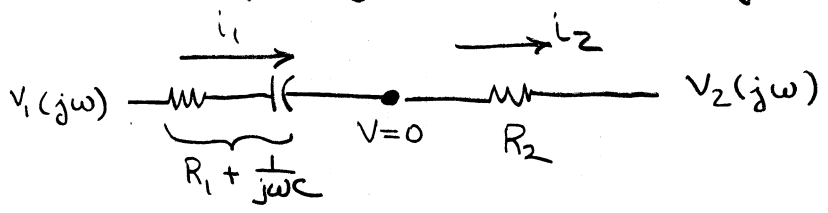Show that the transfer function  $T(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)}$  of the circuit shown below has a high-pass gain characteristic,



We solve by using KCL at the inverting node.



From KCL  $i_1 = i_2$

$$\frac{V_1(j\omega) - 0}{R_1 + \frac{1}{j\omega C}} = \frac{0 - V_2(j\omega)}{R_2}$$

$$R_2 V_1(j\omega) = -V_2(j\omega) \left[ R_1 + \frac{1}{j\omega C} \right] = -V_2(j\omega) \left[ \frac{j\omega R_1 C + 1}{j\omega C} \right]$$

Cross-multiplying and re-arranging

$$T(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = - \frac{j\omega R_2 C}{1 + j\omega R_1 C}$$

$$20 \log_{10} |T(j\omega)| = 20 \log_{10} |\omega R_1 C| - 20 \log_{10} |1 + j\omega R_1 C|$$

