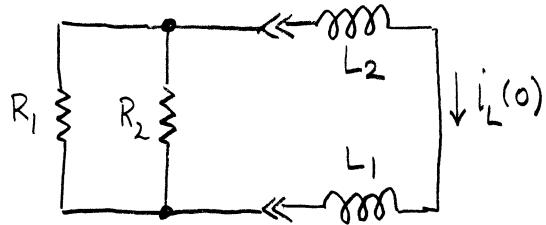


### Example 7-2


Find the response of the state variable of the RL circuit in the figure below using  $L_1 = 10\text{mH}$ ,  $L_2 = 30\text{mH}$ ,  $R_1 = 2\text{k}\Omega$ ,  $R_2 = 6\text{k}\Omega$ , and  $i_L(0) = 100\text{mA}$ .



The inductors are in series and can be replaced by an equivalent  $L_{EQ}$ .

$$L_{EQ} = L_1 + L_2 = 10\text{mH} + 30\text{mH} = 40\text{mH}$$

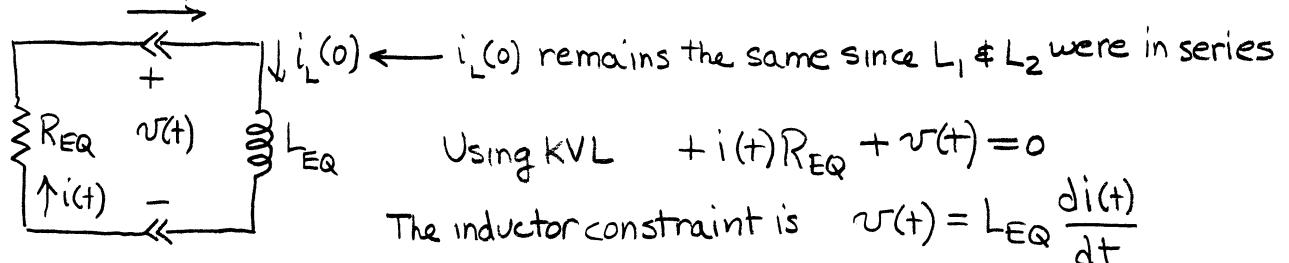The resistors are in parallel and can be replaced by  $R_{EQ} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(2k)(6k)}{2k+6k} = 1.5k$



$$\text{Using KVL } +i(t)R_{EQ} + v(t) = 0$$

$$\text{The inductor constraint is } v(t) = L_{EQ} \frac{di(t)}{dt}$$

$$i(t)R_{EQ} + L_{EQ} \frac{di(t)}{dt} = 0$$

$$\frac{L_{EQ}}{R_{EQ}} \frac{di(t)}{dt} + i(t) = 0$$

Assume  $i(t) = Ke^{st}$ , then

$$\frac{L_{EQ}}{R_{EQ}} Kse^{st} + Ke^{st} = 0$$

$$\frac{L_{EQ}}{R_{EQ}} s + 1 = 0 \Rightarrow s = -\frac{R_{EQ}}{L_{EQ}} = -\frac{1500}{40 \times 10^{-3}}$$


$$s = -37500$$

$$\therefore i(t) = Ke^{-37500t} = Ke^{-\frac{t}{26.7\mu s}}$$

$$i(t=0) = Ke^0 = 100\text{mA}$$

$$\therefore i(t) = 0.1e^{-\frac{t}{26.7\mu s}} \text{ A.}$$

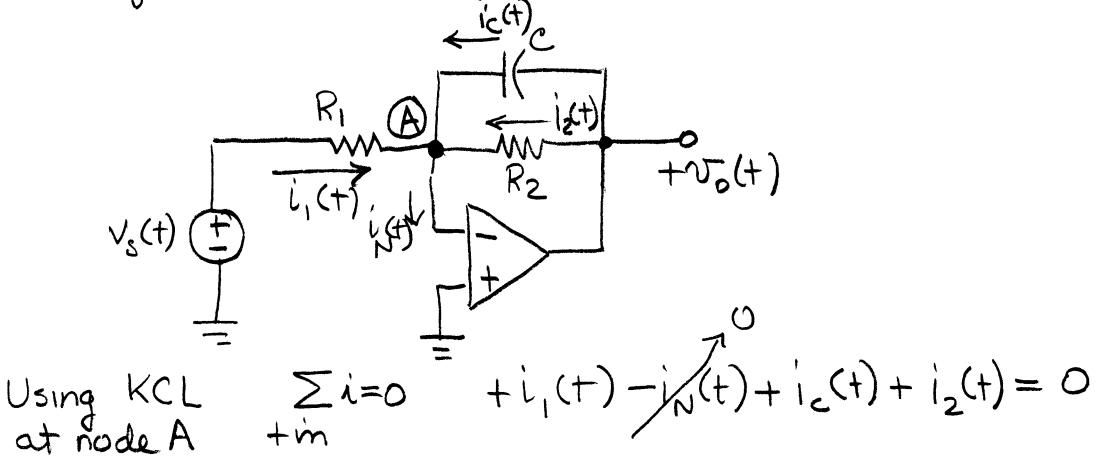consider a circuit which is difficult to Thevenize.  
Derive equations in terms of a more convenient variable.



$$\frac{V_s - 0}{R_1} + 0 + C \frac{d}{dt} (v_o - 0) + \frac{v_o - 0}{R_2} = 0$$


$$C \frac{d v_o}{d t} + \frac{v_o}{R_2} = - \frac{V_s}{R_1}$$

$$R_2 C \underbrace{\frac{d v_o}{d t}}_{\text{differential equation in } v_o} + v_o = - \frac{R_2}{R_1} V_s(t)$$

differential equation in  $v_o$   
rather than the  
capacitor voltage  $v_c$

## 7-2 First Order Circuit Step Response

Consider the following circuit

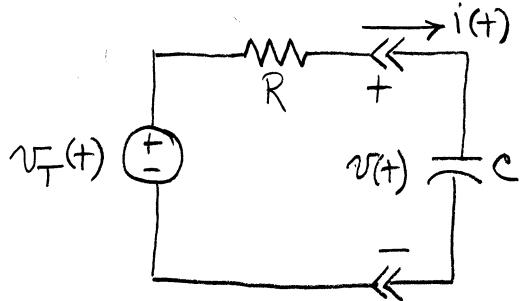

We solved this circuit previously for  $v_T(t) = 0, t \geq 0$

Consider the case where  $v_T(t) = V_A u(t)$

The circuit differential equation is

$$R_T C \frac{dv}{dt} + v = V_A u(t)$$

$$\text{or } R_T C \frac{dv}{dt} + v = V_A \quad \text{for } t \geq 0$$

While there are many methods to solve this equation  
we will use superposition.

$$v(t) = \underbrace{v_N(t)}_{\substack{\text{natural response} \\ \text{when input is} \\ \text{set to zero.}}} + \underbrace{v_F(t)}_{\substack{\text{forced response} \\ \text{to the input} \\ \text{step function}}}$$

Natural response:

$$R_T C \frac{dv_N}{dt} + v_N = 0$$

$$-\frac{t}{R_T C}$$

$$\text{Solution is } v_N(t) = K e^{-\frac{t}{R_T C}} \quad t \geq 0$$

which we have seen previously.

### Forced response

$$R_T C \frac{dV_F(t)}{dt} + V_F(t) = V_A \quad t \geq 0$$

A solution is  $V_F(t) = V_A \quad t \geq 0$


since  $\frac{dV_F}{dt} = 0$  for  $t > 0$

The Total response is the sum of the natural and forced response,

$$v(t) = v_N(t) + v_F(t)$$

$$v(t) = k e^{-\frac{t}{R_T C}} + V_A$$

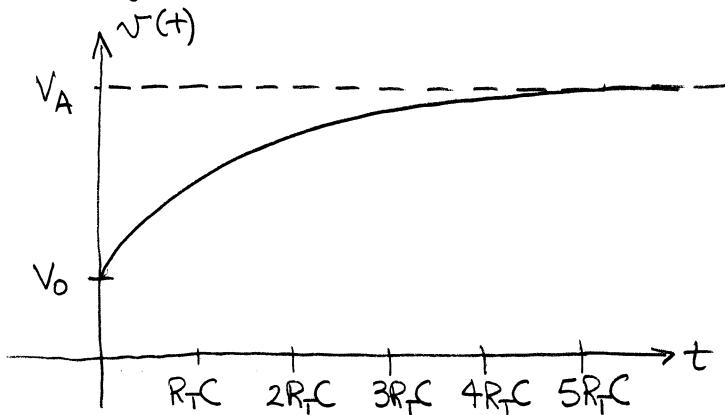This is the general solution and is plotted below.




From this plot we can easily see that

$$\lim_{t \rightarrow 0^+} v(t) = V_0 \quad \text{initial value}$$

$$\lim_{t \rightarrow \infty} v(t) = V_A \quad \text{final value}$$

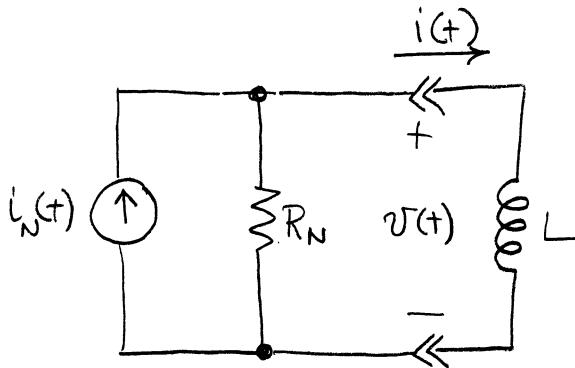For a RL circuit  
with a  $I_A$ ,  $U(t)$   
input,



The differential equation is  $\frac{L}{R_N} \frac{di(t)}{dt} + i(t) = I_A$  for  $t \geq 0$

The natural response  $\frac{L}{R_N} \frac{di_N}{dt} + i_N = 0$

has the solution  $i_N(t) = ke^{-\frac{R_N t}{L}} = ke^{-\frac{t}{L/R_N}}$  for  $t \geq 0$

The forced response is from  $\frac{L}{R_N} \frac{di_F}{dt} + i_F = I_A$  for  $t \geq 0$


which has solution  $i_F(t) = I_A$  for  $t \geq 0$

The general solution is then

$$i(t) = i_N(t) + i_F(t) = ke^{-\frac{t}{L/R_N}} + I_A \quad t \geq 0$$

A step function drives the state variable from an initial value (determined by what happened for  $t < 0$ ) to a final value (determined by the magnitude of the step at  $t = 0$ )

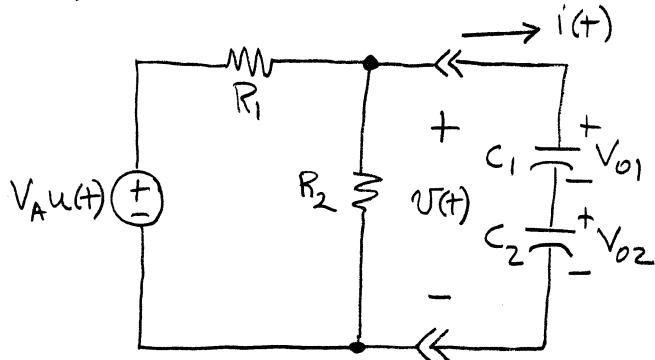Example 7-4 Find the response of the given RC circuit.



$$V_A = 100 \text{ V}$$

at  $t=0$   $V_{o1} = 5 \text{ V}$

$$V_{o2} = 10 \text{ V}$$

$$C_1 = 0.1 \mu\text{F}$$

$$C_2 = 0.5 \mu\text{F}$$

$$R_1 = 30 \text{ k}\Omega$$

$$R_2 = 10 \text{ k}\Omega$$

The two capacitors can be replaced by a single equivalent capacitor


$$C_{EQ} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2}$$

$$C_{EQ} = \frac{(0.1)(0.5)}{0.1 + 0.5} = 0.0833 \mu\text{F}$$

The initial voltage on  $C_{EQ}$  is the sum of the initial voltages on  $C_1$  and  $C_2$

$$V_0 = V_{o1} + V_{o2} = 5 + 10 = 15 \text{ volts.}$$

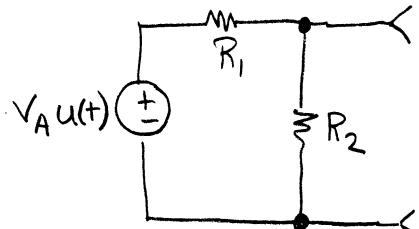We next find the Thevenin equivalent seen by  $C_{EQ}$ .




$$V_T = V_{o2} = \frac{R_2}{R_1 + R_2} V_A u(t) = \frac{10k}{30k + 10k} 100 u(t)$$

$$V_T(t) = 25 u(t)$$

Replacing the voltage source by a short we see that

$$R_T = R_1 \parallel R_2 = \frac{(30k)(10k)}{30k + 10k} = 7.5k$$
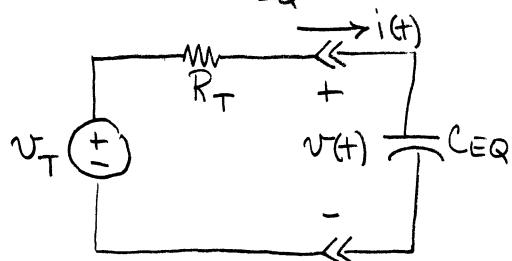
$$\tau_c = R_T C_{EQ} = (7.5 \times 10^3)(0.0833 \times 10^{-6}) = 0.625 \text{ ms}$$



The circuit equation is

$$-V_T(t) + i(t)R_T + V(t) = 0$$

$$\text{but } i(t) = C_{EQ} \frac{dV(t)}{dt}$$

$$-V_T(t) + R_T C_{EQ} \frac{dV(t)}{dt} + V(t) = 0$$

$$R_T C_{EQ} \frac{dV(t)}{dt} + V(t) = V_T(t)$$