
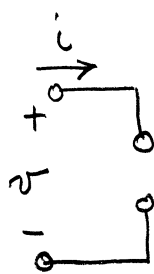


Open and short circuits, switches

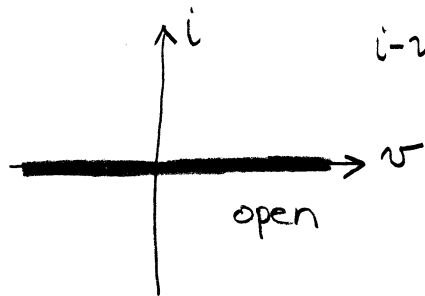


open




$i-v$ characteristic

open

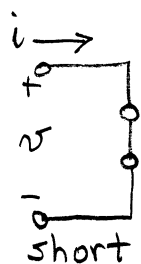


short

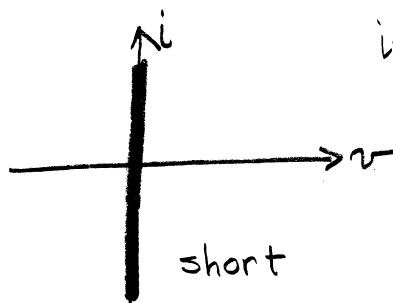

$i-v$ characteristic

short

ideal switch

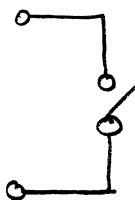

open position
(OFF)




closed position
(ON)


Actual switches have limitations

- maximum current
- maximum voltage
- mechanical actuation (pressure, force)
- operating cycles

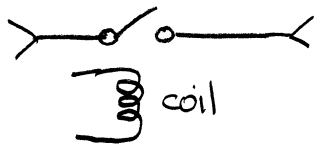
controlled switches computer controlled switches




RELAY

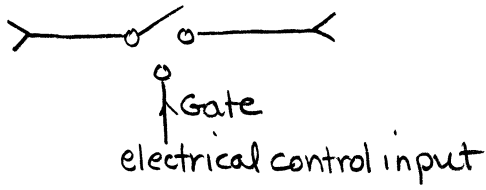


ANALOG SWITCH

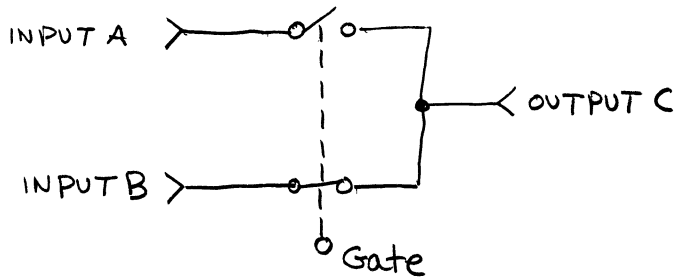

MULTIPLEXER (MUX)

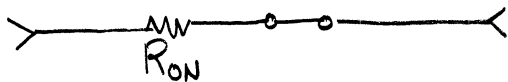


switch model with finite ON resistance

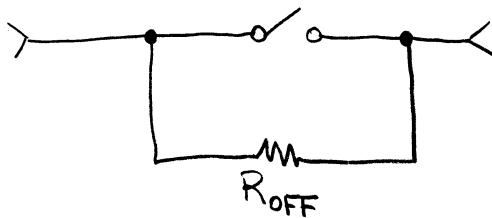

switch model with finite OFF resistance


IDEAL SOURCES

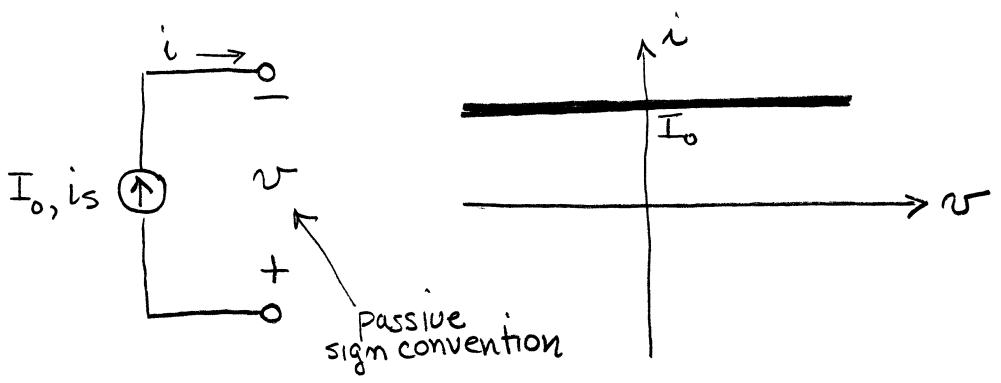ideal current source $i(t) = i_s$; $v = \text{any value}$




i_s time varying current source
 I_0 constant current source


ideal voltage source

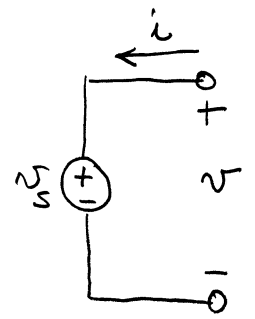

time-varying voltage source

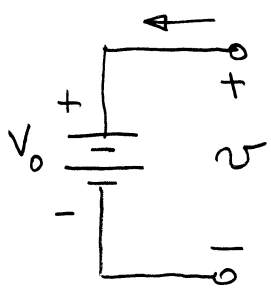


constant voltage source

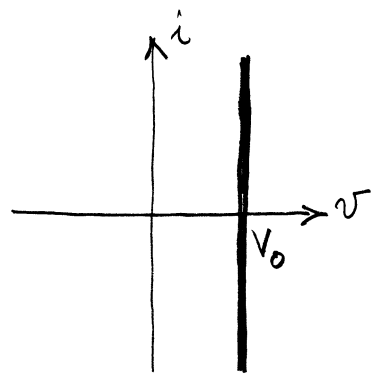

output from a time varying source is called a forcing function or a driving function

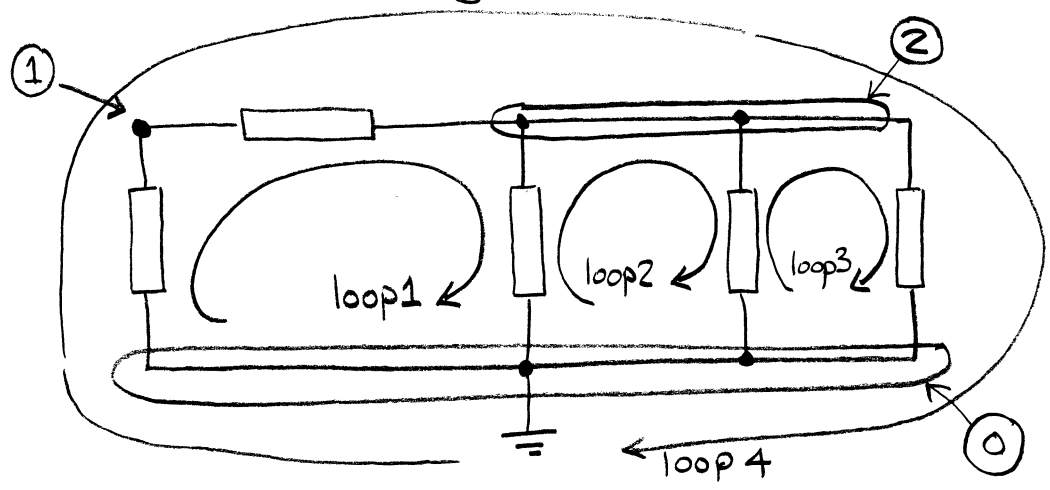2-2 Connection constraints

- circuit - interconnection of electrical devices
- node - electrical junction of two or more devices
- loop - closed path formed by tracing through an ordered sequence of nodes without passing through any node more than once



This circuit has three nodes. We always number the ground node \emptyset .

There are many possible loops. Four are shown.

symbols

