

V_0 is the known
 R_1, R_2 also given

I. Do element equations

$v_A = V_0$	given source	} we will shortly start assuming these.	(1)
$v_1 = i_1 R_1$	Ohm's Law		(2)
$v_2 = i_2 R_2$	Ohm's Law		(3)

II. Do connection equations: KCL @ each node, KVL for loop.

KCL @ A: $\sum i = 0 \quad -i_A - i_1 = 0$ (4)

KCL @ B: $\sum i = 0 \quad i_1 - i_2 = 0$ (5)

KVL: $\sum v = 0 \quad -v_A + v_1 + v_2 = 0$ (6)

III. Substitute element equations into connection equations

Using (6) $-v_A + v_1 + v_2 = 0$

$$-(V_0) + (i_1 R_1) + (i_2 R_2) = 0$$

↑
↑
↑
 from (1) from (2) from (3)


Now use (5) to reduce this to one unknown

$$-V_0 + i_1 R_1 + i_1 R_2 = 0$$

$$i_1 = \frac{V_0}{R_1 + R_2}$$

Given V_0, R_1, R_2 all variables can now be found.

Exercise 2-6

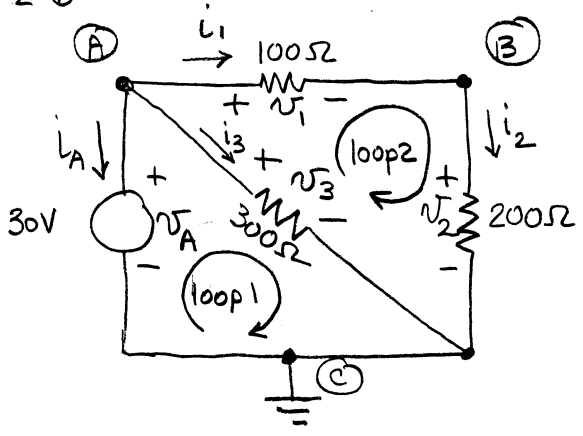

Given: 30V, 100Ω, 200Ω, 300Ω

(a) Write the complete set of element equations.

$$v_A = 30 \tag{1}$$

$$v_1 = 100 i_1 \tag{2}$$

$$v_2 = 200 i_2 \tag{3}$$

$$v_3 = 300 i_3 \tag{4}$$

(b) Write the complete set of connection equations

It is two nodes and two loops.

$$\text{KCL@ node A} \quad \sum_{\text{tm}} i = 0 \quad -i_A - i_1 = 0 \tag{5}$$

$$\text{KCL@ node B} \quad \sum_{\text{tm}} i = 0 \quad +i_1 - i_2 = 0 \tag{6}$$

$$\text{KVL@ loop 1} \quad \sum_{\text{Q}} v = 0 \quad -v_A + v_3 = 0 \tag{7}$$

$$\text{KVL@ loop 2} \quad \sum_{\text{Q}} v = 0 \quad -v_3 + v_1 + v_2 = 0 \tag{8}$$

(c) Solve these equations.

Substitute everything into (8)

$$-(v_A) + (100 i_1) + (200 i_2) = 0$$

\uparrow \uparrow \uparrow
 from (7) from (2) from (3)

$$-30 + 100 i_1 + 200 i_2 = 0$$

$$\text{From (6)} \quad i_1 = i_2 \Rightarrow -30 + 100 i_1 + 200 i_1 = 0$$


$$\therefore i_1 = \frac{30}{100 + 200} = \frac{30}{300} = 0.1 \text{ A} = 100 \text{ mA}$$

All other variables can now be solved for.


How do you assign reference marks?

- optional {
- ① Draw currents from + to - nodes of voltage sources or aligned with current sources if possible.
 - ② Align element currents with loop currents.
- REQUIRED
- ③ Follow passive sign convention
 - ④ When in doubt just do ③

Consider

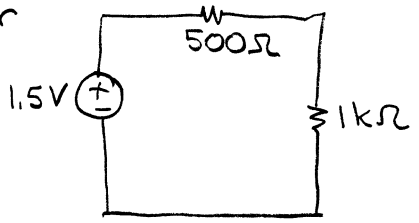


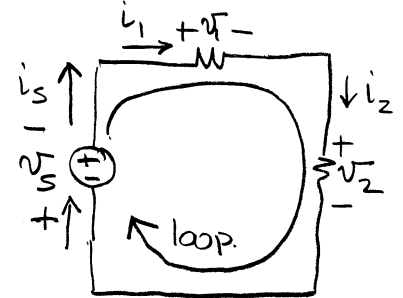Draw loop current from + to -. Follow with passive sign convention for elements.



Note source current was aligned with that of loop. This requires v_s to be in opposite direction to given polarity.

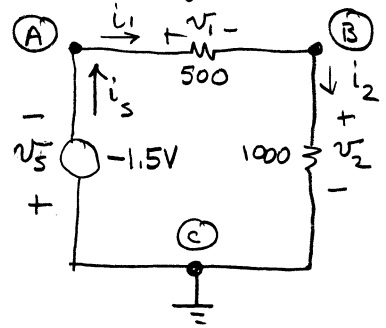Finalize by assigning nodes and reference (ground).



This can now be solved.

$$\left. \begin{aligned} v_s &= -1.5 \\ v_1 &= 500 i_1 \\ v_2 &= 1000 i_2 \end{aligned} \right\} \text{element equations}$$

connection equations

KCL @ A $\sum_{+m} i = 0 \quad + i_s - i_1 = 0$

KCL @ B $\sum_{+m} i = 0 \quad + i_1 - i_2 = 0$

KVL $\sum_{\square} v = 0 \quad + v_s + v_1 + v_2 = 0$


EQUIVALENT CIRCUITS

As circuits get more complex we want to replace parts of the circuit with equivalent but simpler circuits

Circuits are equivalent if they have the same i-v characteristics at a specified pair of terminals.

Equivalent Resistances
Source Transformations

Equivalent resistance (series)

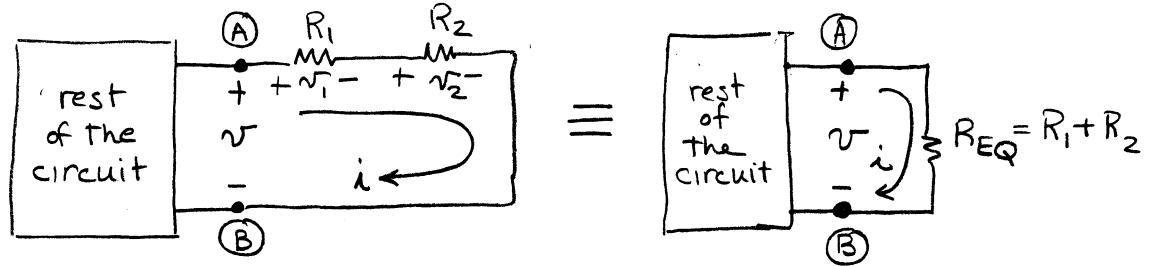

KVL from (A) to (B)

$$\sum v_i \quad -v + v_1 + v_2 = 0$$

or

$$v = v_1 + v_2$$

but $i_1 = i_2 = i$

$$v = i_1 R_1 + i_2 R_2$$

$$v = i R_1 + i R_2$$


$$v = i (R_1 + R_2)$$

For this circuit we simply use Ohm's Law

$$v = i R_{EQ}$$

These are identical if $R_{EQ} = R_1 + R_2$

Equivalent resistance (parallel)

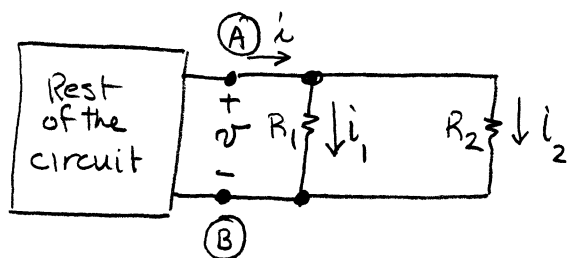

$$\text{KCL @ upper node } \sum_{+m} i = 0 \quad +i - i_1 - i_2 = 0$$


$$i = i_1 + i_2$$

$$\text{using Ohm's Law} \\ i = \frac{V}{R}$$

$$i = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

but $V = V_1 = V_2$ since these are in parallel
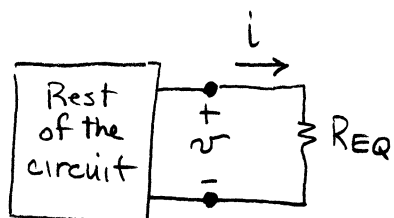
$$i = \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$



For this equivalent circuit

$$i = \frac{V}{R_{EQ}}$$

These circuits will be equivalent if $\frac{1}{R_{EQ}} = \frac{1}{R_1} + \frac{1}{R_2}$

This can be put in a more common form by simply inverting

$$R_{EQ} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$