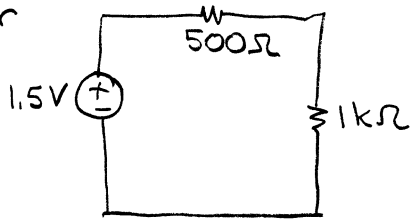



How do you assign reference marks?

- optional {
- ① Draw currents from + to - nodes of voltage sources or aligned with current sources if possible.
 - ② Align element currents with loop currents.
- REQUIRED
- ③ Follow passive sign convention
 - ④ When in doubt just do ③

Consider




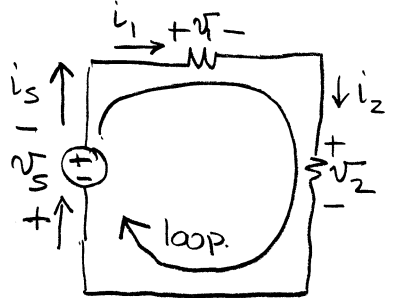Draw loop current from + to -. Follow with passive sign convention for elements.



Note source current was aligned with that of loop. This requires v_s to be in opposite direction to given polarity.

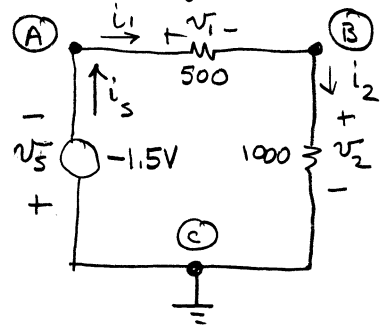Finalize by assigning nodes and reference (ground).



This can now be solved.

$$\left. \begin{aligned} v_s &= -1.5 \\ v_1 &= 500 i_1 \\ v_2 &= 1000 i_2 \end{aligned} \right\} \text{element equations}$$

connection equations

KCL @ A $\sum_{+m} i = 0 \quad + i_s - i_1 = 0$

KCL @ B $\sum_{+m} i = 0 \quad + i_1 - i_2 = 0$

KVL $\sum_{\square} v = 0 \quad + v_s + v_1 + v_2 = 0$


EQUIVALENT CIRCUITS

As circuits get more complex we want to replace parts of the circuit with equivalent but simpler circuits

Circuits are equivalent if they have the same i-v characteristics at a specified pair of terminals.

Equivalent Resistances
Source Transformations

Equivalent resistance (series)

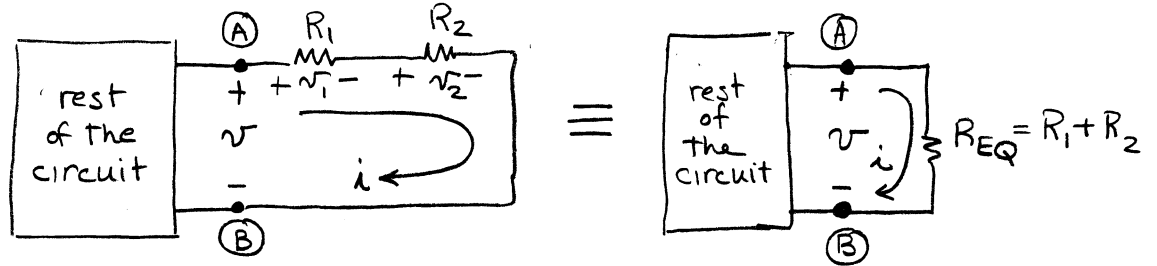

KVL from (A) to (B)

$$\sum_{\text{clockwise}} v_i \quad -v + v_1 + v_2 = 0$$

$$\text{or} \quad v = v_1 + v_2$$

but $i_1 = i_2 = i$

$$v = i_1 R_1 + i_2 R_2$$

$$v = i R_1 + i R_2$$


$$v = i (R_1 + R_2)$$

For this circuit we simply use Ohm's Law

$$v = i R_{EQ}$$

These are identical if $R_{EQ} = R_1 + R_2$

Equivalent resistance (parallel)

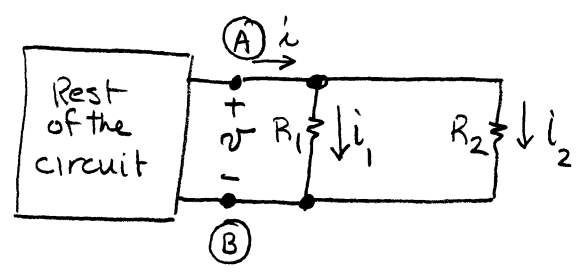


KCL @ upper node $\sum_{+m} i = 0$ $+i - i_1 - i_2 = 0$
 $i = i_1 + i_2$

using Ohm's Law $i = \frac{v}{R}$ $i = \frac{v_1}{R_1} + \frac{v_2}{R_2}$

but $v = v_1 = v_2$ since these are in parallel
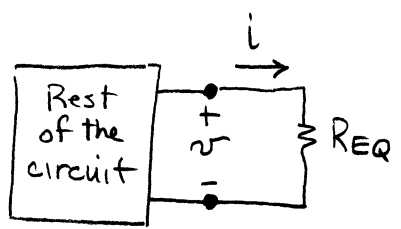
$$i = \frac{v}{R_1} + \frac{v}{R_2} = v \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$



For this equivalent circuit


$$i = \frac{v}{R_{EQ}}$$

These circuits will be equivalent if $\frac{1}{R_{EQ}} = \frac{1}{R_1} + \frac{1}{R_2}$



This can be put in a more common form by simply inverting

$$R_{EQ} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$


Example: between two terminals

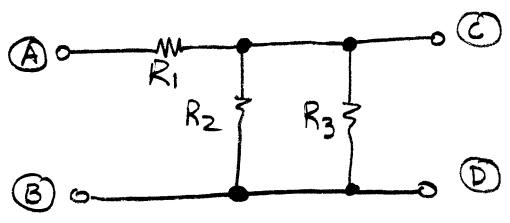

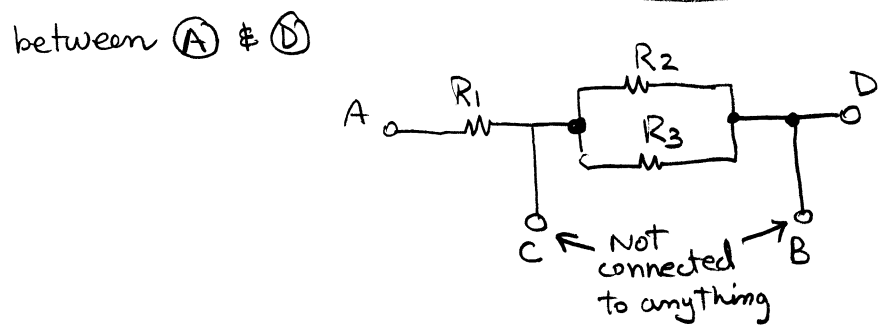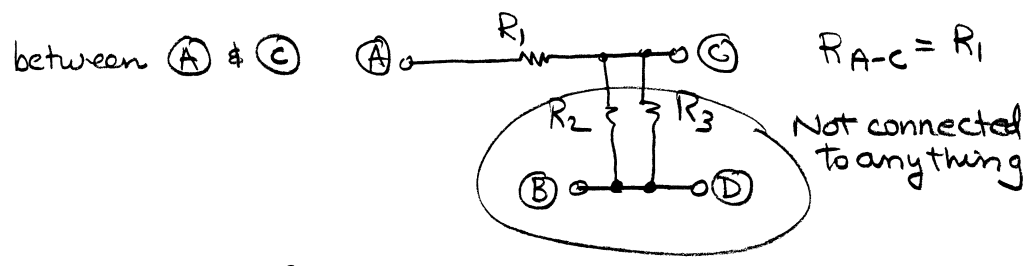We can derive equivalent resistances between any two pairs of terminals - assuming nothing is connected to the others




This is two equivalent resistances

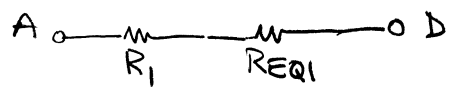


$$R_{EQ1} = \frac{R_2 R_3}{R_2 + R_3}$$

$$R_{EQ1} = R_2 \parallel R_3$$

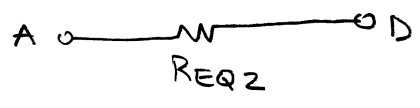


$$R_{EQ2} = R_1 + R_{EQ1}$$

EQUIVALENT SOURCES

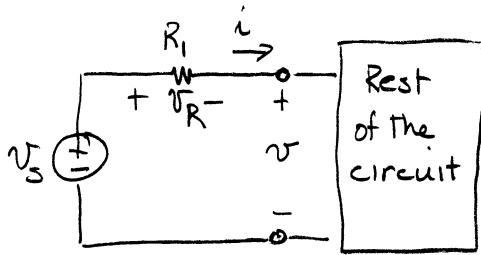

Circuit A

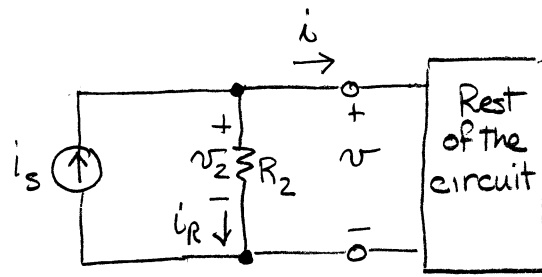

Circuit B

Circuit A and circuit B will be indistinguishable if their $i-v$ characteristics are the same.

Use KVL $\sum v = 0$

$$-v_s + v_R + v = 0$$

Use Ohm's Law

$$v_R = i R_1$$

Combine and rearrange

$$-v_s + i R_1 + v = 0$$

$$i R_1 = -v + v_s$$

$$i = -\frac{v}{R_1} + \frac{v_s}{R_1}$$

Use KCL $\sum i = 0$

$$+i_s - i_R - i = 0$$

Use Ohm's Law

$$i_R = \frac{v}{R_2} = \frac{v}{R_2}$$

$$i = -i_R + i_s$$

$$i = -\frac{v}{R_2} + i_s$$

these will be identical if $R_1 = R_2 = R$
and $i_s = \frac{v_s}{R_1}$

