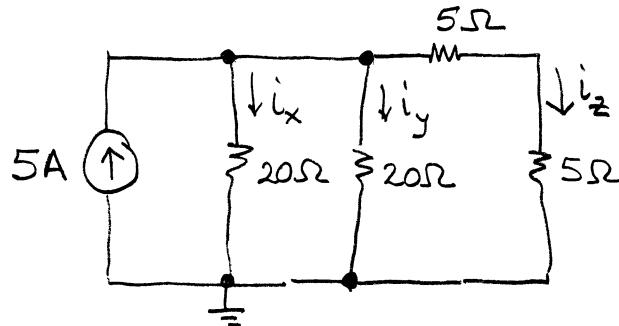
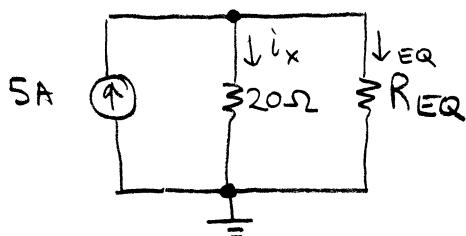
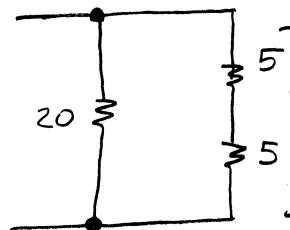


Example 2-18


Find the current i_x .

Reduce this circuit to

The problem now is to calculate R_{EQ} for

These two are in series and can simply be added together.

$$R'_{EQ} = 5 + 5 = 10\Omega$$

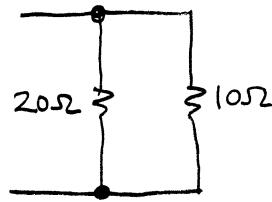

This is now a parallel circuit. The equivalent resistance is given by

$$\frac{1}{R_{EQ}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\text{or } R_{EQ} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(20)(10)}{20 + 10}$$

$$R_{EQ} = 6\frac{2}{3}\Omega$$

Now use a current divider to find i_x

$$i_x = \frac{R_{EQ}}{20 + R_{EQ}} \cdot 5A = \frac{6.67}{20 + 6.67} (5A) = 1.25 \text{ Amperes.}$$

Exercise 2-12

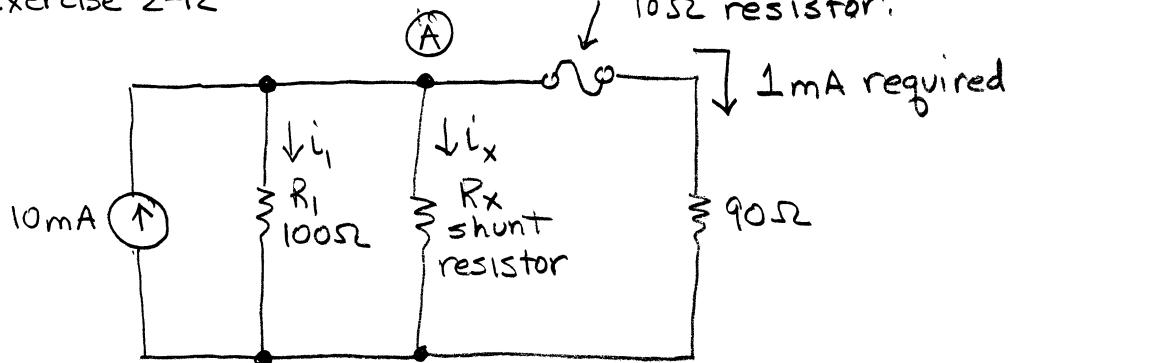

② You protect the device with a 1.5mA fuse which looks like a 10Ω resistor.

- ③ Calculate R_x
so that only 1mA goes to the device.

This is a current division problem.

The fuse plus 90Ω resistor are in series and can be replaced by a $R_{EQ} = R_1 + R_2 = 10 + 90 = 100\Omega$

Since there is a 1mA current through R_{EQ} the voltage across R_{EQ} is $V_A = i R_{EQ} = (1 \times 10^{-3})(100) = 0.1$ volts.

The same 0.1 volts appears across R_1 and R_x . The current thru R_1 is then

$$i_1 = \frac{V_A}{R_1} = \frac{0.1 \text{ volts}}{100} = 1 \text{ mA}$$

Applying KCL @ A gives

$$\begin{aligned} \sum i = 0 & \quad +10 \text{mA} - 1 \text{mA} - i_x - 1 \text{mA} = 0 \\ & \quad +i_m \\ i_x & = 8 \text{mA} \end{aligned}$$


This allows us to solve for R_x

$$R_x = \frac{v}{i} = \frac{0.1 \text{ volts}}{8 \times 10^{-3} \text{ amps}} = 12.5 \text{ ohms.}$$

2-6 Circuit Reduction

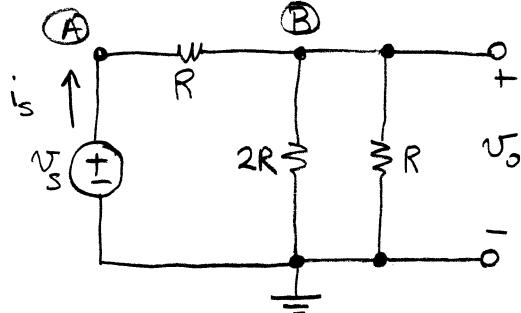Example 2-20

Use series and parallel equivalence to find the output voltage and the input current in the circuit shown below.




Solution approach

a. combine parallel resistors R and 2R


b. calculate V_o using voltage divider

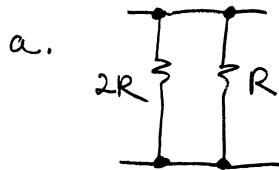c. combine all resistances to determine input current i_s



From (2-22)

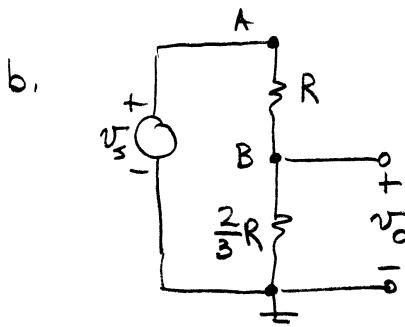
$$R_{EQ} = 2R \parallel R = \frac{(2R)(R)}{2R+R} = \frac{2R^2}{3R} = \frac{2}{3}R$$



From (2-31) $V_K = \frac{R_K}{R_{EQ}} V_{TOTAL}$

$$V_o = \frac{\frac{2}{3}R}{R + \frac{2}{3}R} V_s = \frac{\frac{2}{3}R}{\frac{5}{3}R} V_s = \frac{2}{5} V_s$$

resistors
in series add

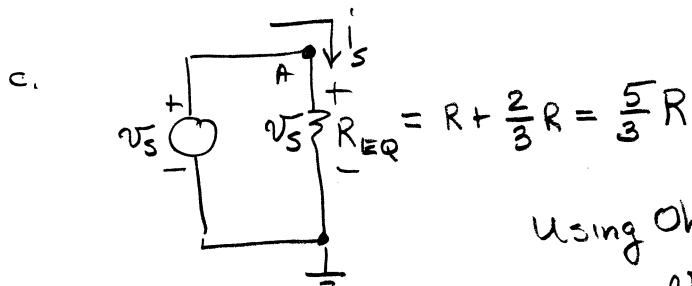


Using Ohm's Law

$$i_s = \frac{V_s}{R_{EQ}} = \frac{V_s}{\frac{5}{3}R} = \frac{3}{5} \frac{V_s}{R}$$

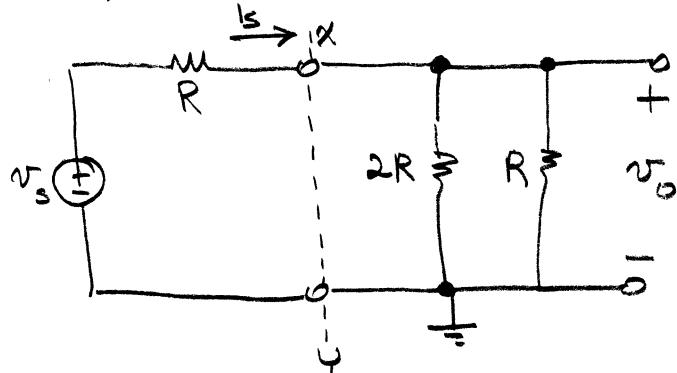Example 2-21

Use source transformations to find the output voltage v_o and the input current i_s in the circuit shown below.




a. apply a source transformation to $v_s - R$ left of X-Y

b. combine the two parallel resistors

c. use current division to find i_s

d. calculate v_o

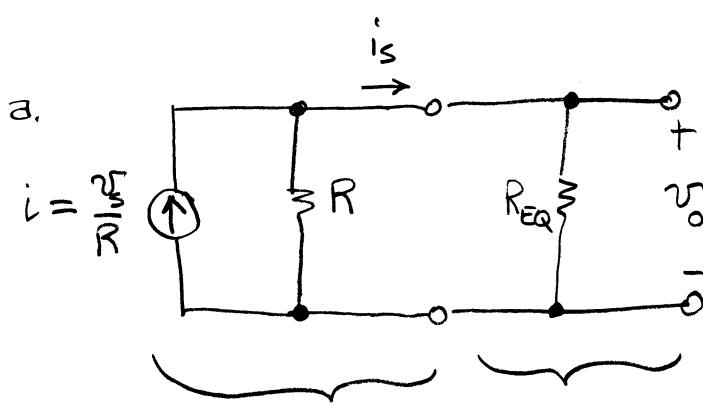

a.

b.

$$R_{EQ} = \frac{(2R)(R)}{2R+R} = \frac{2R^2}{3R} = \frac{2}{3}R.$$

c. Using current divider


$$i_s = \frac{R}{R+R_{EQ}} \quad i = \frac{R}{R+\frac{2}{3}R} \quad \frac{v_s}{R} = \frac{3}{5} \frac{v_s}{R}$$

d. calculate v_o using Ohm's Law

$$v_o = i_s R_{EQ} = \left(\frac{3}{5} \frac{v_s}{R}\right) \left(\frac{2}{3} R\right) = \frac{2}{5} v_s$$

Example 2-22

Find v_x in the circuit below.

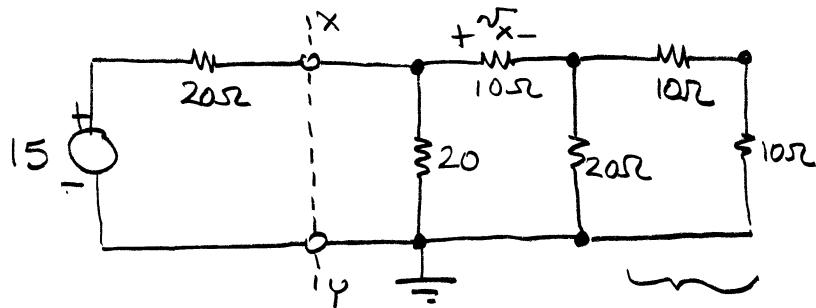


a. do source transformation

b. combine resistors

$$i = \frac{15}{20}$$

$$i = \frac{3}{4} \text{ A}$$

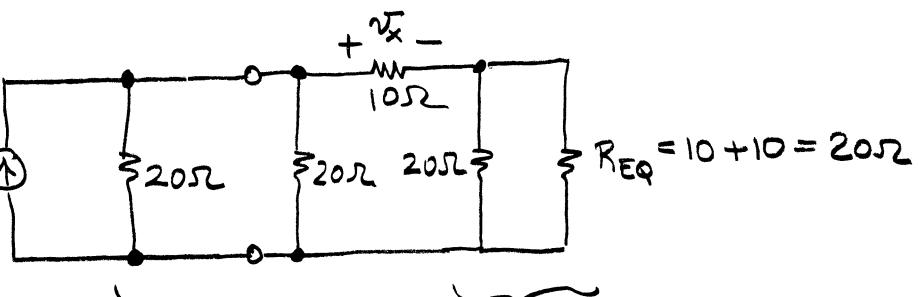


c. combine resistors

$$R_{EQ1} = \frac{(20)(20)}{20 + 20} = 10$$

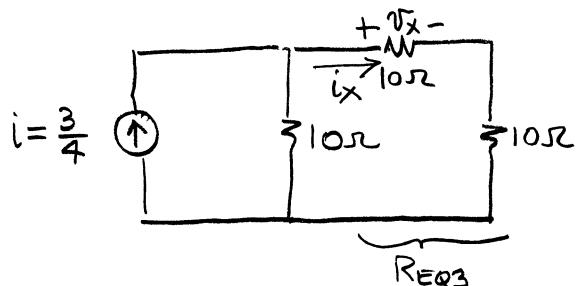
d. combine resistors

$$R_{EQ2} = \frac{(20)(20)}{20 + 20} = 10$$



$$c.2 \quad R_{EQ3} = 10 + 10 = 20\Omega$$

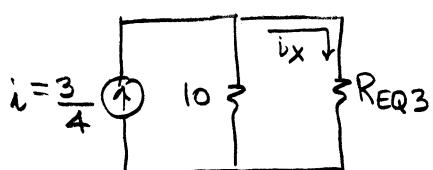- e. several ways to finish
 e.1 use source transformation and voltage divider, OR
 e.2 combine two 10Ω resistors in series and use a current divider followed by Ohm's Law



using current divider

$$i_x = \frac{10}{10 + R_{EQ3}} i$$

$$i_x = \frac{10}{10 + 20} \left(\frac{3}{4}\right) = \frac{1}{3} \cdot \frac{3}{4} = \frac{1}{4}$$

using Ohm's Law $v_x = i_x(10\Omega) = \frac{1}{4}(10) = 2.5 \text{ Volts}$