
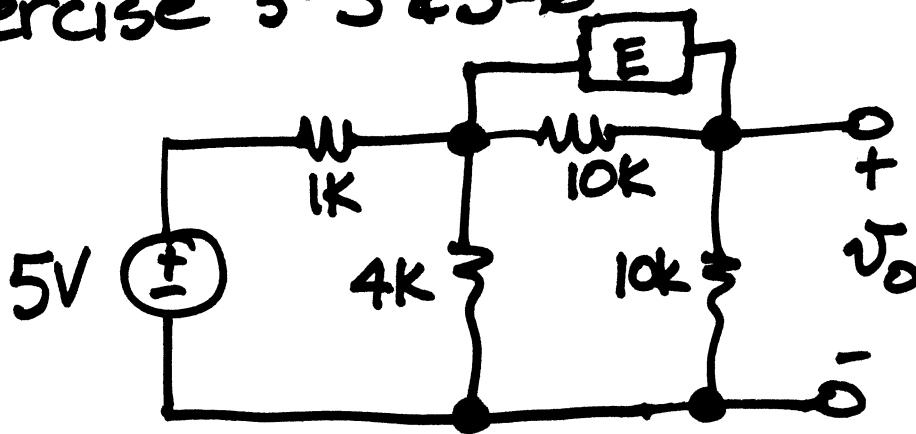





# NODE VOLTAGE

Exercise 3-5 & 3-6

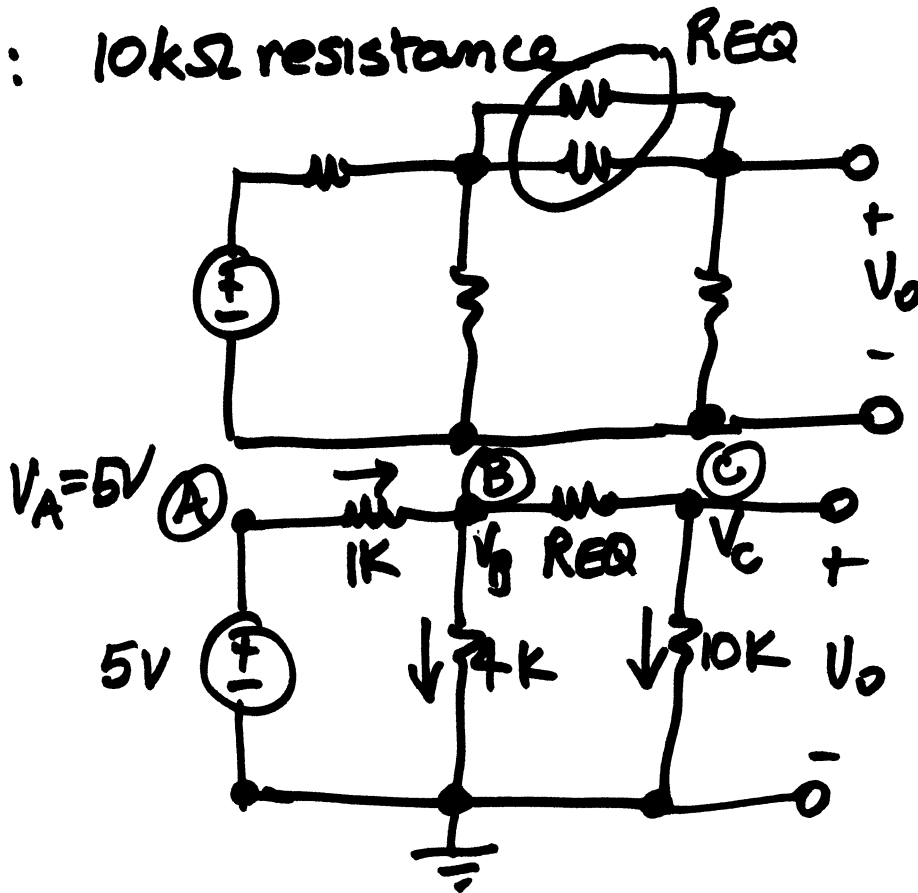



E:  $10k\Omega$  resistance  $R_{EQ}$



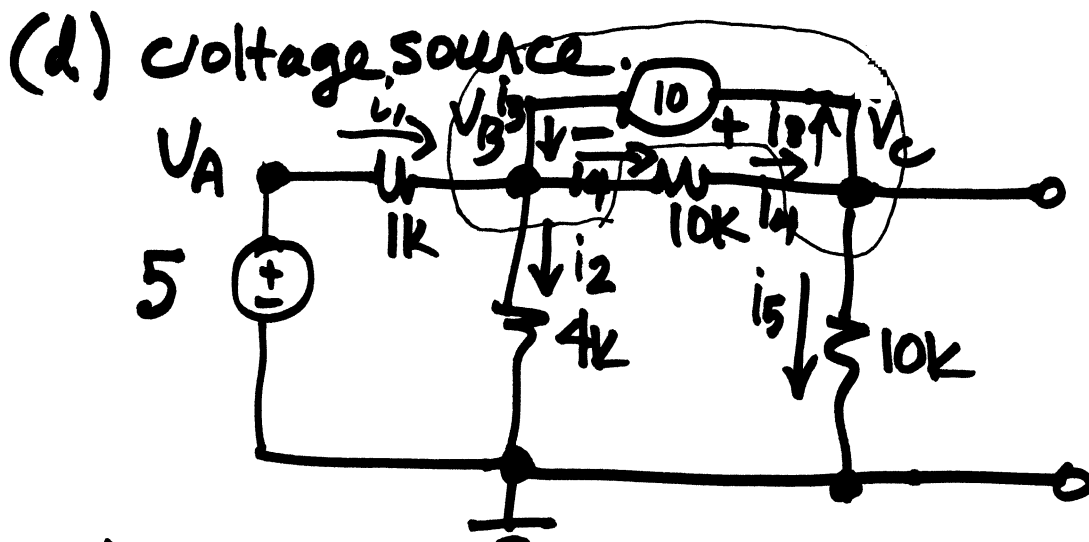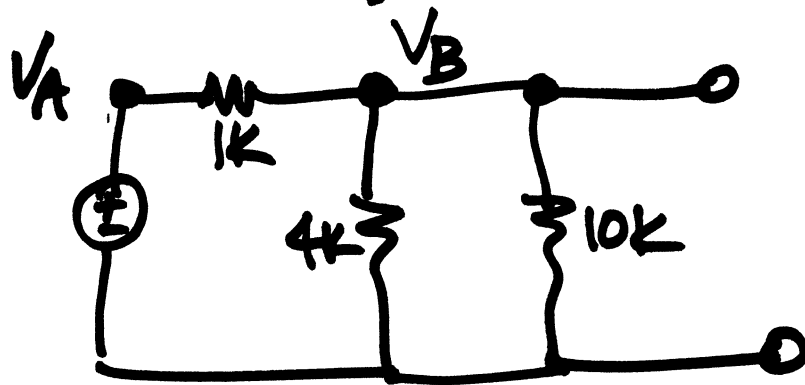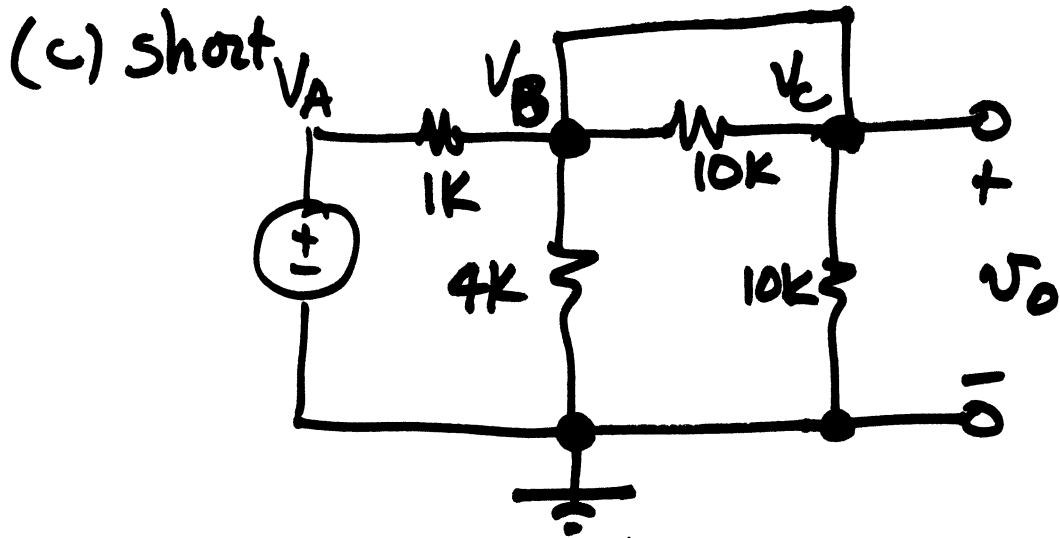

$$V_C - V_B = +10 \quad \text{Supernode}$$
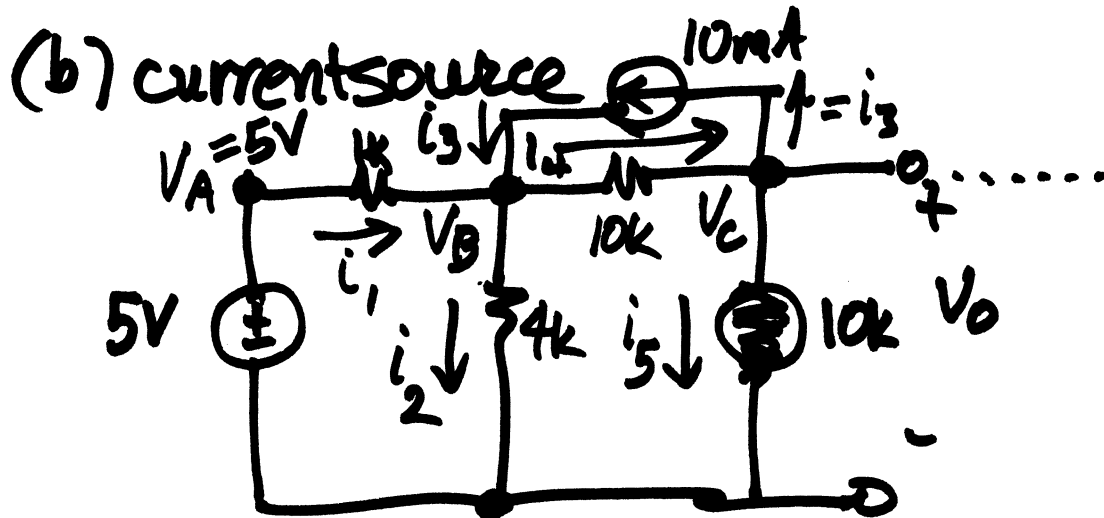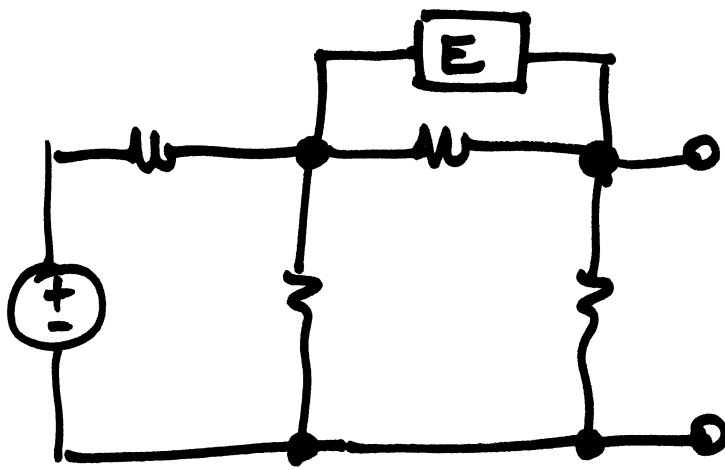
$$\text{supernode } \sum_{+m} i = 0 \quad +i_1 - i_2 - i_4 + i_4 - i_5 = 0$$




$$\text{KCL @ B } \sum i_{\text{in}} = +i_1 - i_2 + i_3 - i_4 = 0$$

$$\left( \frac{5 - V_B}{1 \times 10^3} \right) - \left( \frac{V_B - 0}{4 \times 10^3} \right) + (10 \times 10^{-3}) - \left( \frac{V_B - V_C}{10 \times 10^3} \right) = 0$$


$$\text{KCL @ C } \sum i_{\text{in}} = -i_3 + i_4 - i_5 = 0$$

$$-(10 \times 10^{-3}) + \left( \frac{V_B - V_C}{10 \times 10^3} \right) - \left( \frac{V_C - 0}{10 \times 10^3} \right) = 0$$


Exercise 3-5

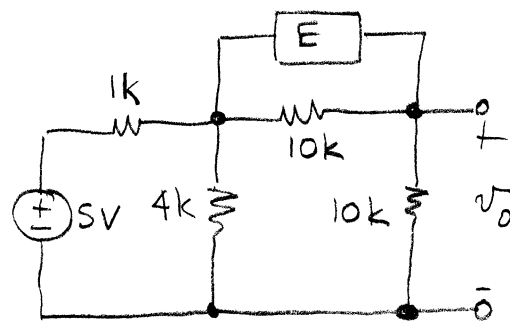

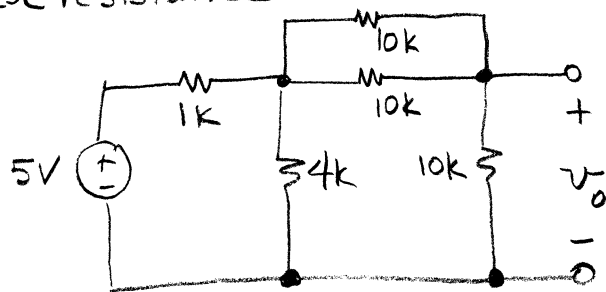Find  $v_o$  when the element E is  
 (a) a  $10k\Omega$  resistance.



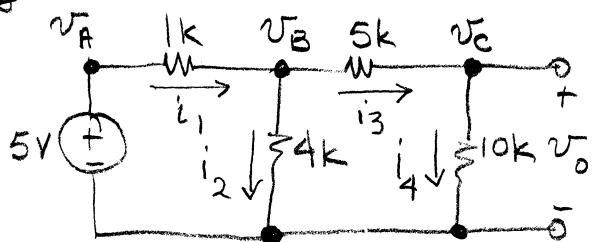Simply combine the two parallel resistors  $R_{EQ} = \frac{(10k)(10k)}{10k+10k} = 5k$



label nodes. By inspection  $v_A = 5$   $v_C = v_o$   
 $\Rightarrow$  We only have two unknowns  $v_B$  and  $v_C$  and only need two equations.

$$\sum_{\text{tin}} i @ B \quad +i_1 - i_2 - i_3 = 0$$

$$\sum_{\text{tin}} i @ C \quad +i_3 - i_4 = 0$$

No current to output terminals!

Currents are  $i_1 = \frac{v_A - v_B}{1k} = \frac{5 - v_B}{1k}$

$$i_2 = \frac{v_B - 0}{4k} = \frac{v_B}{4k}$$

$$i_3 = \frac{v_B - v_C}{5k}$$

$$i_4 = \frac{v_C - 0}{10k} = \frac{v_C}{10k}$$

Substituting

$$\frac{5 - v_B}{1k} - \frac{v_B}{4k} - \frac{v_B - v_C}{5k} = 0$$

$$\left(\frac{v_B - v_C}{5k}\right) - \left(\frac{v_C}{10k}\right) = 0$$

$$\left(\frac{1}{1k} + \frac{1}{4k} + \frac{1}{5k}\right) v_B - \frac{1}{5k} v_C = \frac{5}{1k}$$

$$\left(\frac{1}{5k}\right) v_B - \left(\frac{1}{5k} + \frac{1}{10k}\right) v_C = 0$$

$$(20 + 5 + 4) v_B - 4 v_C = 100$$

$$2 v_B - (2 + 1) v_C = 0$$

$$29 v_B - 4 v_C = 100$$

$$2 v_B - 3 v_C = 0$$


$$29\left(\frac{3}{2} v_C\right) - 4 v_C = 100$$

$$87 v_C - 8 v_C = 200$$

$$79 v_C = 200$$

$$v_C = +2.53 \text{ volts.}$$

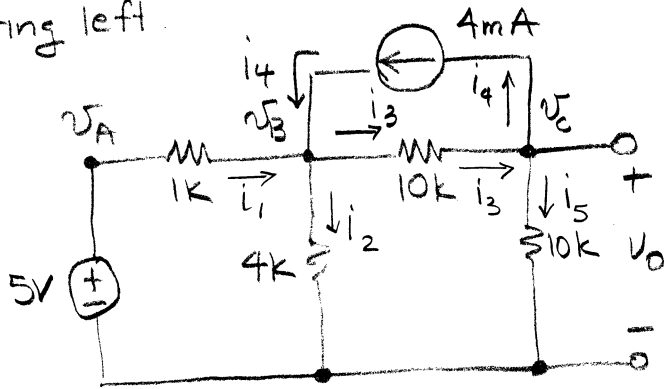(b) a 4mA independent current source with reference arrow pointing left.



by inspection  $v_A = 5 \text{ Volts}$

$$\sum i @ B \quad +i_1 - i_2 - i_3 + i_4 = 0$$

$$\sum i @ C \quad +i_3 - i_4 - i_5 = 0$$

currents are  $i_1 = \frac{v_A - v_B}{1k}$

$$i_2 = \frac{v_B - 0}{4k}$$

$$i_3 = \frac{v_B - v_C}{10k}$$

$$i_4 = 4 \text{ mA}$$

$$i_5 = \frac{v_C - 0}{10k}$$

Substituting and multiplying  $\left( \frac{v_A - v_B}{1k} - \frac{v_B}{4k} - \frac{v_B - v_C}{10k} + 4 \text{ mA} = 0 \right) \times 10 \times 10^3$

$$\left( \frac{v_B - v_C}{10k} - 4 \text{ mA} - \frac{v_C}{10k} = 0 \right) \times 10 \times 10^3$$

$$v_A = +5$$

$$50 - 10v_B - 2.5v_B - v_B + v_C + 40 = 0$$

$$v_B - v_C - 40 - v_C = 0$$

Rearranging

$$(-13.5v_B + v_C = -90) \times 2$$

$$v_B - 2v_C = +40$$

$$-27v_B + 2v_C = -180$$

$$v_B + 2v_C = +40$$

$$-26v_B = -140$$

$$v_B = +5.385$$

$$-13.5v_B + v_C = -90$$

$$-13.5(5.385) + v_C = -90$$


$$-72.70 + v_C = -90$$

$$v_C = -17.31 \text{ volts.}$$


$$\therefore v_o = -17.3 \text{ volts.}$$

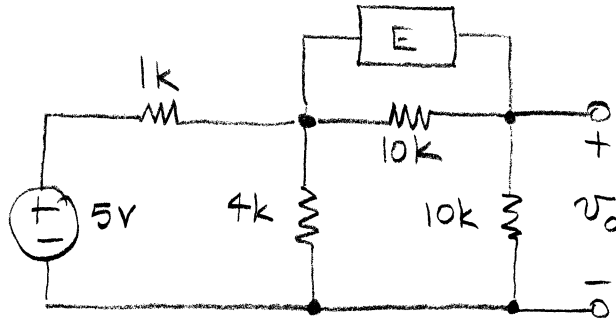Exercise 3-6

Find  $v_o$  in the circuit below when the element E is



(a) an open circuit

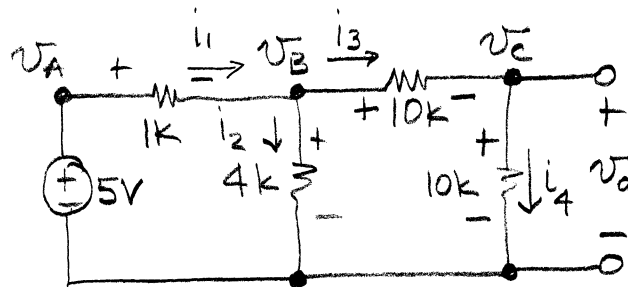

by inspection  $v_A = +5$  volts

$$\sum i @ B \quad +i_1 - i_2 - i_3 = 0$$

$$\sum i @ C \quad +i_3 - i_4 = 0$$

$$i_1 = \frac{v_A - v_B}{1k} = \frac{5 - v_B}{1k}$$

$$i_2 = \frac{v_B - 0}{4k}$$

$$i_3 = \frac{v_B - v_C}{10k}$$

$$i_4 = \frac{v_C - 0}{10k}$$

substituting

$$\frac{5 - v_B}{1k} - \frac{v_B}{4k} - \frac{v_B - v_C}{10k} = 0$$

$$\frac{v_B - v_C}{10k} - \frac{v_C}{10k} = 0$$



multiplying by  $10 \times 10^3$

$$50 - 10v_B - 2.5v_B - v_B + v_C = 0$$

$$v_B - v_C - v_C = 0$$

rearranging

$$-13.5v_B + v_C = -50$$

$$v_B - 2v_C = 0$$

multiplying by 2

$$-27v_B + 2v_C = -100$$

$$v_B - 2v_C = 0 \quad \textcircled{1}$$


adding together

$$-26v_B = -100$$

$$v_B = + 3.846 \text{ Volts.}$$

$$\text{From } \textcircled{1} \quad v_C = \frac{v_B}{2} = \frac{3.846}{2} = +1.923 \text{ volts}$$

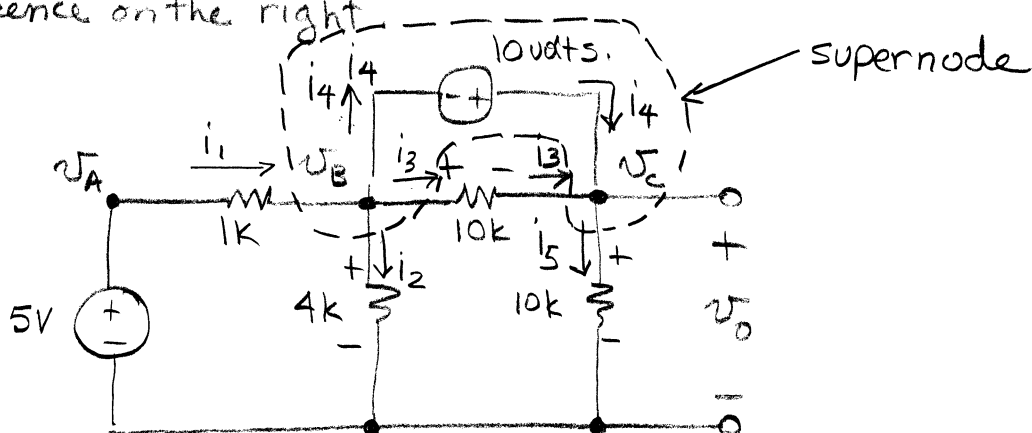(b) A 10-volt independent voltage source with the plus reference on the right



We have to use a supernode since we do not know  $i_4$ .

Define the super node shown above

$$\text{@ supernode } \sum i = 0 \quad +i_1 - i_2 - i_3 + i_3 - i_5 = 0$$

+in these cancel

$i_4$  does not appear since it is inside the supernode.

The other equation is simply that of the voltage source.

$$v_C - v_B = +10$$

$$i_1 = \frac{v_A - v_B}{1k} = \frac{5 - v_B}{1k}$$

$$i_2 = \frac{v_B - 0}{4k}$$

$$i_3 = \frac{v_B - v_C}{10k}$$

$$i_4 = ?$$

$$i_5 = \frac{v_C - 0}{10k}$$

Substituting:

$$\frac{5 - v_B}{1k} - \frac{v_B}{4k} - \frac{v_C}{10k} = 0$$

$$+ v_C - v_B = +10$$

Multiply top equation by  $10 \times 10^3$

$$50 - 10v_B - 2.5v_B - v_C = 0$$

$$v_C - v_B = 10$$

---

Rearranging

$$-12.5v_B - v_C = -50$$

$$-v_B + v_C = 10 \quad \text{①}$$

---

Adding

$$-13.5v_B = -40$$

$$v_B = +2.963 \text{ volts.}$$

substituting into ①:  $-2.963 + v_C = 10$

$$v_C = 10 + 2.963 = +12.963 \text{ volts}$$

$$v_o = v_C = +12.963 \text{ volts}$$