

Homework Prob 3-20 is duplicated.
Should have been 3-19
We will ~~stop~~ problem 3-20
not replace duplicate.

New Lab Kirchoff's Laws & Superposition

Lab 4

Kirchhoff's Laws and Superposition




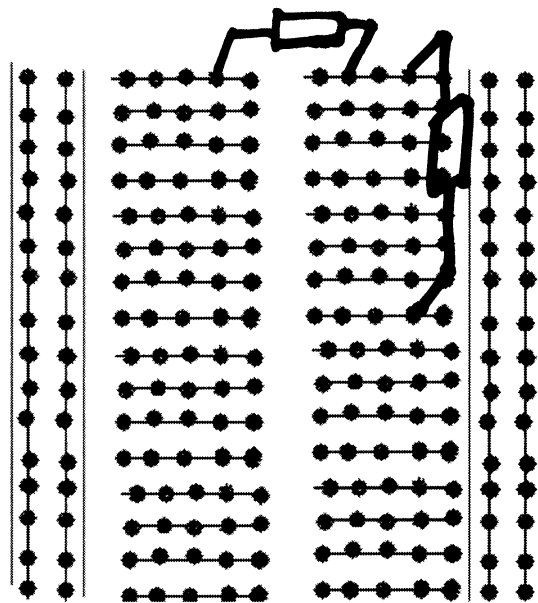
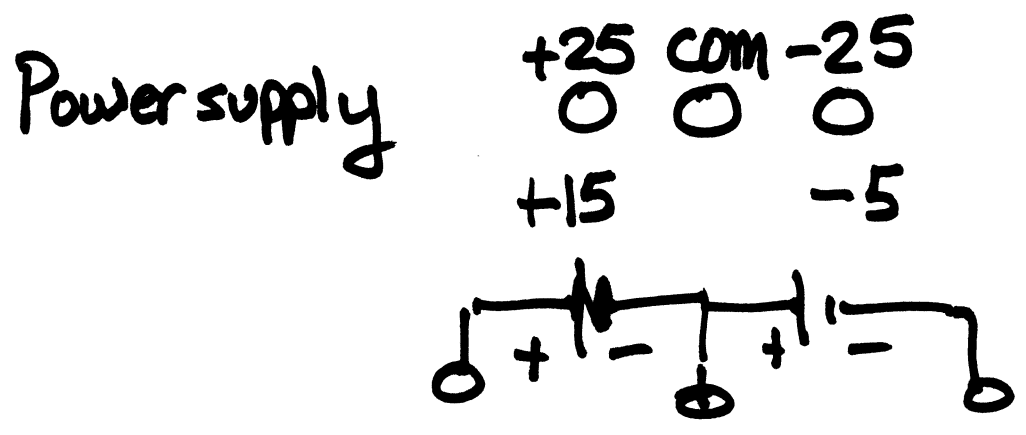


Diagram 1

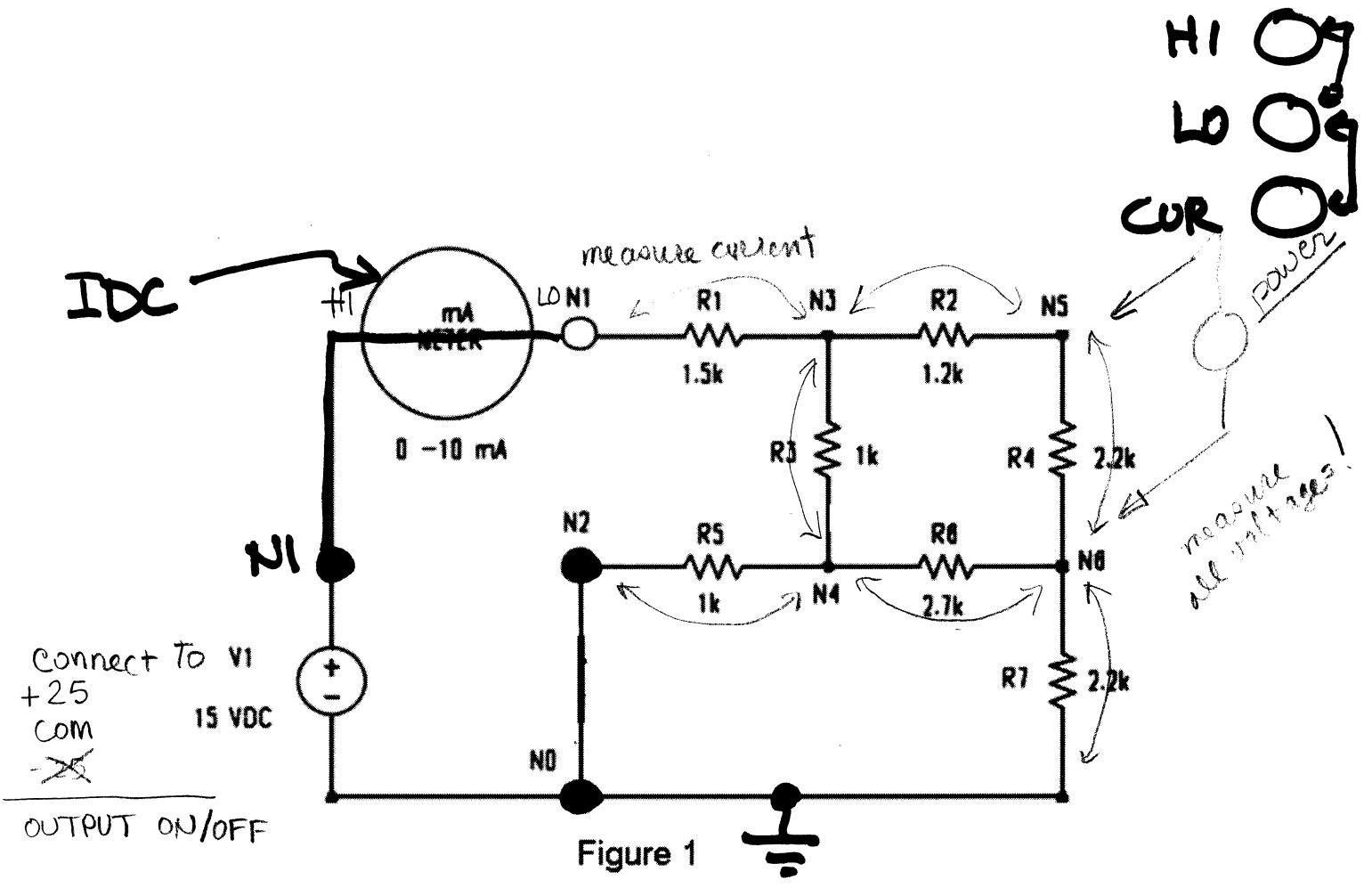

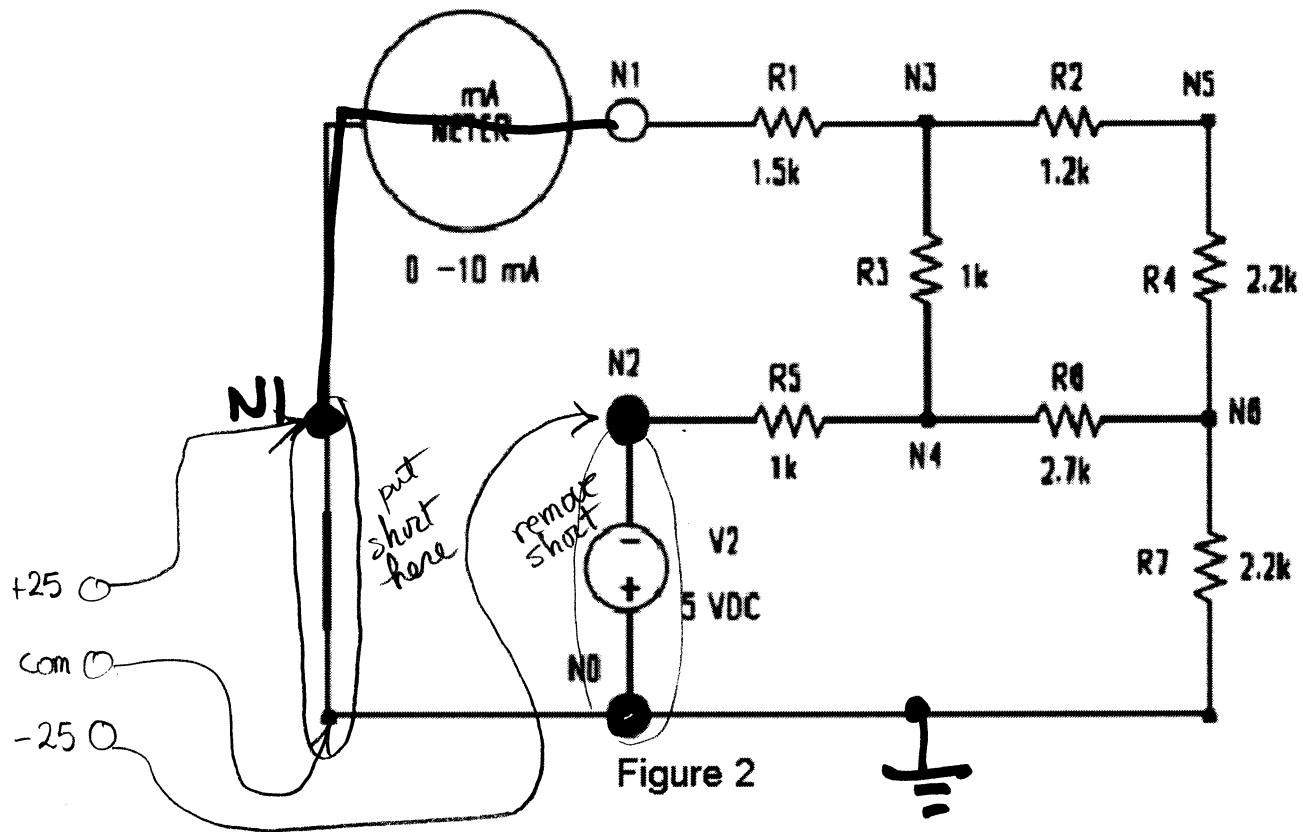


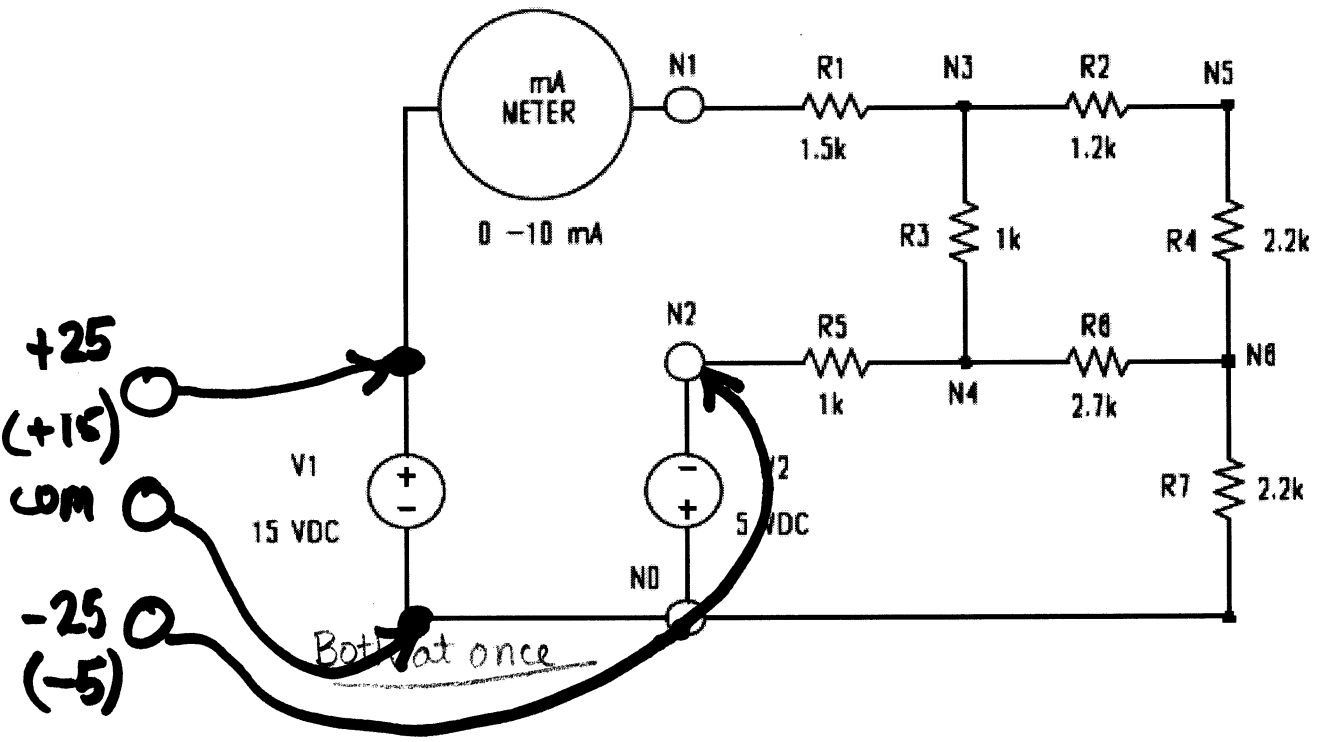


VERIFY SUPERPOSITION.

LOOP

MESH CURRENT

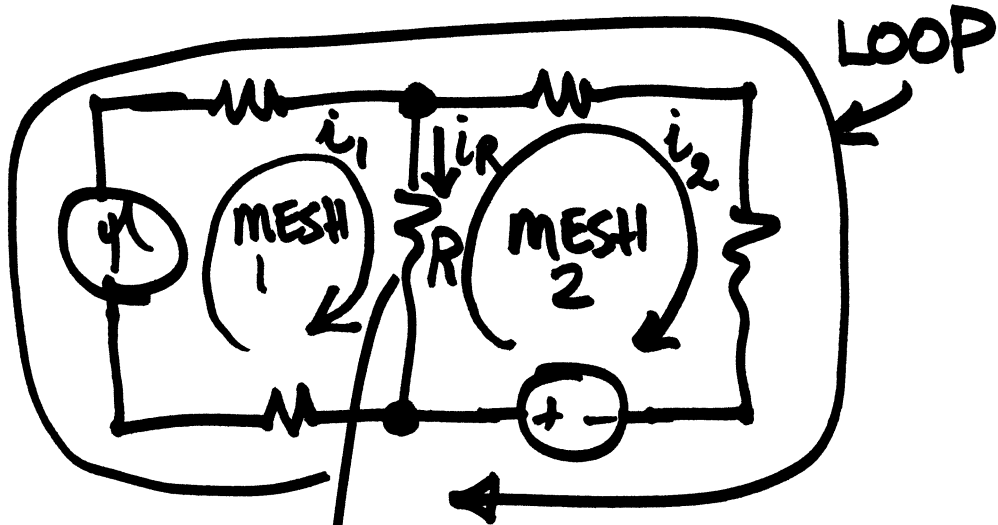


MESH CURRENT ANALYSIS

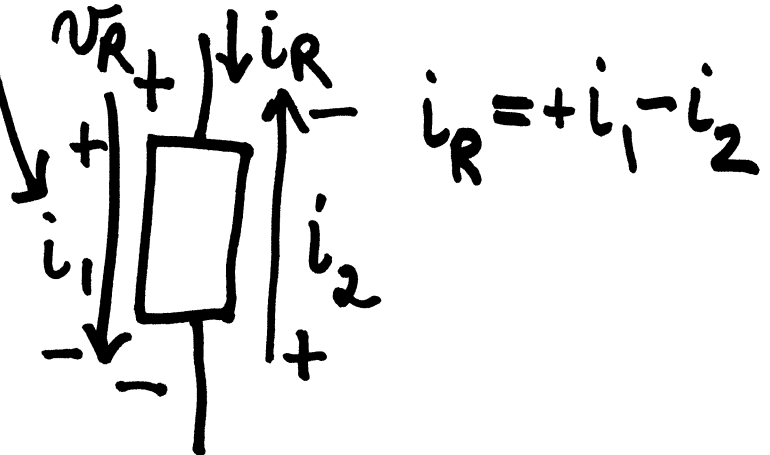

$$v_R = i_R R = +i_1 R - i_2 R$$

Figure 3-18 mesh current

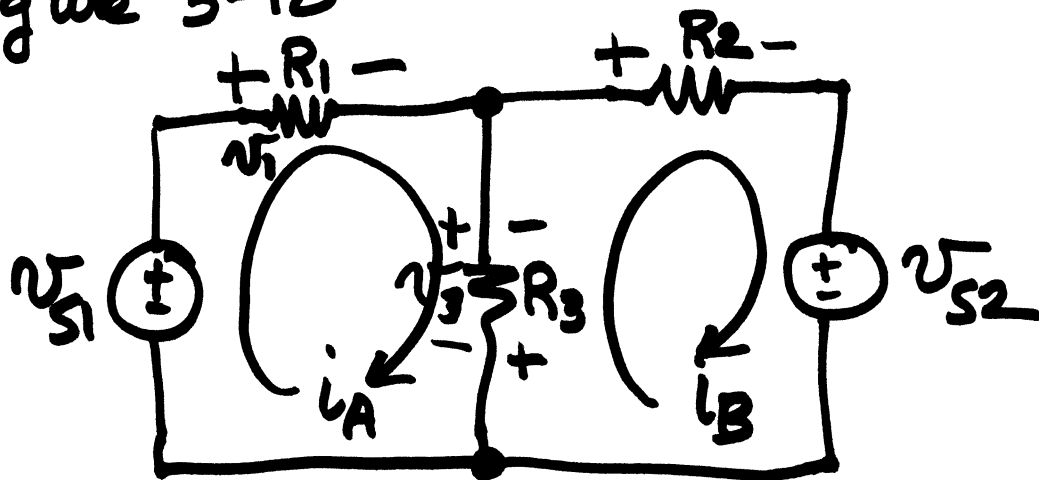

really KVL equations for each mesh

mesh A \curvearrowright
$$-v_{S1} + v_1 + v_3 = 0$$

put in element values
$$-v_{S1} + \underline{i_A R_1} + \underline{i_A R_3} - i_B R_3 = 0 \quad (1)$$

mesh B \curvearrowright
$$-v_3 + v_2 + v_{S2} = 0$$

$$\underline{i_B R_3} - \underline{i_A R_3} + \underline{i_B R_2} + v_{S2} = 0 \quad (2)$$


$$(R_3 + R_1) i_A - R_3 i_B = +v_{S1}$$

$$-R_3 i_A + (R_2 + R_3) i_B = -v_{S2}$$


Mesh current technique

- problems with current sources


1. source transformation

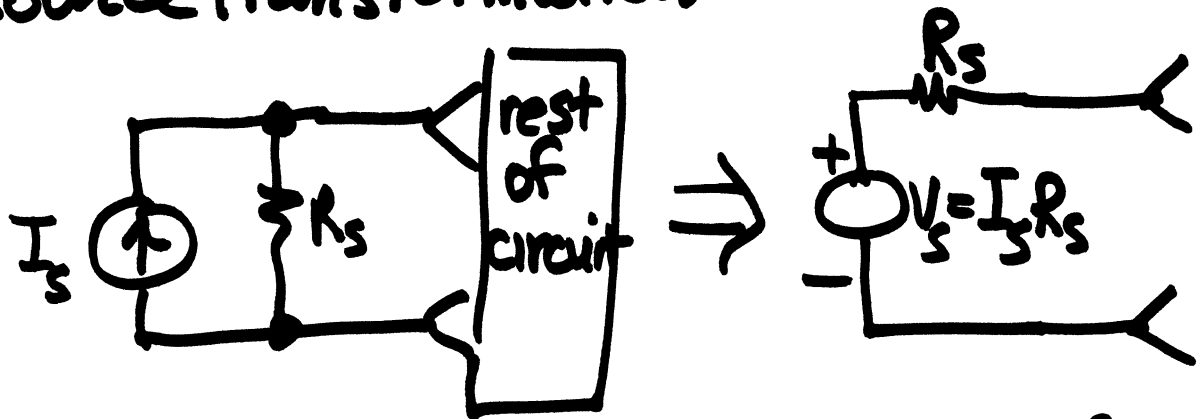

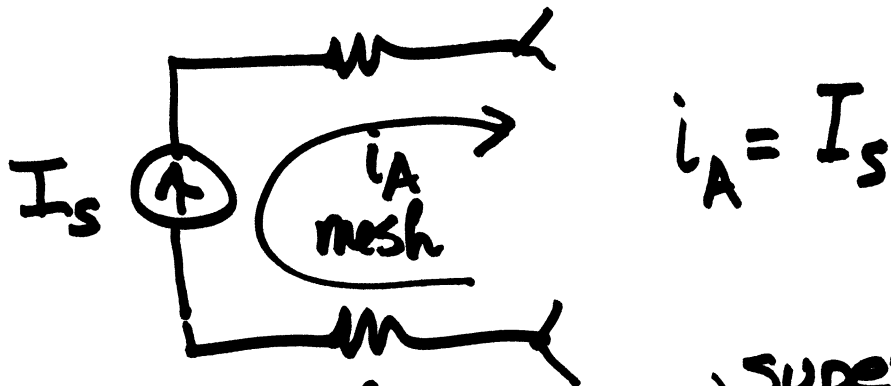2. current source in an outer mesh (single current mesh)




3. supermesh

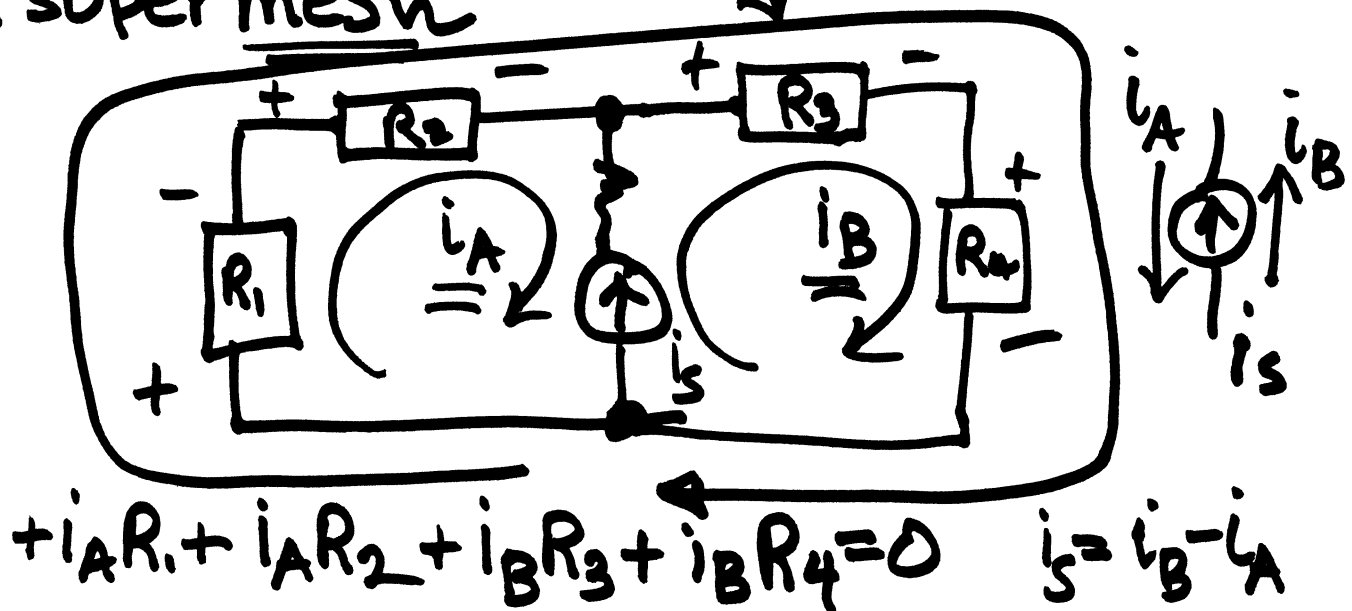


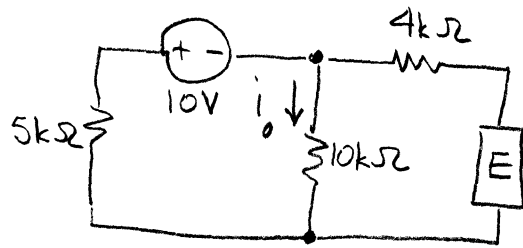Exercise 3-8

Use mesh analysis to find the current i_o in the circuit below when the element E is



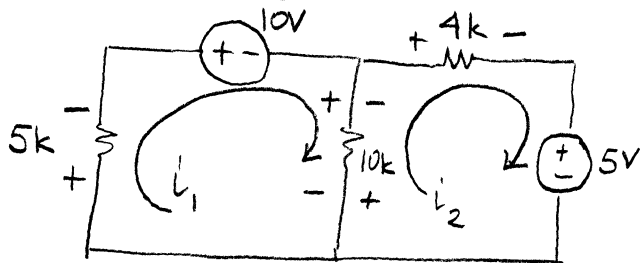(a) a 5Volt voltage source with the positive reference at the top.



$$\text{mesh 1 } \mathcal{C} \quad + 5k i_1 + 10 + 10k i_1 - 10k i_2 = 0$$

$$\text{mesh 2 } \mathcal{C} \quad + 10k i_2 - 10k i_1 + 4k i_2 + 5 = 0$$

$$\text{rearranging} \quad \begin{array}{r} +15k i_1 - 10k i_2 = -10 \times \frac{10^{-3}}{5} \\ -10k i_1 + 14k i_2 = -5 \times \frac{10^{-3}}{5} \end{array}$$

$$3i_1 - 2i_2 = -2 \times 10^{-3} \quad (1)$$

$$-2i_1 + 2.8i_2 = -1 \times 10^{-3} \quad (2)$$

multiply top equation by $\frac{2}{3}$

$$2i_1 - \frac{4}{3}i_2 = -\frac{4}{3} \times 10^{-3}$$

$$-2i_1 + \frac{14}{5}i_2 = -1 \times 10^{-3}$$

Add and solve for i_2

$$\left(-\frac{4}{3} + \frac{14}{5}\right) i_2 = \left(-\frac{4}{3} - 1\right) \times 10^{-3}$$

$$\frac{-20 + 42}{15} i_2 = \frac{-7}{3} \times 10^{-3}$$

$$\frac{22}{15} i_2 = -\frac{7}{3} \times 10^{-3}$$

$$i_2 = -\frac{7 \cdot 15}{3 \cdot 22} \times 10^{-3} = -1.591 \text{ mA}$$

using Eqn (1)


$$3i_1 - 2(-1.591 \text{ mA}) = -2 \text{ mA}$$

$$3i_1 + 3.182 \text{ mA} = -2 \text{ mA}$$

$$i_1 = \frac{-2 \text{ mA} - 3.182 \text{ mA}}{3}$$

$$i_o = i_1 - i_2 = \frac{(-2 - 3.182) \text{ mA}}{3} - (-1.591 \text{ mA}) = -0.136 \text{ mA}$$

(b) a $10\text{ k}\Omega$ resistor.

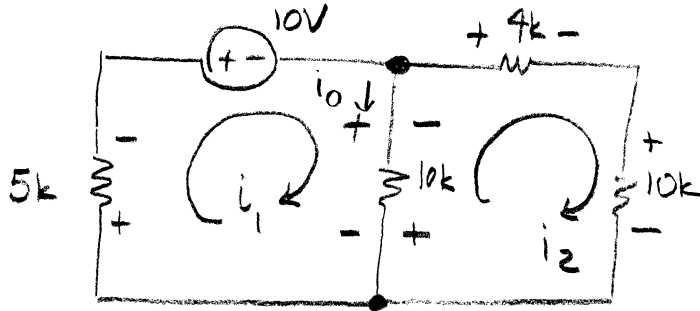

$$\text{mesh 1} \quad +5\text{k}i_1 + 10 + 10\text{k}i_1 - 10\text{k}i_2 = 0$$

$$\text{mesh 2} \quad +10\text{k}i_2 - 10\text{k}i_1 + 4\text{k}i_2 + 10\text{k}i_2 = 0$$

$$\text{rearranging} \quad \left(\begin{array}{l} 15\text{k}i_1 - 10\text{k}i_2 = -10 \\ -10\text{k}i_1 + 24\text{k}i_2 = 0 \end{array} \right) \times \frac{10^{-3}}{5}$$

$$3i_1 - 2i_2 = -2\text{mA} \quad \textcircled{1}$$

multiply $\times \frac{3}{2}$

$$-2i_1 + \frac{24}{5}i_2 = 0 \quad \textcircled{2}$$

$$3i_1 - 2i_2 = -2\text{mA}$$

$$-3i_1 + \frac{36}{5}i_2 = 0$$

$$\left(-2 + \frac{36}{5}\right)i_2 = -2\text{mA}$$

$$i_2 = \frac{-2}{-2 + \frac{36}{5}}\text{mA} = -0.385\text{mA}$$

Substituting into $\textcircled{2}$

$$-2i_1 + \frac{24}{5}(-0.385\text{mA}) = 0$$


$$-2i_1 - 1.846\text{mA} = 0$$

$$i_1 = -0.923\text{mA}$$


$$i_0 = i_1 - i_2 = (-0.923\text{mA}) - (-0.385\text{mA}) = -0.538\text{mA}$$

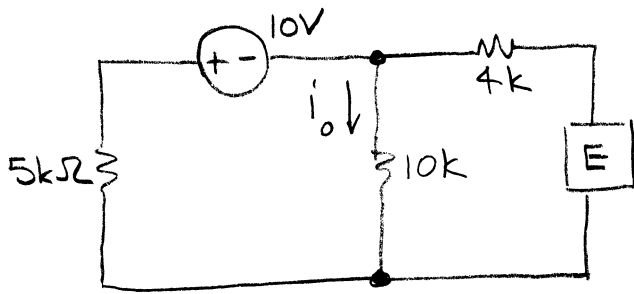Exercise 3-9

Use mesh analysis to find the current i_0 in the circuit below when the element E is



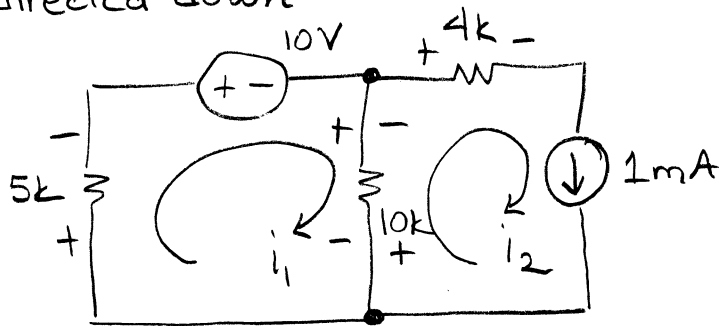- (a) a 1mA current source with the reference arrow directed down



This is a current source with a mesh current i_2 going through it. By inspection $i_2 = 1\text{mA}$ and we don't need to write a mesh equation for it.

$$\text{For mesh 1: } \begin{aligned} \text{KVL: } +5ki_1 + 10 + 10ki_1 - 10ki_2 &= 0 \\ (15ki_1 - 10ki_2 = -10) \times \frac{1}{5} \times 10^{-3} \end{aligned}$$

$$3i_1 - 2i_2 = -2\text{mA}$$

$$3i_1 - 2(1\text{mA}) = -2\text{mA}$$

$$\Rightarrow i_1 = 0$$

$$i_0 = i_1 - i_2 = (0) - (1\text{mA}) = -1\text{mA}$$

- (b) two 20 kΩ resistors in parallel.

We can replace the two parallel resistors by an equivalent R_{EQ} :

$$R_{EQ} = \frac{(20k)(20k)}{20k + 20k} = 10k$$

This is exactly the same problem as Example 3-8 b.