


SUPER POSITION

ANY OUTPUT CAN BE EXPRESSED AS A SUM OF CONTRIBUTIONS FROM EACH SOURCE IN THE CIRCUIT

TURN OFF ALL SOURCES BUT ONE


TURN "OFF"

voltage source

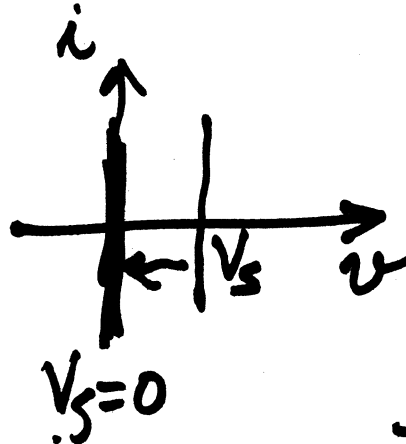


replace the voltage by a short

current source

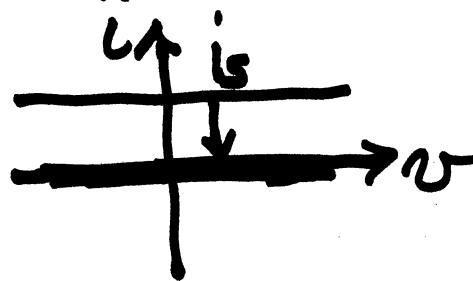


replace the current source by an open

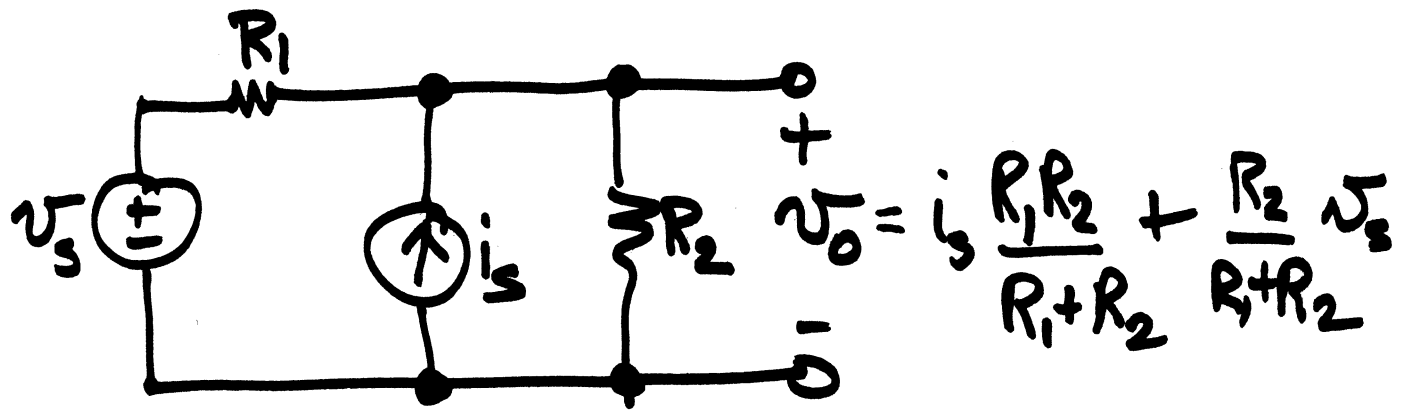


super position

① turn off the voltage source

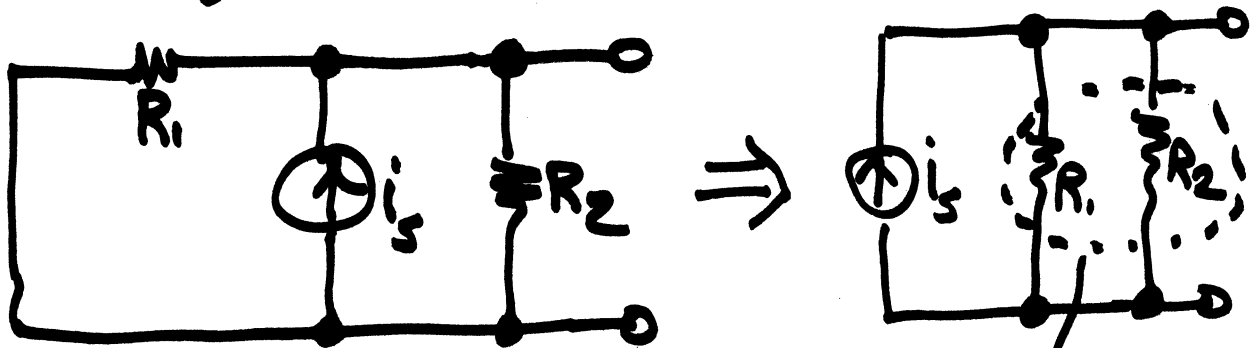

$$R_{EQ} = \frac{R_1 R_2}{R_1 + R_2}$$

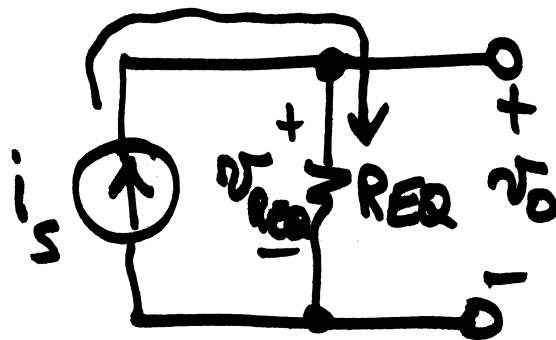


$$v_{R_{EQ}} = i_s R_{EQ} = v_o$$

contribution to v_o
from the current source


$$i_s \frac{R_1 R_2}{R_1 + R_2}$$

② TURN THE CURRENT SOURCE OFF


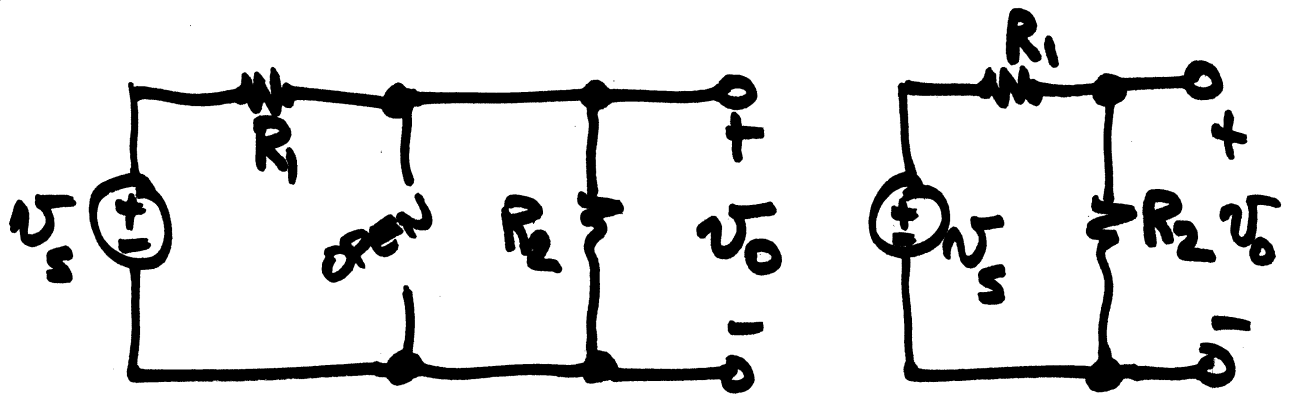


using voltage divider $V_0 = \frac{R_2}{R_1 + R_2} V_S$

Example 3-12

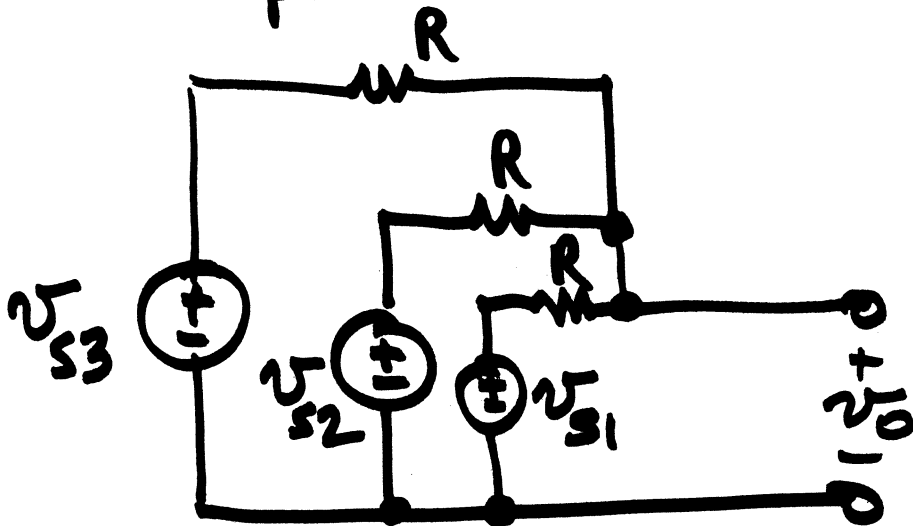

TURN OFF v_{s2} & v_{s3}

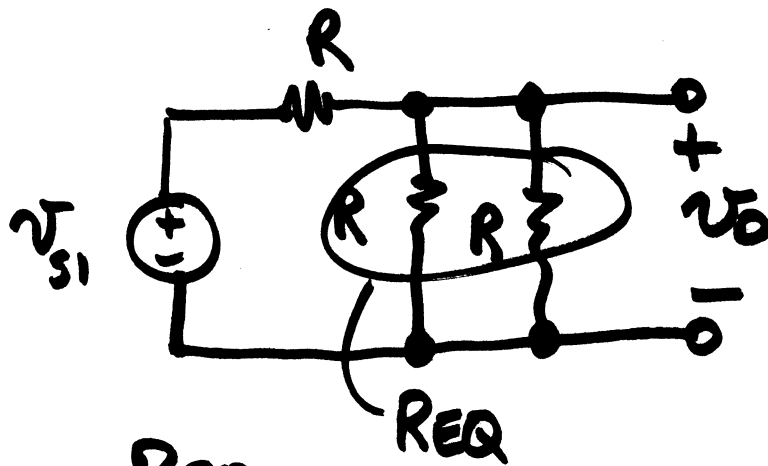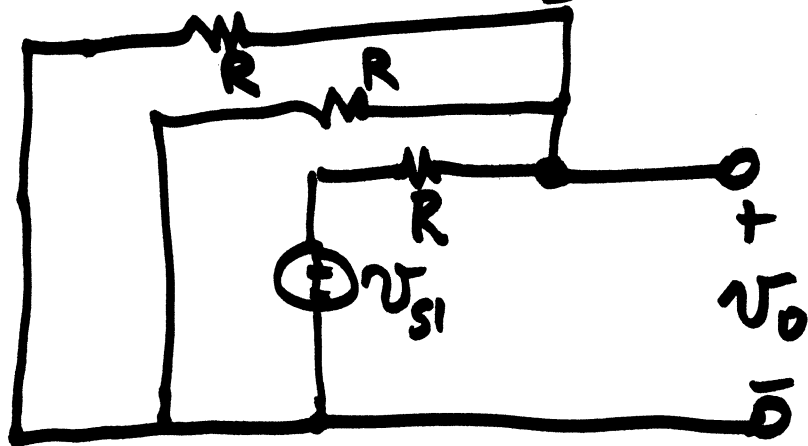

$$v_0 = \frac{R_{EQ}}{R + R_{EQ}} v_{s1}$$