
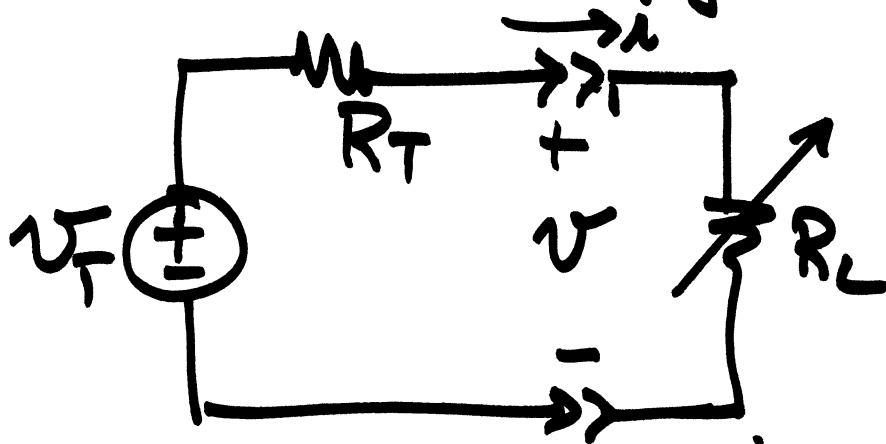


3.5 Maximum signal transfer

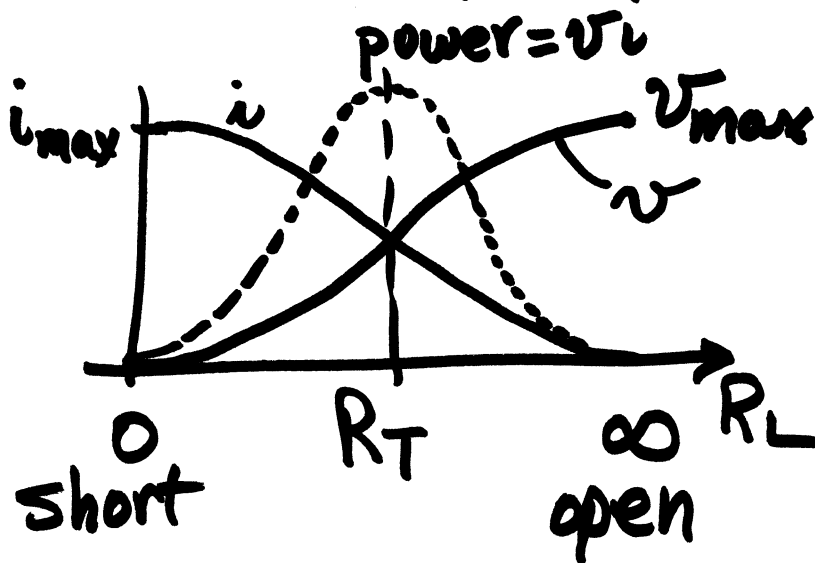

$$i = \frac{V_T}{R_T + R_L}$$



$$v = \frac{R_L}{R_T + R_L} V_T$$


$$P = v \cdot i = \frac{R_L}{R_T + R_L} V_T \cdot \frac{V_T}{R_T + R_L} = \frac{R_L V_T^2}{(R_T + R_L)^2}$$

What R_L maximizes P ?


$$\frac{\partial P}{\partial R_L} = 0$$

$$\frac{V_T^2}{(R_T + R_L)^2} + \frac{R_L V_T^2 (-2)}{(R_T + R_L)^3} = 0$$


$$R_L = R_T$$

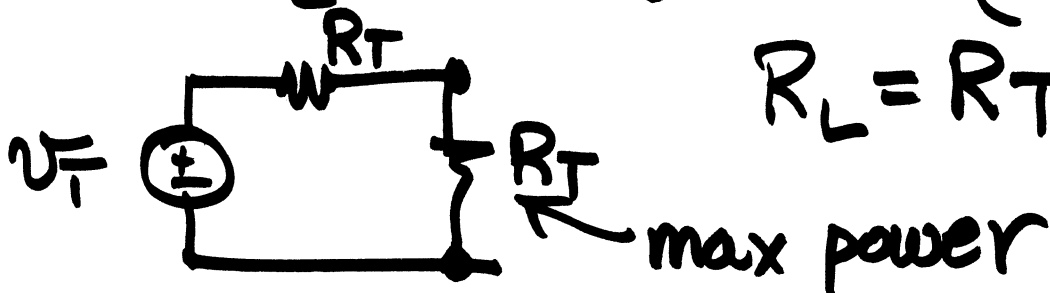


Example

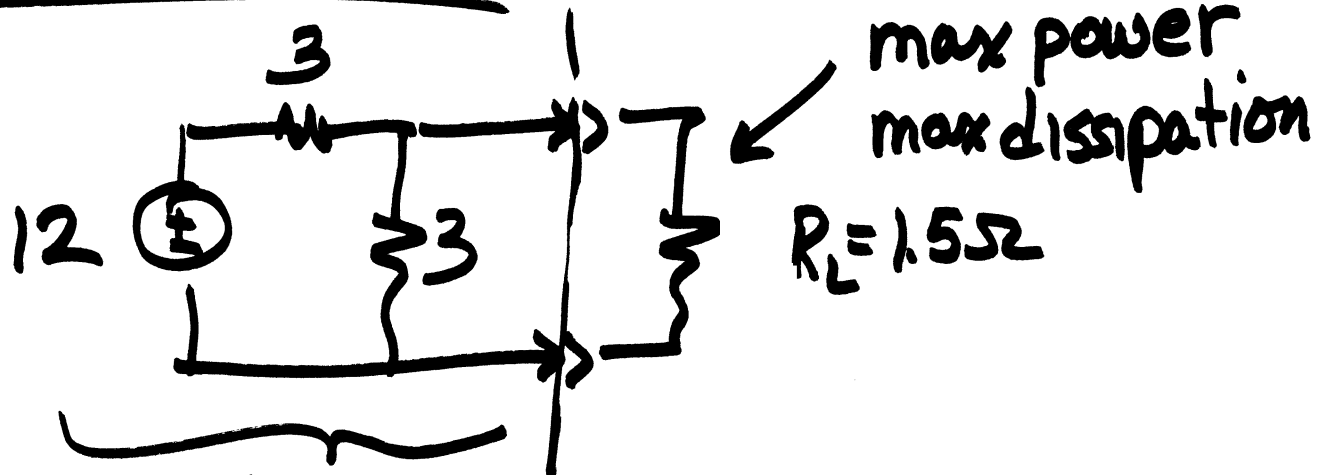

Thevenin's Theorem

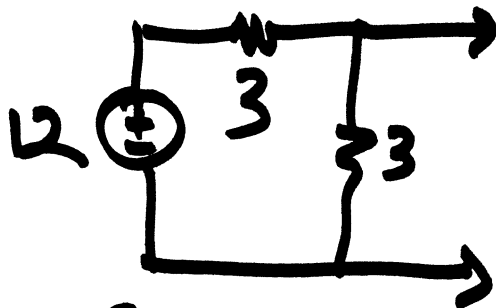

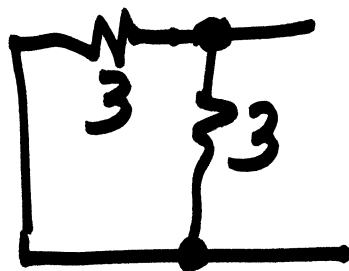
Find R_T ? Turn off all sources
and compute $R_{EQ} = R_T$



$$R_{EQ} = \frac{3 \cdot 3}{3 + 3} = 1.5\Omega$$


3-47

12


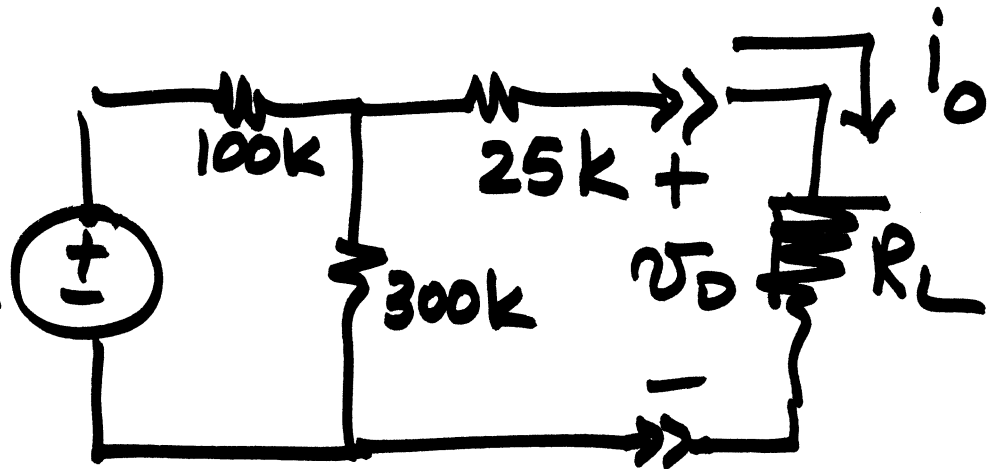


Thevenin equivalent circuit

R_T

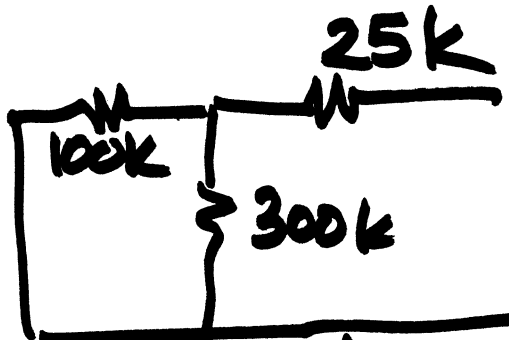


V_{oc} :

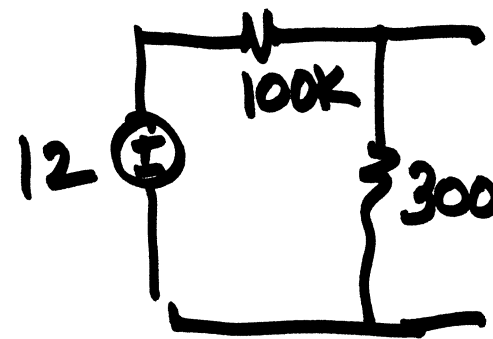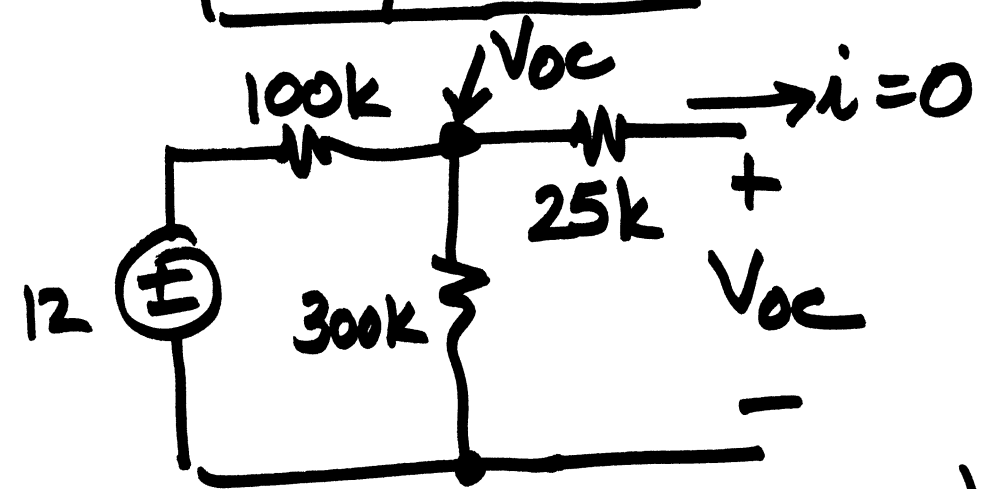

voltage divider

$$V_{oc} = \frac{300k}{100k + 300k} \cdot 12$$

Thevenin i, i Load

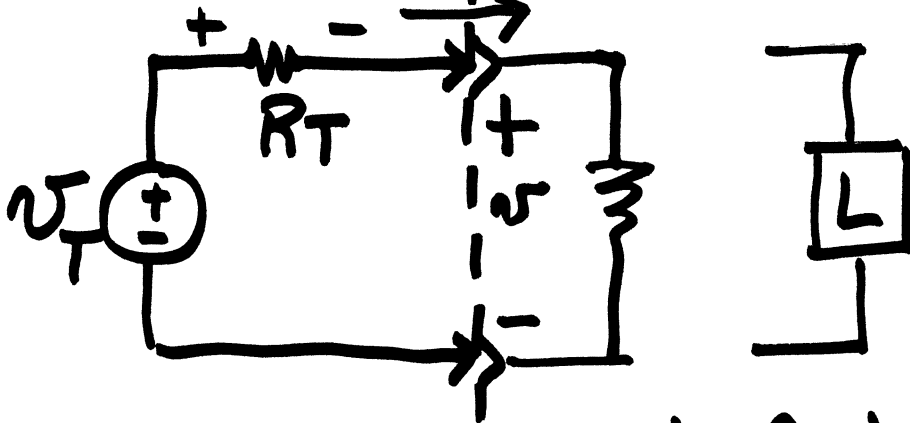



v, i terminal characteristics


series circuit \Rightarrow KVL

$$-V_T + i R_T + v = 0$$

$$i R_T = V_T - v$$
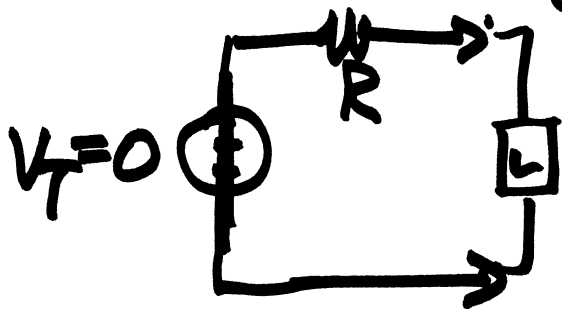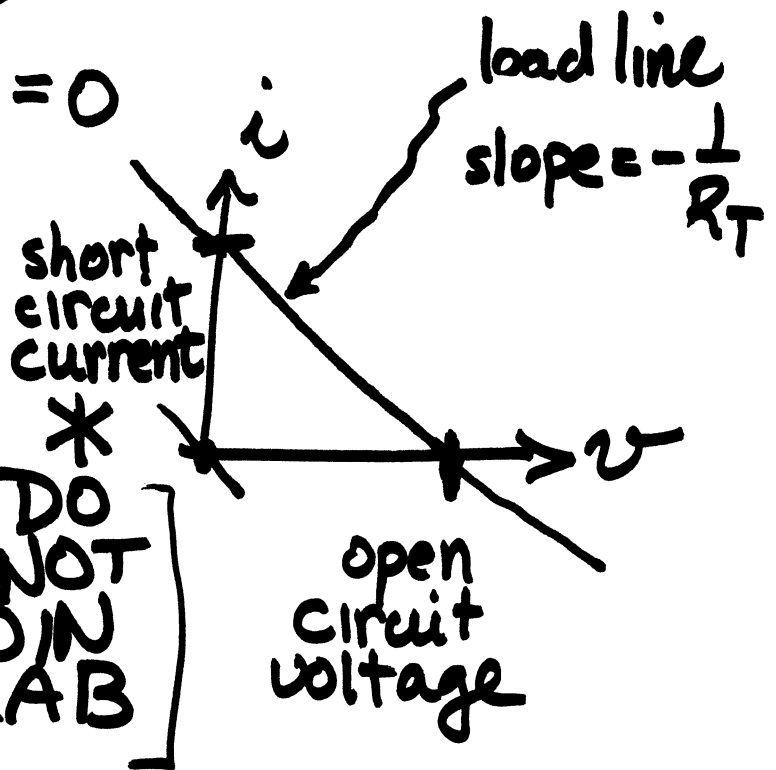
$$i = \frac{V_T}{R_T} - \frac{1}{R_T} v$$




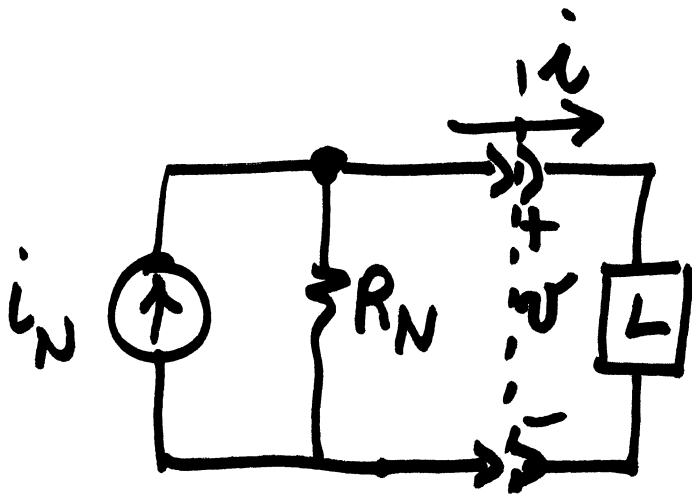

KCL

$$\sum i = 0$$

$$+i_N - \frac{v}{R_N} - i = 0$$

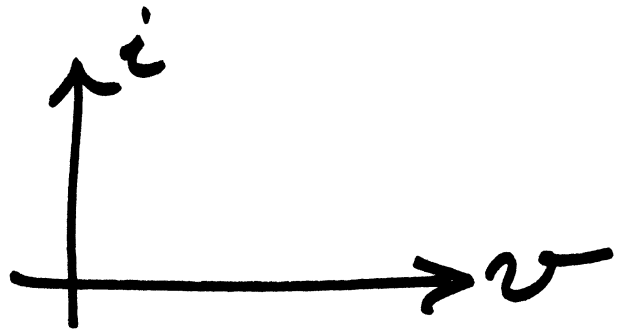

Norton:

$$i = i_N - \frac{v}{R_N}$$


Thevenin:

$$i = \frac{v_T}{R_T} - \frac{v}{R_T}$$






$$i_N = \frac{v_T}{R_T} \quad R_T = R_N$$

3-44 math. equation



i (mA)	-10	-5	0	+5	+10	12	13	14
v (V)	+5	+4	+3	+2	+1	0	-1	-2

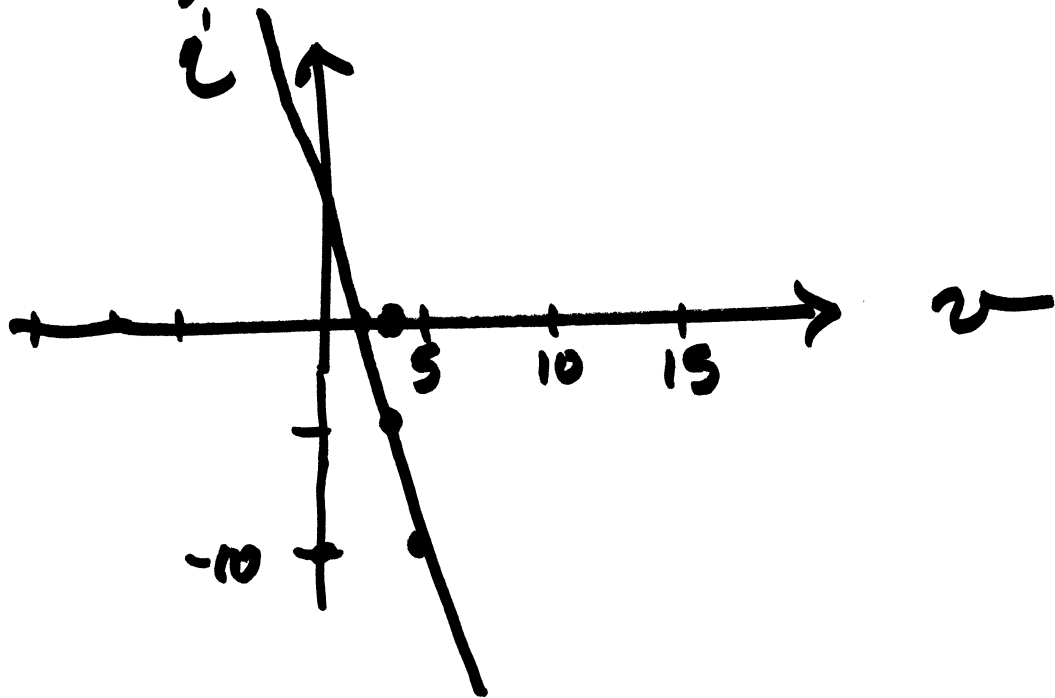



3-46 source transformations

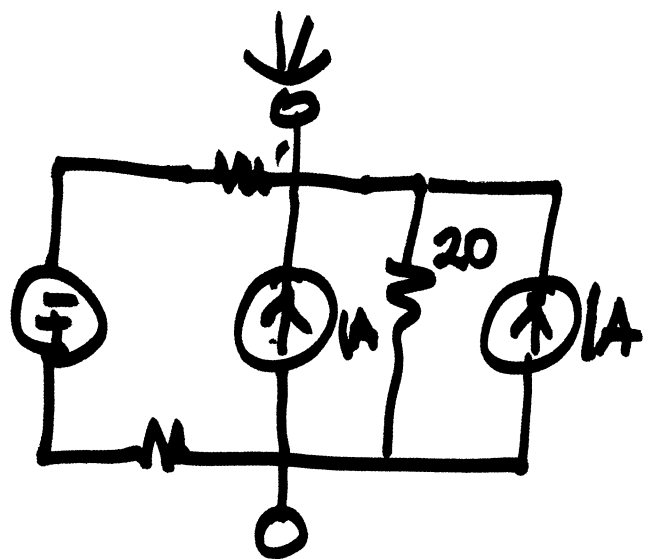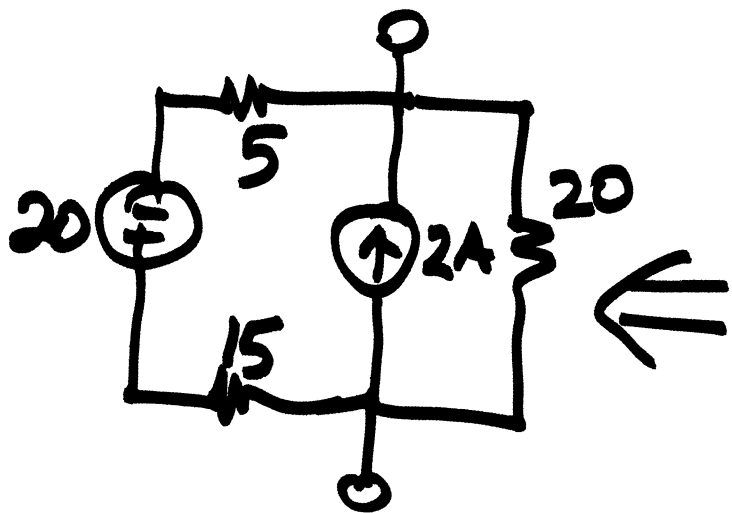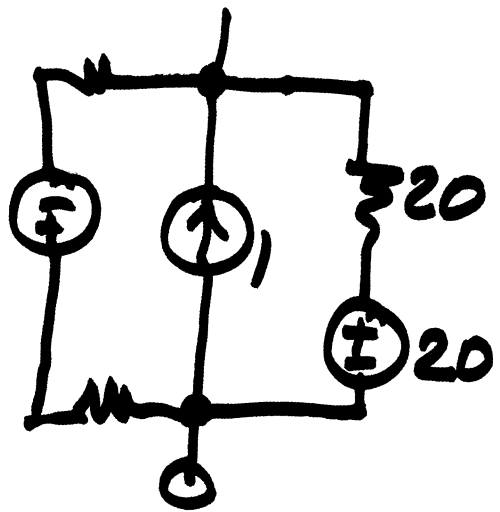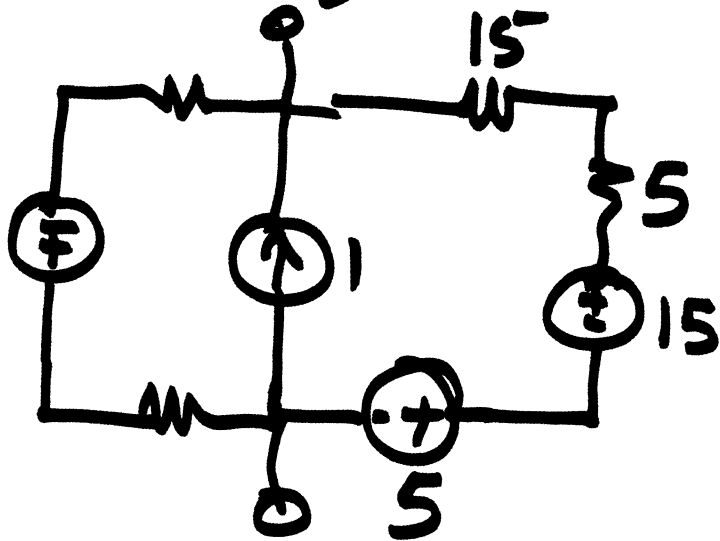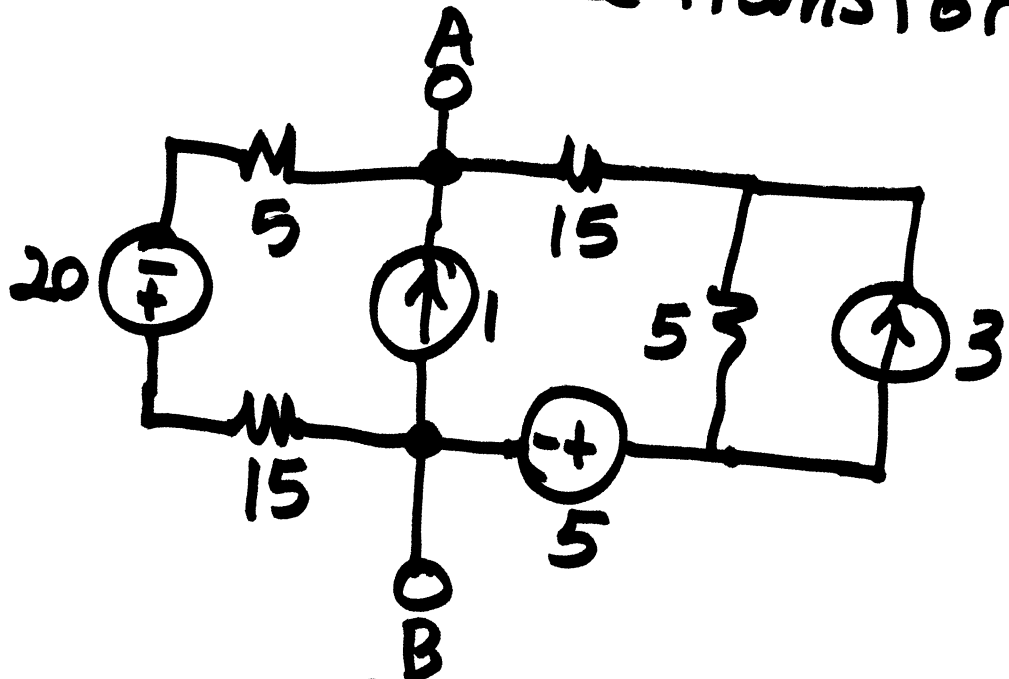


LAST YEAR'S QUIZ

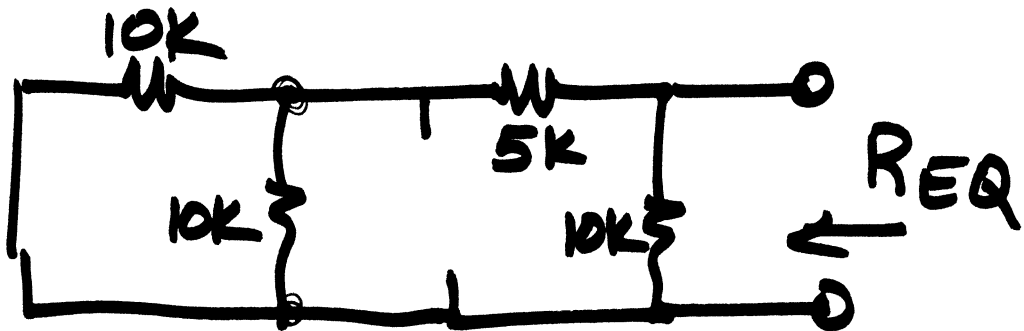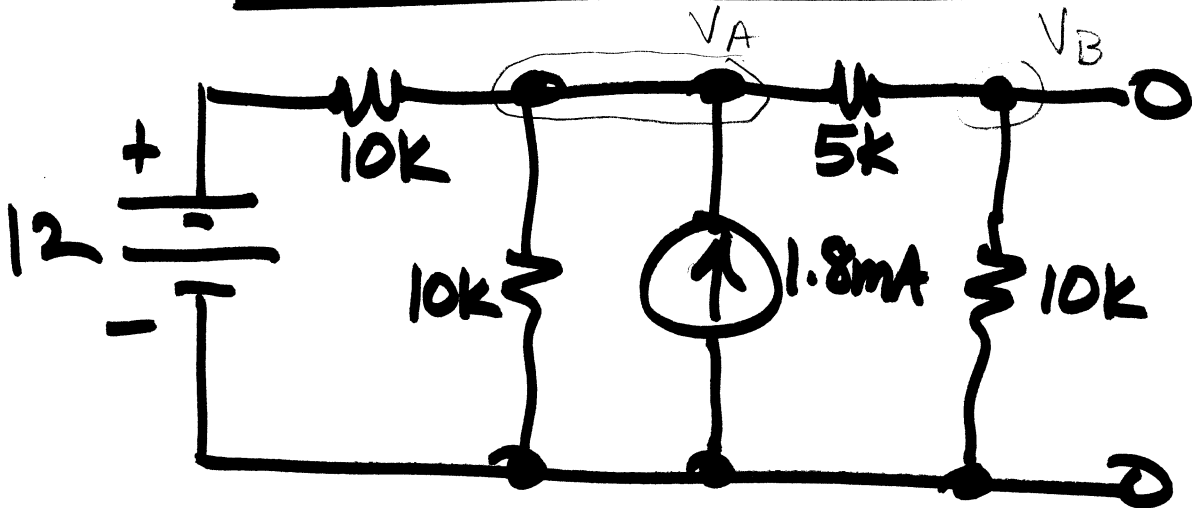

$$R_T = R_{EQ} = 5$$

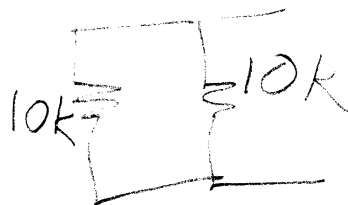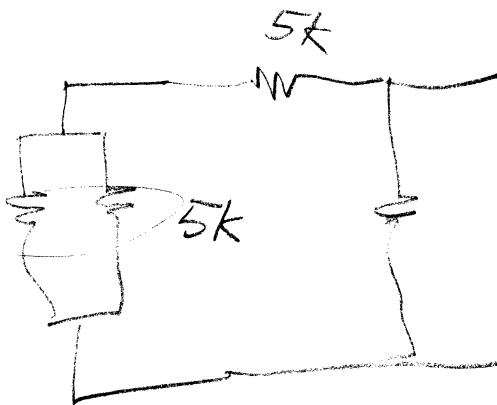

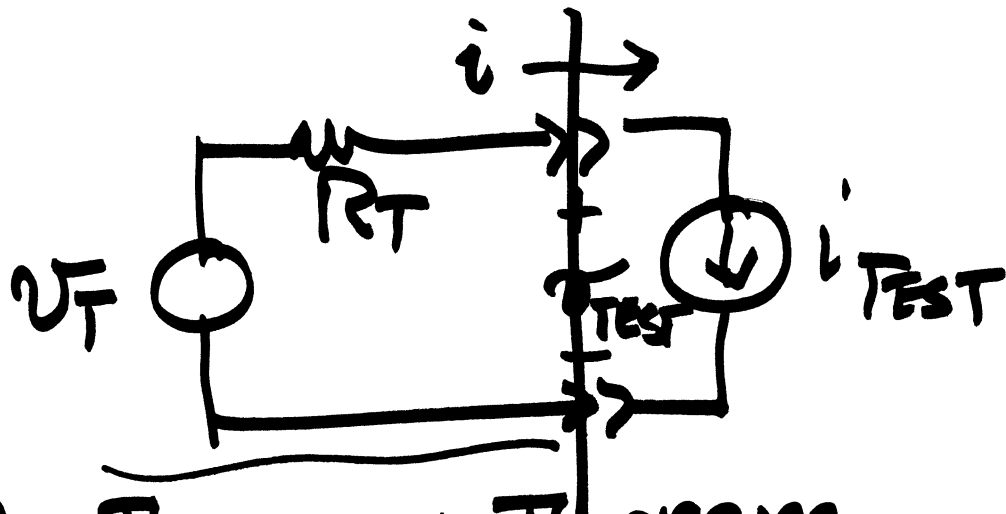

Proof of Thevenin's Theorem .

find V_{TEST} by superposition

$$V_{TEST} = V_{(volt.\ source)} + V_{(current\ source)}$$

