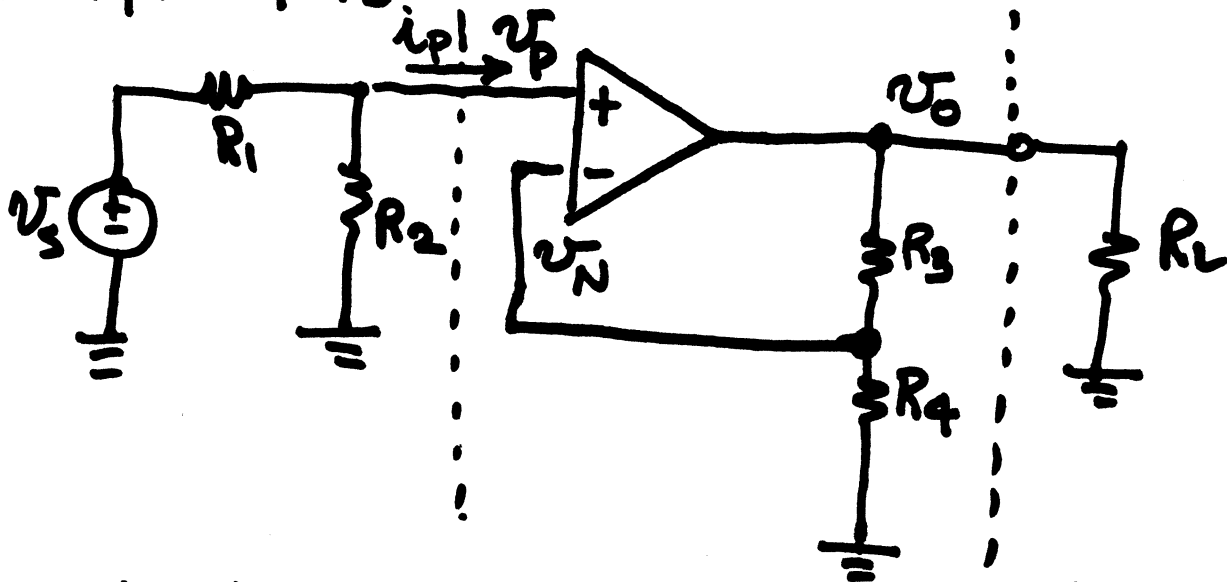


# Example 4-13



input voltage divider

op AMP amplifier


load

$$V_p = \frac{R_2}{R_1 + R_2} V_s \quad \rightarrow \quad V_n = \frac{R_4}{R_3 + R_4} V_o$$


block diagrams

$$\frac{V_o}{V_s} = K_1 K_2$$
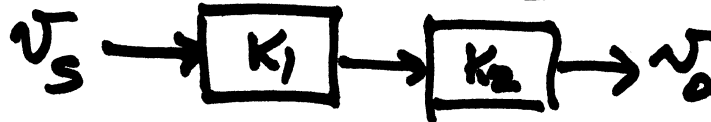
$$V_o = \frac{R_2}{R_1 + R_2} \frac{R_3 + R_4}{R_4} V_s$$




# Voltage Follower

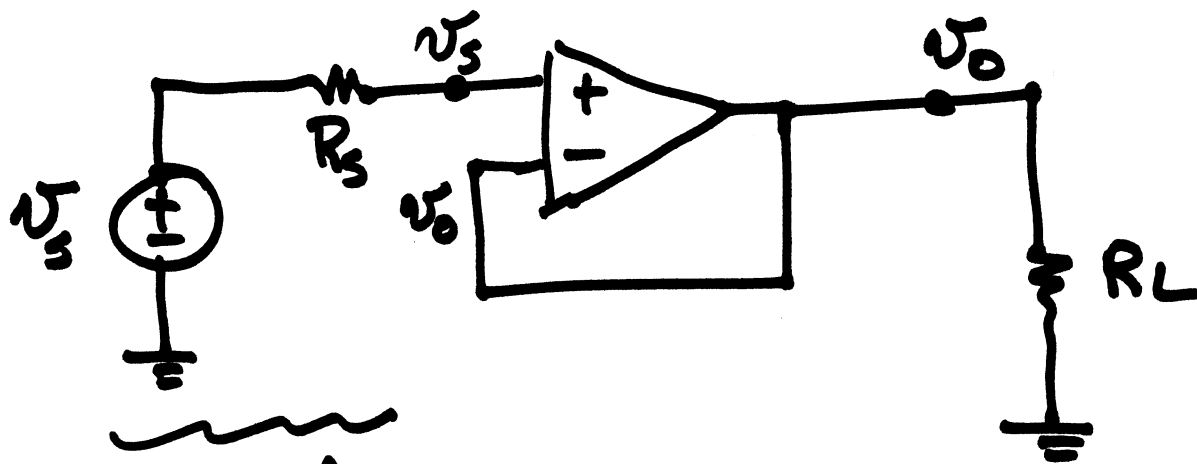


Thevenized  
input source

$$V_o = V_s$$

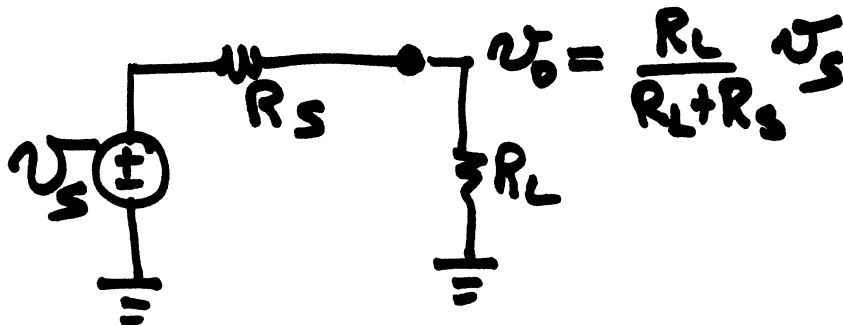increases  
output voltage  
and power  
to load




# Exercise 4-10

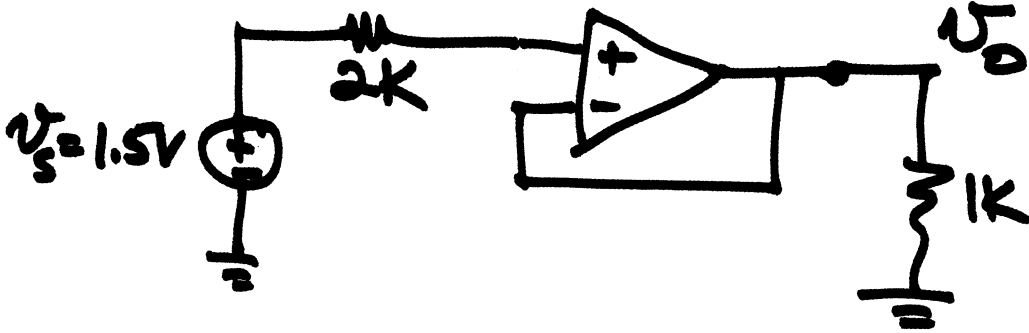


$$v_o = 1.5$$
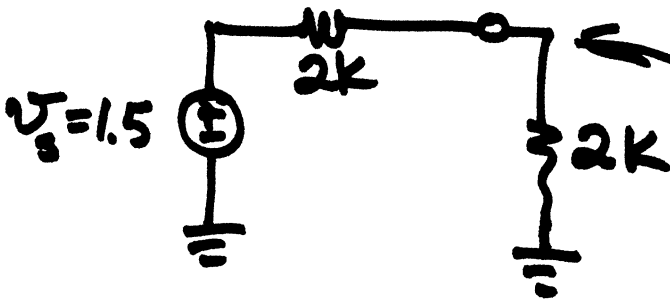
$$P_{OUT} = \frac{(1.5)^2}{1000} = 2.25 \text{ mW}$$



$$v_o = \frac{2k}{2k+2k} v_s = \frac{1}{2}(1.5)$$

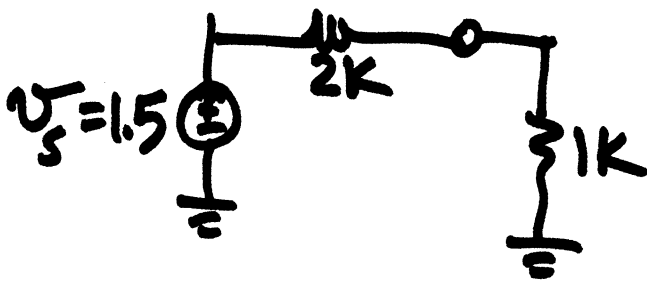
$$P_{OUT} = \frac{v_o^2}{R} = \frac{(\frac{1.5}{2})^2}{2000} = 0.281 \text{ mW}$$




$$v_o = \frac{1k}{2k+1k} v_s = \frac{1}{3}(1.5)$$

$$P_{OUT} = \frac{(\frac{1.5}{3})^2}{1000} = 0.25 \text{ mW}$$

# Exercise 4-34

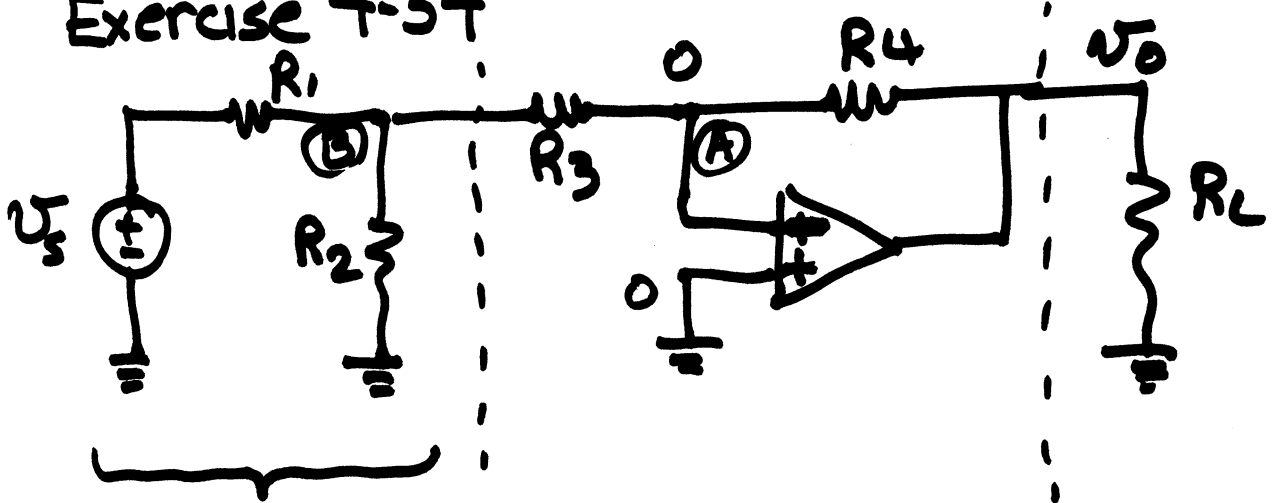

Thevenize

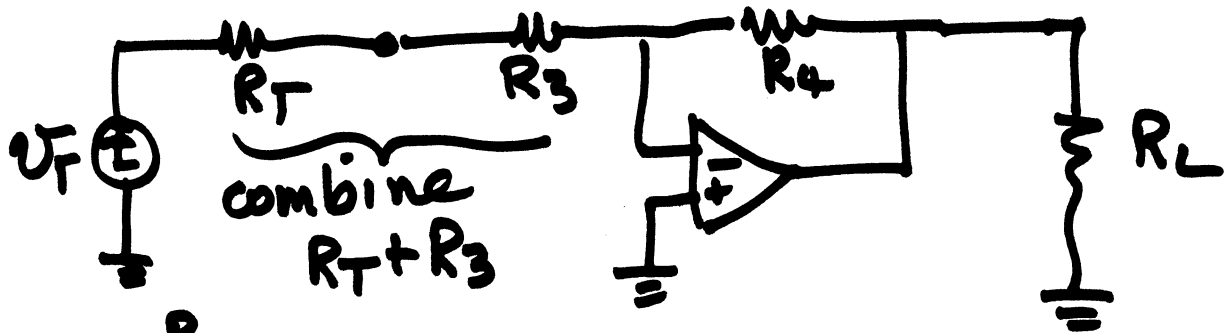


$$v_T = \frac{R_2}{R_1 + R_2} v_s$$

$$R_T = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$


amplifier  $v_o = - \frac{R_4}{R_T + R_3} v_T$

$$v_o = - \frac{R_2 R_4}{R_1 R_2 + R_1 R_3 + R_2 R_3} v_s \text{ after algebra}$$


# Exercise 4-11

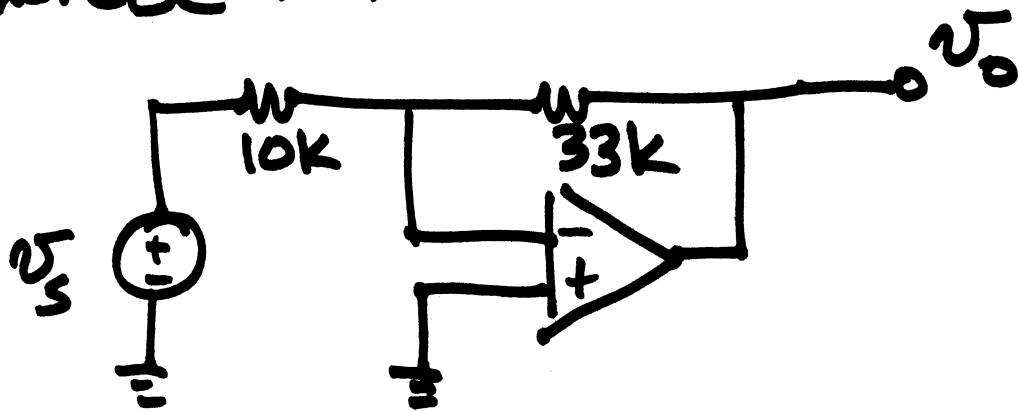
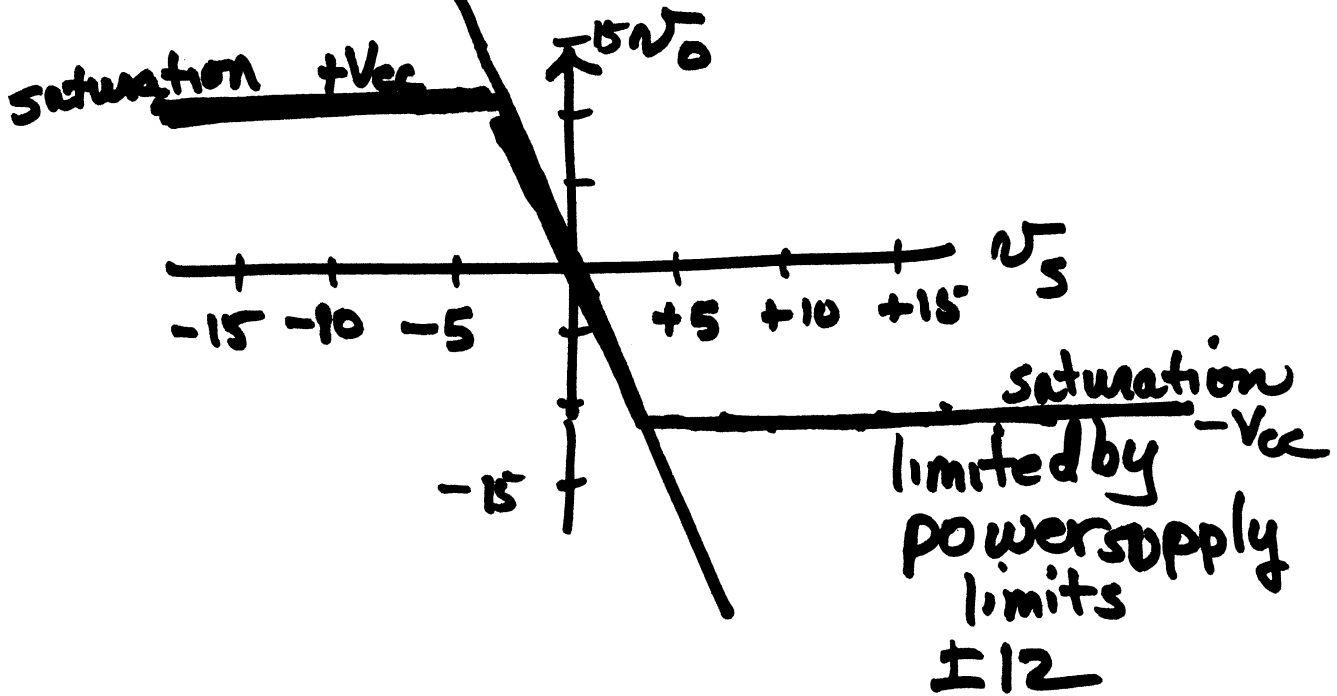
$$v_o = -\frac{33k}{10k} v_s = -3.3 v_s$$



# Example 4-18

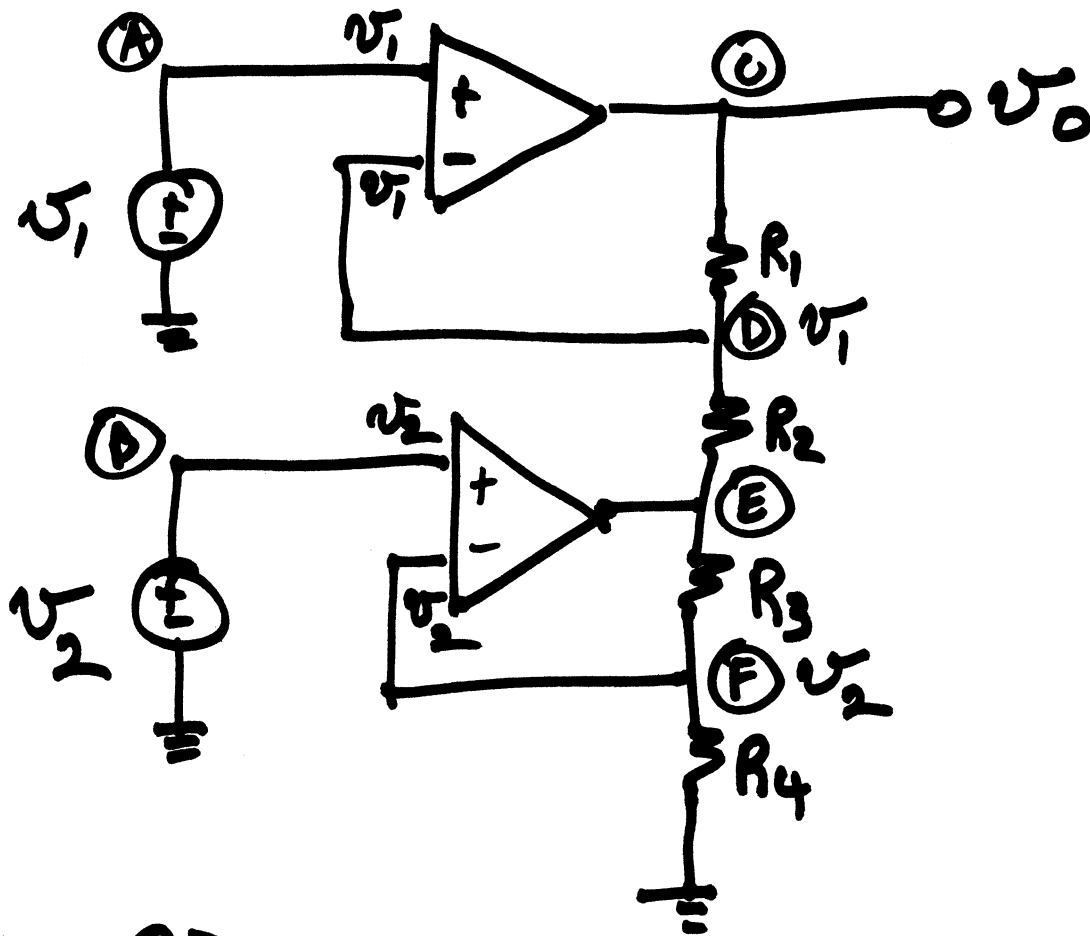

KCL @ D

$$\frac{v_0 - v_1}{R_1} - \frac{v_1 - v_E}{R_2} = 0$$

KCL @ F

$$\frac{v_E - v_2}{R_3} - \frac{v_2 - 0}{R_4} = 0$$

$$v_0 = \frac{R_1 + R_2}{R_2} v_1 - \frac{R_1}{R_2 R_4} (R_3 + R_4) v_2$$