
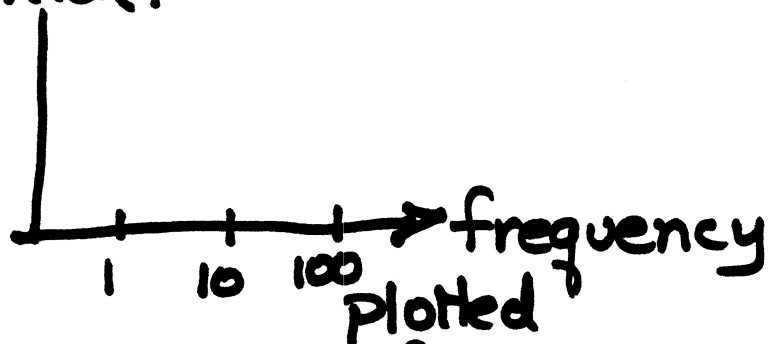


Frequency response (Bode plot)

Horizontal:

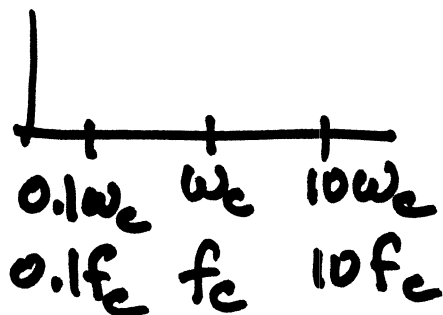

Plotted
as f or ω
in decades (powers of 10)
octaves



Vertical:

plot gain

$$T(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)}$$

in phasor domain
(for sinusoids)

phasor - complex number

$$T(j\omega) = \underline{\underline{\underline{|T(j\omega)| \angle T(j\omega)}}}}$$

usually plot the magnitude


decibels plot gain (vertical axis)
indecibels

$$|T(j\omega)|_{dB} = 20 \log_{10} |T(j\omega)|$$

for cutoff frequency $\omega_c \Rightarrow \left| \frac{T(j\omega)}{\sqrt{2}} \right|$

$$20 \log_{10} \left| \frac{T(j\omega)}{\sqrt{2}} \right| = 20 \log_{10} |T(j\omega)| - 20 \log_{10} \sqrt{2}$$

$$= 20 \log_{10} |T(j\omega)| - 3 \text{ dB}$$

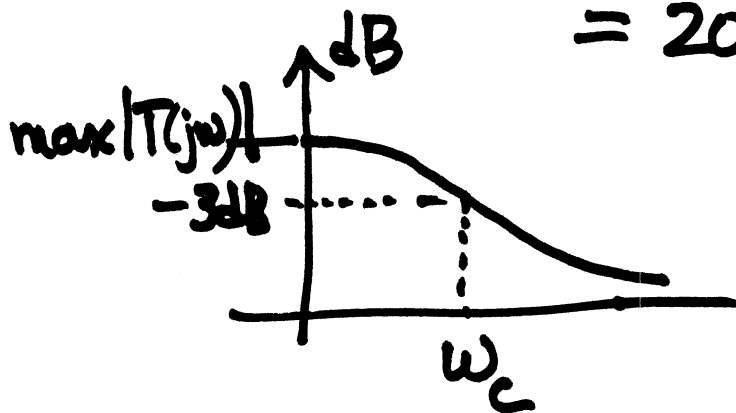


cutoff frequency
is often called the
3dB frequency

numerator: $20 \log_{10}(1) \rightarrow 0 \text{ dB}$

denominator: $\frac{\omega L}{R} \gg 1 \quad -20 \log_{10} \frac{\omega L}{R}$

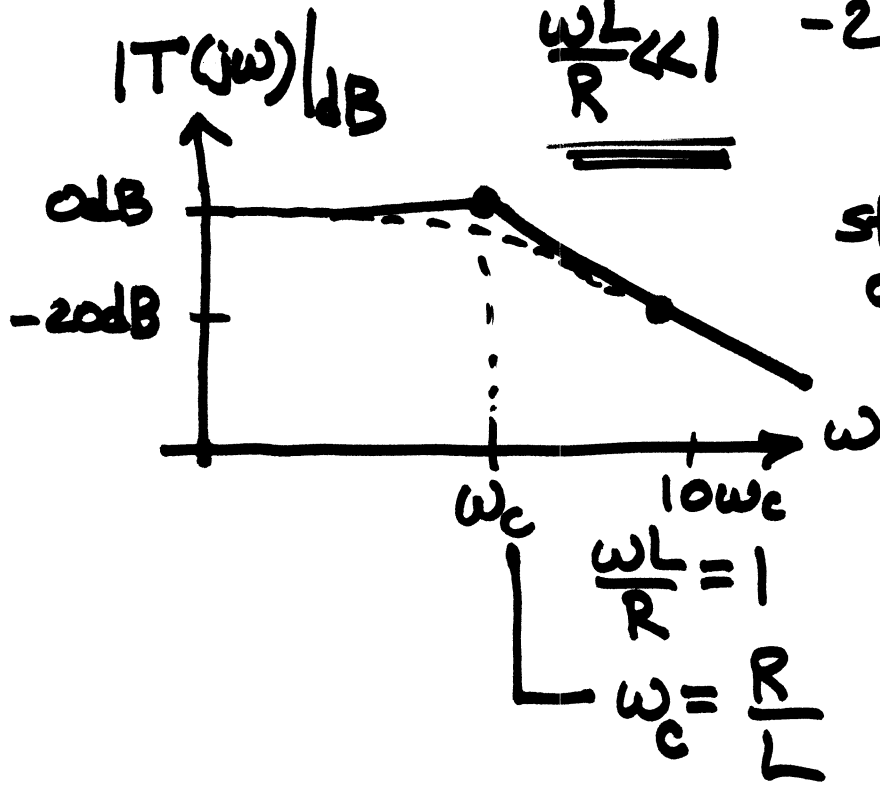$\frac{\omega L}{R} \ll 1 \quad -20 \log_{10}(1) \rightarrow 0 \text{ dB}$



straight-line approximation


always occurs when denom. is $1 + j$

$-20 \log_{10} \frac{\omega L}{R}$

suppose $\omega \rightarrow 10\omega$

$-20 \log_{10} \frac{10\omega L}{R} \rightarrow -20 \log_{10} 10 - 20 \log_{10} \frac{\omega L}{R}$
 $-20 \quad -20 \log_{10} \frac{\omega L}{R}$
 \uparrow
 -20 dB/decade

Example 12-2

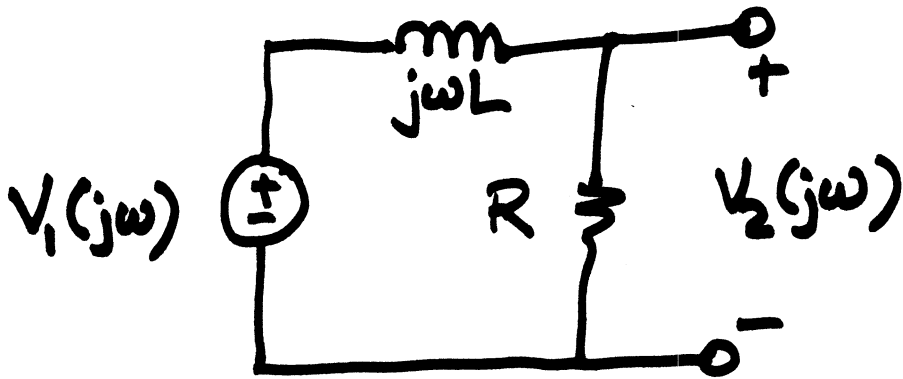

voltage divider $V_2(j\omega) = \frac{R}{R + j\omega L} V_1(j\omega)$

gain $T(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{R}{R + j\omega L} = \frac{1}{1 + j\frac{\omega L}{R}}$

divide by R
to get a leading 1
this is "standard" form

$$20 \log_{10} |T(j\omega)| = 20 \log_{10} \left| \frac{1}{1 + j\frac{\omega L}{R}} \right|$$

$$= 20 \log_{10} |1| - 20 \log_{10} \left| 1 + j\frac{\omega L}{R} \right|$$

0dB


$$\frac{\omega L}{R} \ll 1 \quad -20 \log_{10} |1|$$

0dB

$$\frac{\omega L}{R} \gg 1 \quad -20 \log_{10} \left| j\frac{\omega L}{R} \right|$$

$$-20 \log_{10} \frac{\omega L}{R}$$

Example 12-3

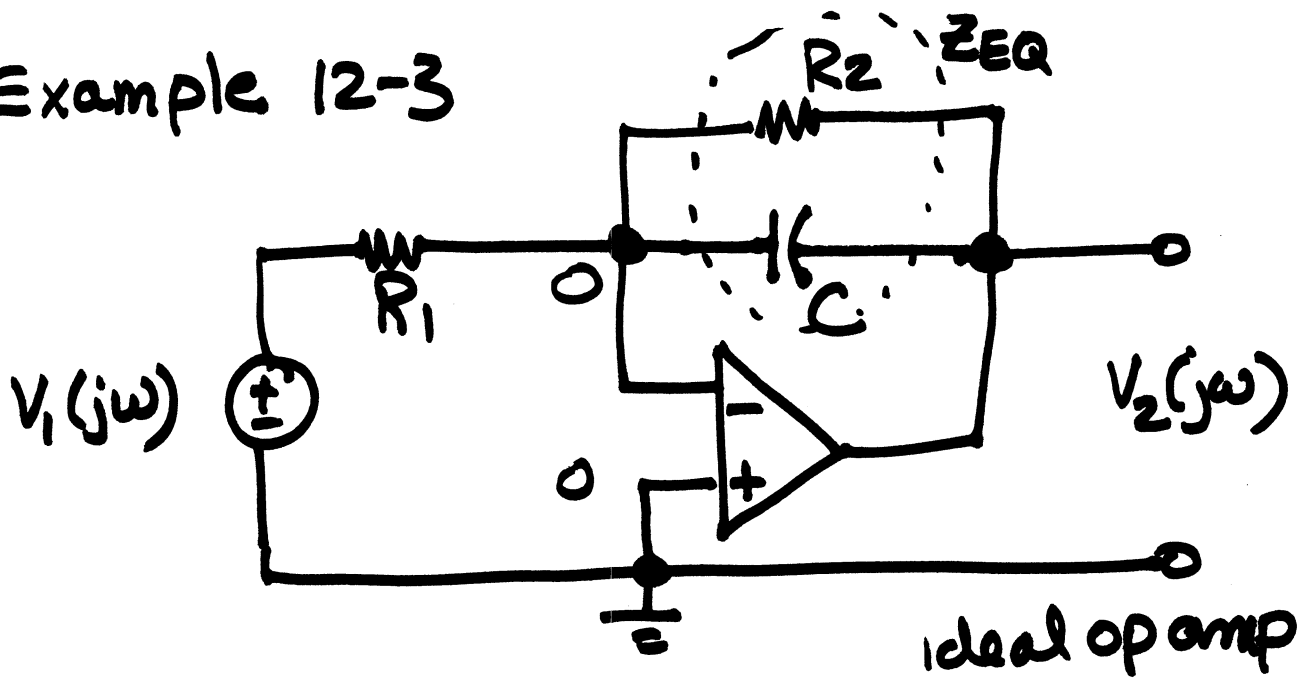


Find the gain $\frac{V_2(j\omega)}{V_1(j\omega)}$

$$Z_{EQ} = R_2 \parallel \frac{1}{j\omega C}$$

$$= \frac{R_2 \left(\frac{1}{j\omega C} \right)}{R_2 + \frac{1}{j\omega C}}$$

$$Z_{EQ} = \frac{R_2}{j\omega R_2 C + 1}$$
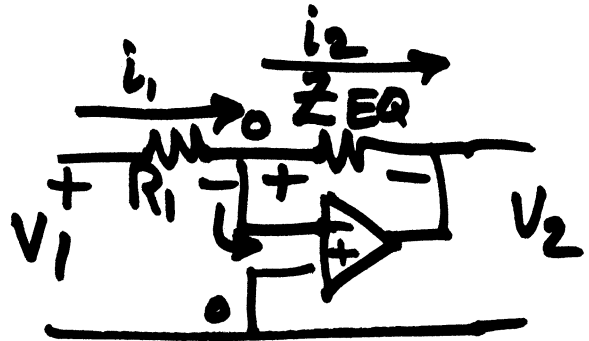
$$\frac{1}{Z_{EQ}} = \frac{1}{R_2} + \frac{1}{\frac{1}{j\omega C}}$$



$$i_1 = \frac{V_1(j\omega) - 0}{R_1}$$

$$i_2 = \frac{0 - V_2(j\omega)}{Z_{EQ}}$$

$i_1 = i_2$ for ideal op-amp since $i_{IN} = 0$

$$\frac{V_1(j\omega)}{R_1} = - \frac{V_2(j\omega)}{Z_{EQ}}$$

$$\frac{V_2(j\omega)}{V_1(j\omega)} = - \frac{Z_{EQ}}{R_1} = - \frac{R_2}{1 + j\omega R_2 C}$$

Plot $\frac{V_2(j\omega)}{V_1(j\omega)} = -\frac{R_2/R_1}{1+j\omega R_2 C}$

$$20 \log_{10} \left| \frac{-\frac{R_2}{R_1}}{1+j\omega R_2 C} \right| = 20 \log_{10} \left(\frac{R_2}{R_1} \right) - 20 \log_{10} (1+j\omega R_2 C)$$

