

MU QUIZ #3 OLIN 408
3:30 TODAY

Two methods to solve transient problems

1. write equations in state variable

$$L \rightarrow i$$

$$C \rightarrow v$$


2. initial - final value theorem

$$(IV - FV)e^{-\frac{t}{T_c}} + FV$$

IV - initial value

FV - final value

T_c - time constant

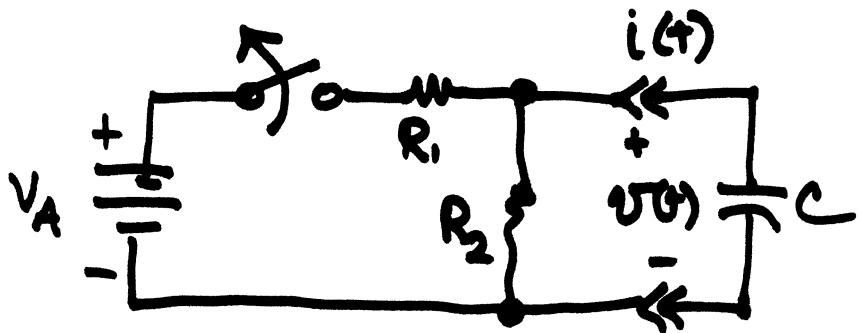

1. initial condition value

dc or steady state value before
switch opens

$$V_{R_2} = \frac{R_2}{R_1 + R_2} V_A$$


$$i_c = 0$$

$$i_c = C \frac{dV_c}{dt}$$

capacitor
acting like
an open

$$V_c(0) = V_{R_2} = \frac{R_2}{R_1 + R_2} V_A$$


2. final value $t \rightarrow \infty$

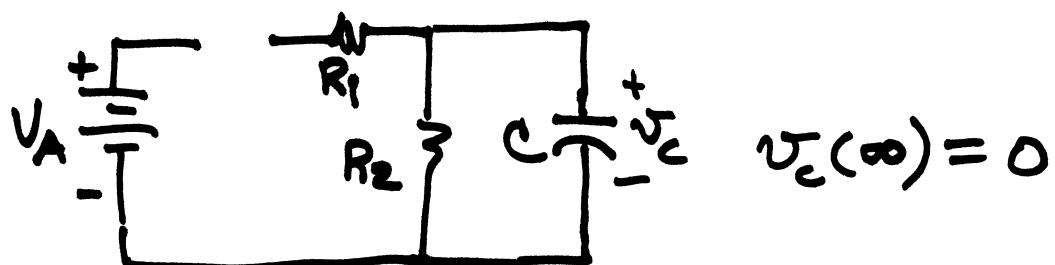

3. Time constant $t \geq 0$


$$T_C = \frac{1}{R_2 C}$$

Example 7-8

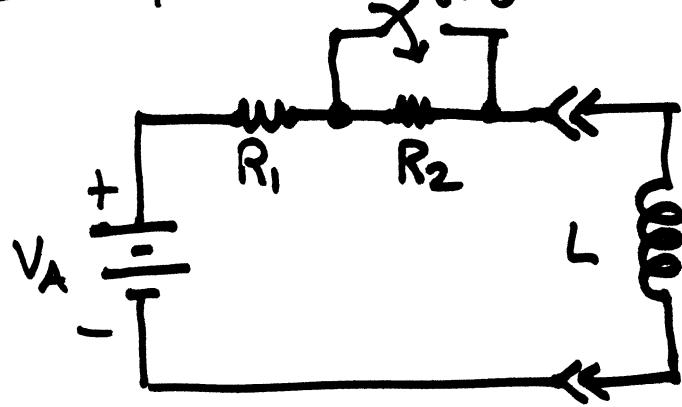


1. initial value $t < 0$


steady state

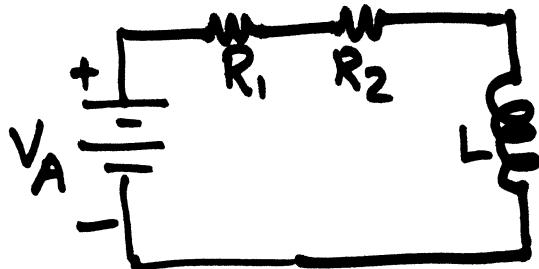

$$V_L = L \frac{di}{dt} \Big|_{t=0} = 0$$

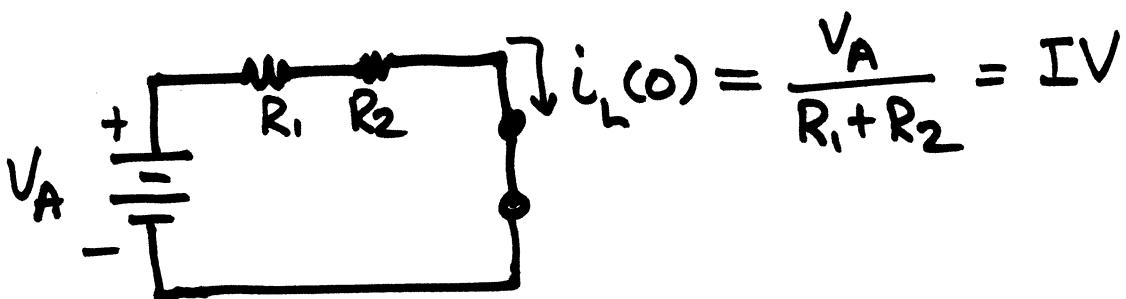


2. final value $t \rightarrow \infty$

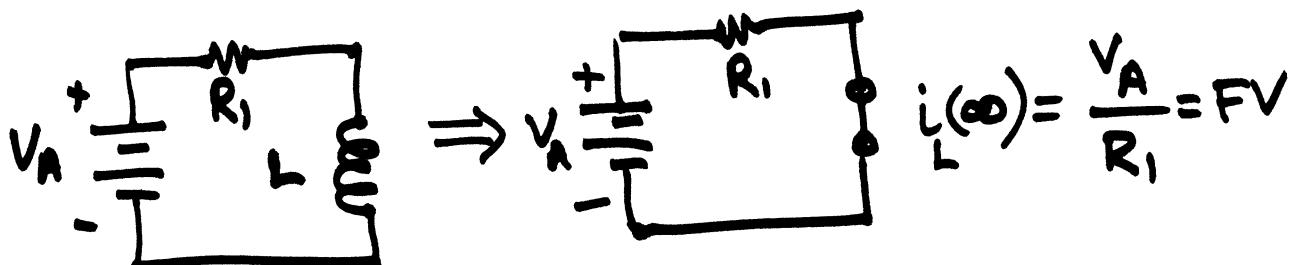


3. Time constant $t \geq 0$

$$\tau_c = \frac{L}{R_1}$$

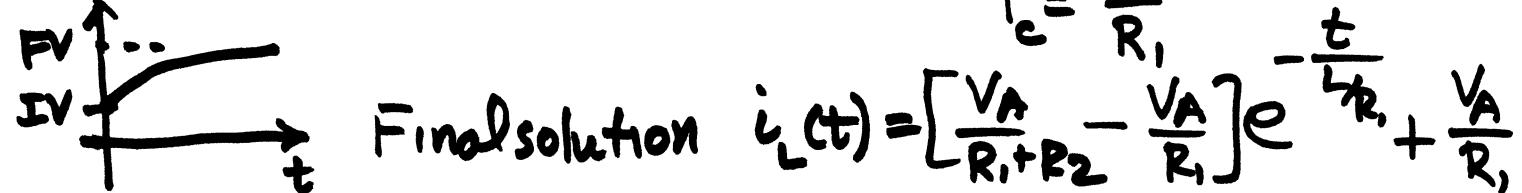

Example 7-9

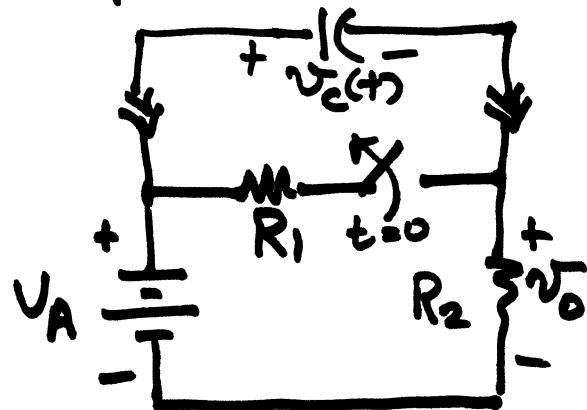

want $V_O(+)$


- Recognize that we will find $V_C(t)$ first.
state variable

- initial value

$t < 0$

steady state

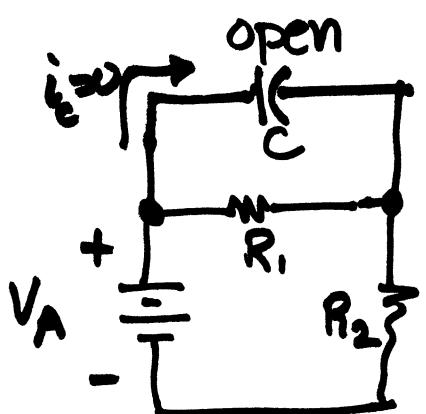
$$i_C = C \frac{dV_C}{dt} \xrightarrow{t \rightarrow 0} 0$$



$$V_C(0) = \frac{R_1}{R_1 + R_2} V_A = IV$$

voltage divider

- Final value $t \rightarrow \infty$

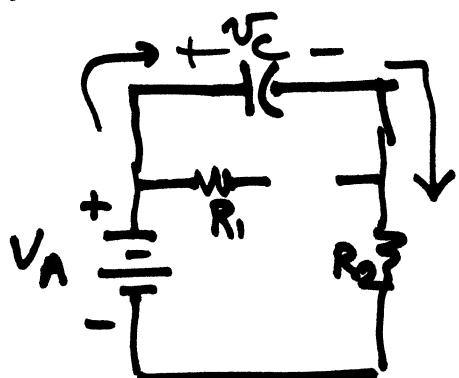


capacitor is fully charged
to V_A


$$-V_A + V_C(\infty) + V_{R_2}(\infty) = 0$$

$$V_C(\infty) = V_A$$

3. Time constant

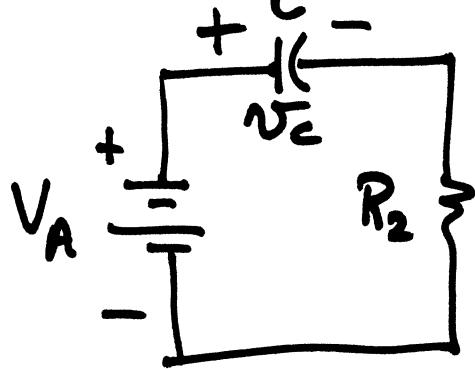


$$\tau_c = R_2 C$$

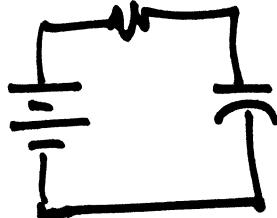

$$\begin{aligned} \bar{V}_c(t) &= (IV - FV) e^{-\frac{t}{\tau_c}} + FV \quad t \geq 0 \\ &= \left(\frac{R_1}{R_1 + R_2} V_A - V_A \right) e^{-\frac{t}{R_2 C}} + V_A \end{aligned}$$

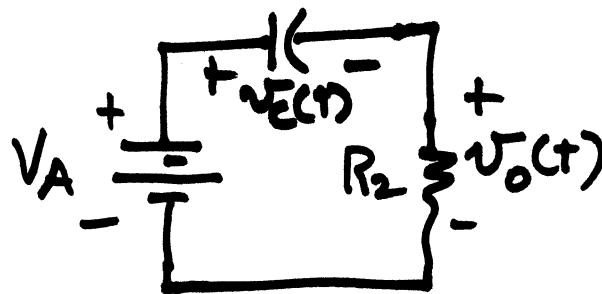4. find $\bar{V}_o(t)$ in terms of $\bar{V}_c(t)$ $t \geq 0$




KVL:

$$-V_A + \bar{V}_c(t) + V_o(t) = 0$$

$$V_o(t) = V_A - \bar{V}_c(t)$$

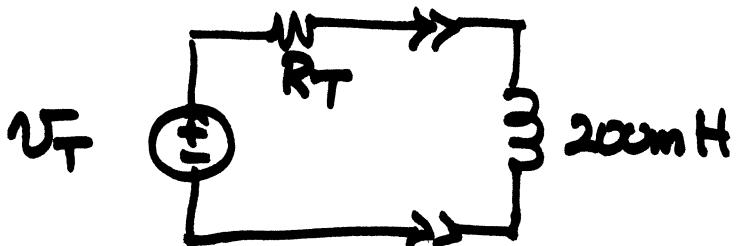Example 7-10

$$i_L(t) = 50 + 100e^{-5000t} \text{ mA}$$



(a) identify forced and natural responses

natural solution always of form Ke^{st}
 $i_{\text{natural}} = 100e^{-5000t}$


$$i_{\text{TOTAL}} = i_{\text{NATURAL}} + i_{\text{DC FORCED}}$$

$$i_{\text{FORCED}} = 50$$

(b) identify time constant $T_c = \frac{L}{R_T} = \frac{1}{5000} = 0.2 \text{ ms.}$

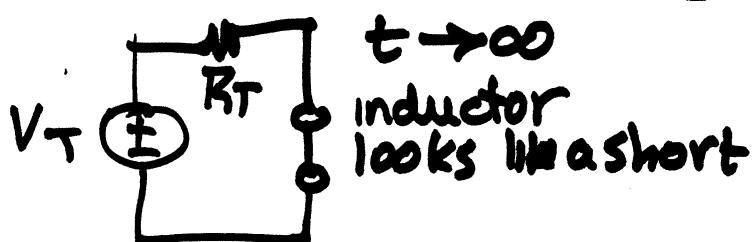(c) identify Thevenin equivalent circuit.

$$T_c = \frac{L}{R_T} \quad R_T = \frac{L}{T_c} = \frac{200 \text{ mH}}{0.2 \times 10^{-3} \text{ seconds}} = 1000 \Omega$$



$$\begin{aligned} i_L(\infty) &= 50 \text{ mA} \\ V_T &= R_T i_L(\infty) \\ &= (1000)(50 \text{ mA}) \\ &= 50 \text{ Volts} \end{aligned}$$