
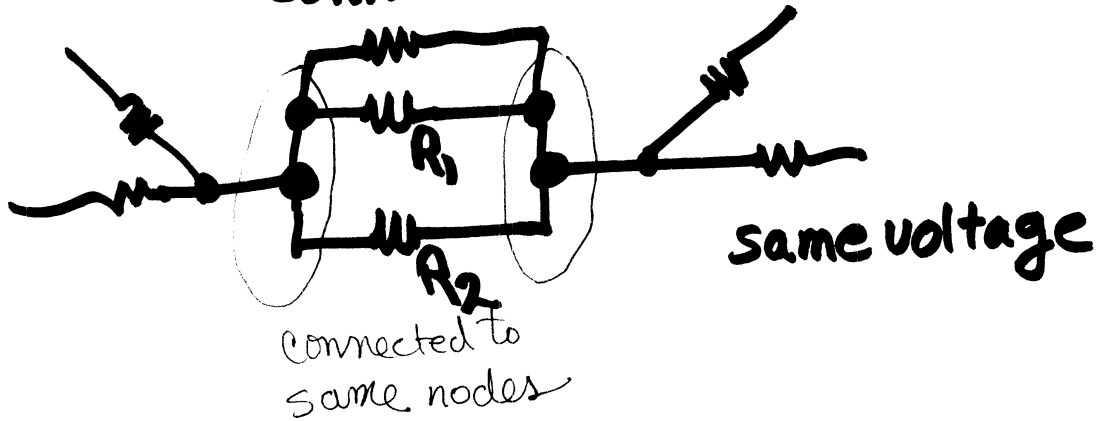


Series resistance

Parallel resistance

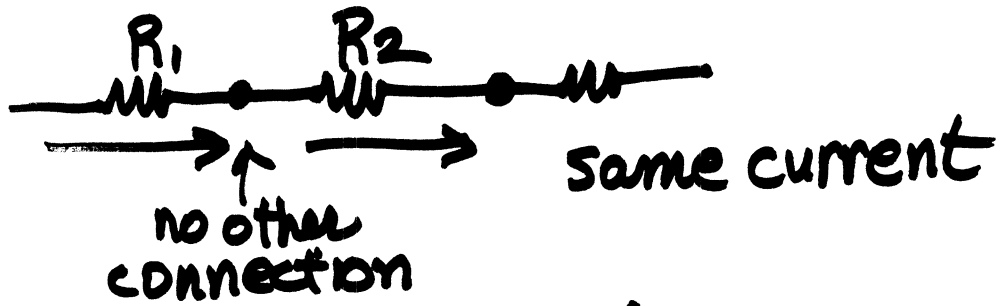


Simplify circuits

series: $R_{EQ} = R_1 + R_2$

parallel: $\frac{1}{R_{EQ}} = \frac{1}{R_1} + \frac{1}{R_2}$

equivalent resistance (series)

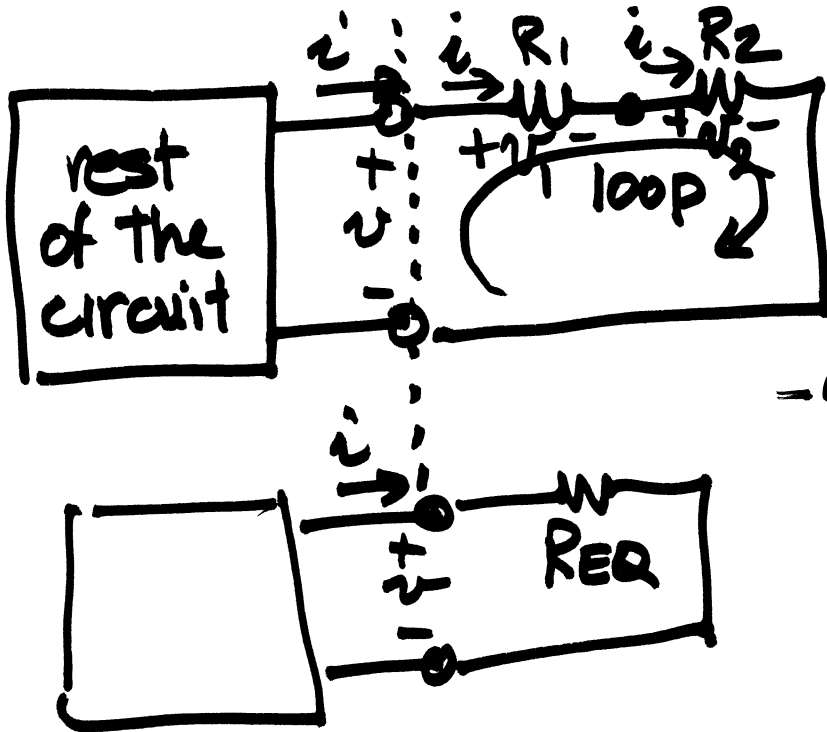

$$v_1 = iR_1$$

$$v_2 = iR_2$$

$$\text{KVL } \sum v = 0$$


$$-v + v_1 + v_2 = 0$$

$$-v + iR_1 + iR_2 = 0$$

$$v = i(R_1 + R_2)$$

$$v = iR_{EQ}$$

equivalent resistance (parallel)

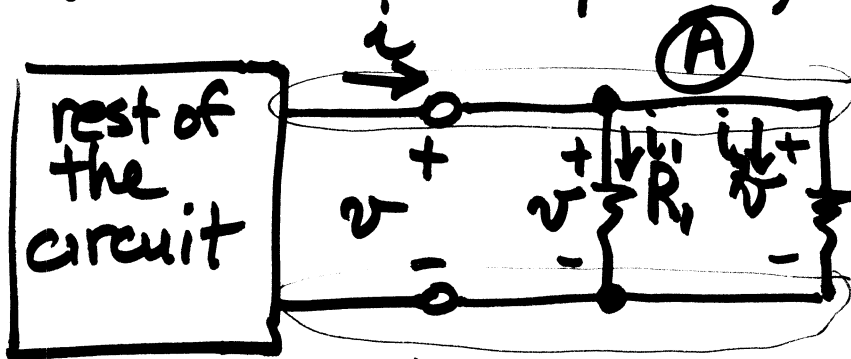

KCL upper node

$$\sum i = 0 \text{ (A)}$$

$$+i - i_1 - i_2 = 0$$

$$+i - \left(\frac{v}{R_1}\right) - \left(\frac{v}{R_2}\right) = 0$$

$$i = v \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$


$$i = \frac{v}{R_{EQ}} \quad \frac{1}{R_{EQ}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$R_{EQ} = \frac{R_1 R_2}{R_1 + R_2}$$


$$i_1 = \frac{v}{R_1}$$

$$i_2 = \frac{v}{R_2}$$



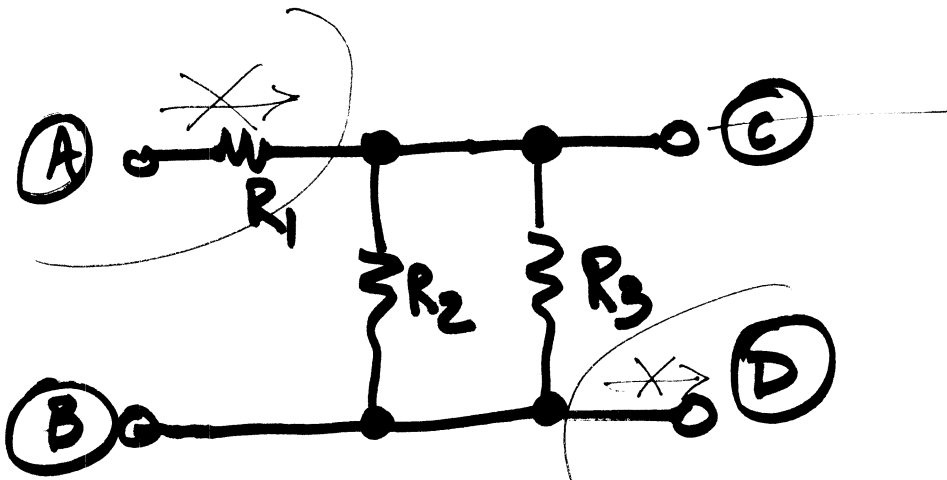


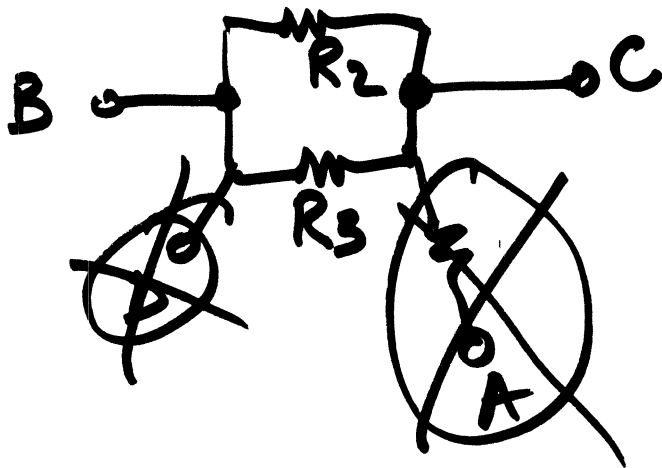
Resistance between \textcircled{C} - \textcircled{B}



$$R_{EQ} = \frac{R_2 R_3}{R_2 + R_3}$$



Source Transformation

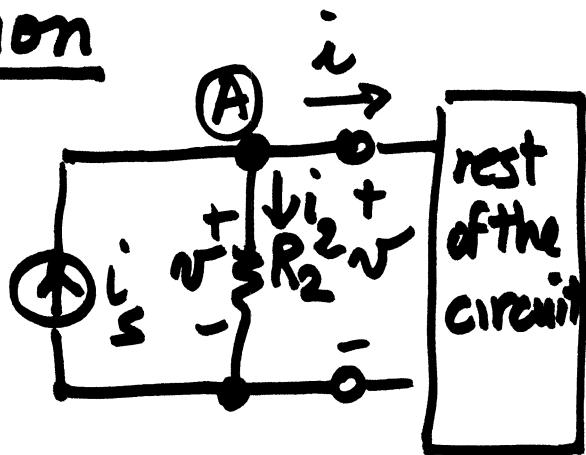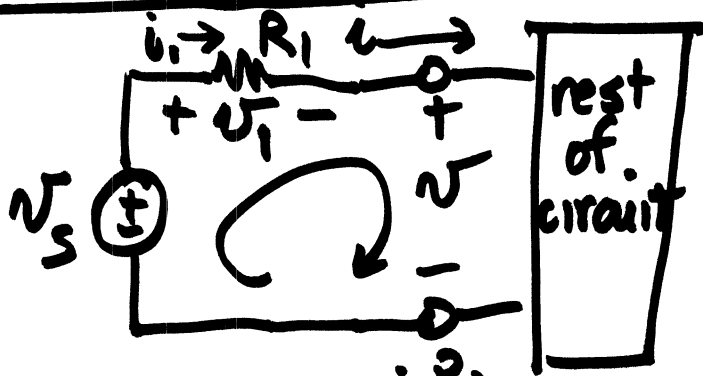

KVL $-v_s + v_1 + v = 0$

$-v_s + iR_1 + v = 0$

$v = v_s - iR_1$

@A $\sum i = 0$ $i_2 = \frac{v}{R_2}$

$+i_s - i_2 - i = 0$

$+i_s - \frac{v}{R_2} - i = 0$

$v = (i_s - i)R_2$

$v = i_s R_2 - iR_2$



require

$v_s = i_s R_2$



$R_1 = R_2$



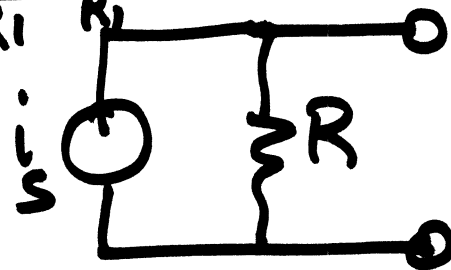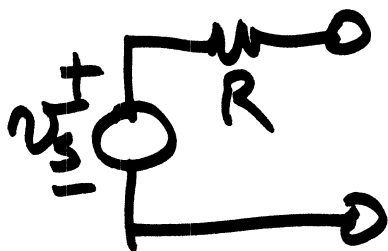$iR_1 = v_s - v$
 $i = \frac{v_s}{R_1} - \frac{v}{R_1}$



$i_s = \frac{v_s}{R}$

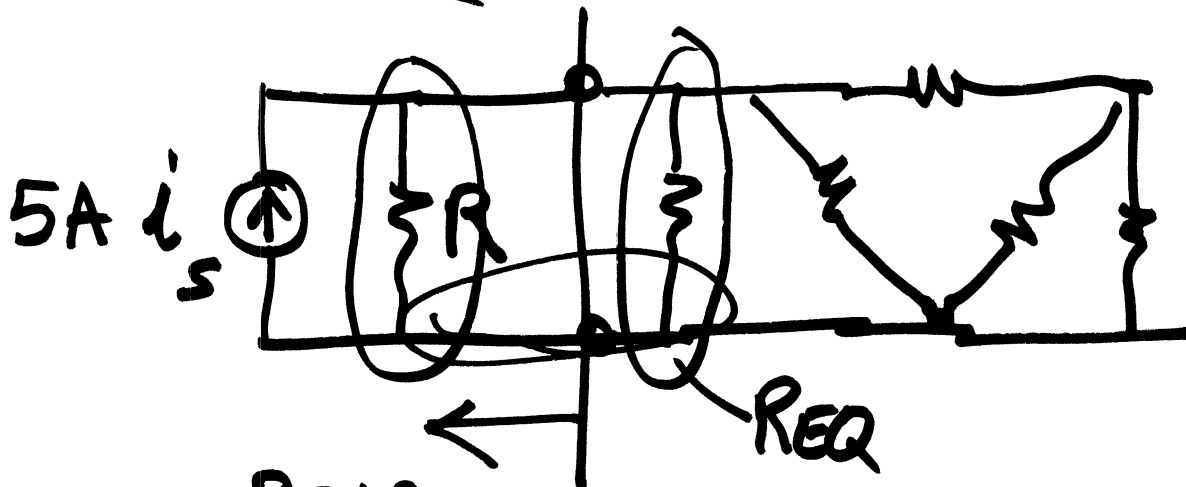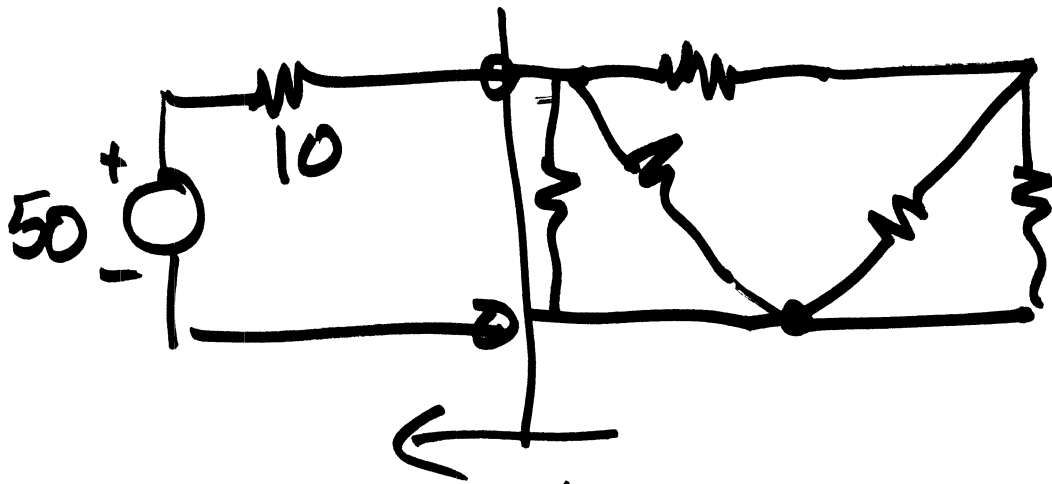

$$R = 10$$

$$i_s = \frac{U}{R} = \frac{50}{10} = 5A.$$

