

#1

$$v(t) = 100 - 200 \cos(\pi t) - 75 \sin(40000\pi t) + 35 \cos(80000\pi t) \text{ mV} \leftarrow \text{watch units}$$

a) $T_0 = ?$ $T_0 = \frac{1}{f_0} = \frac{1}{\omega/2\pi} = \frac{1}{\pi/2\pi} = 2$ $T_0 = 2s$ You can assume seconds, because $Hz = \frac{1}{s}$

b) Avg Value = ?

$V_{Avg} = DC \text{ Value} = 100mV$

c) Amp of fund?

$V = 200mV$

d) highest freq. ?

$$\omega = 80000\pi = 2\pi f$$

$f = 40kHz$

#2



$L = 25mH$
Voltage

$$v_L = L \frac{di_L}{dt}$$

derivative is slope.

$$\frac{\text{rise}}{\text{run}} = \frac{20mA}{5\mu s} = 4000$$


$$v_L(t) = (25m)(4k) = 100V$$

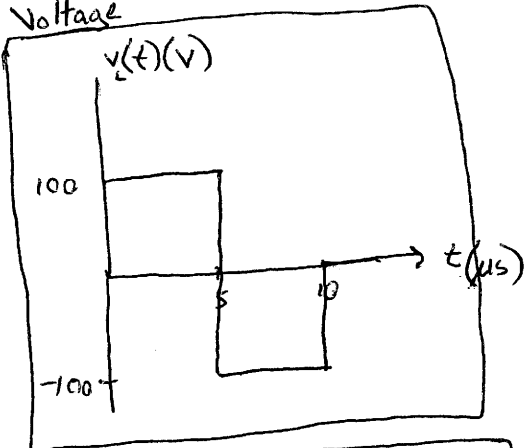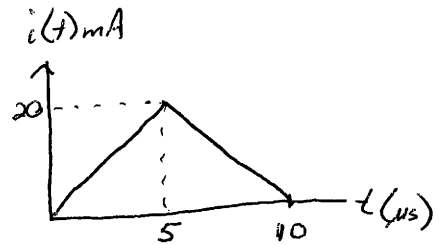

Energy


$$w_L(t) = \frac{1}{2} L i^2(t)$$

$$\frac{1}{2} (25m)(20m)^2 = 5\mu J$$

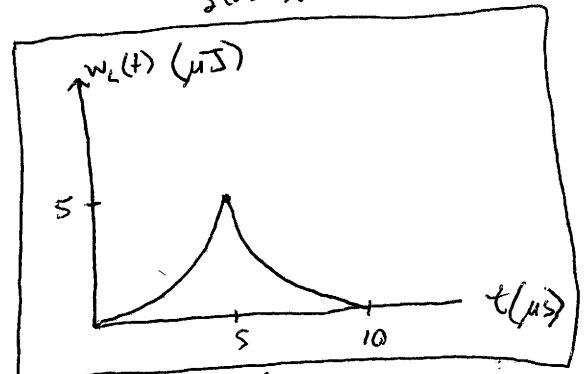

Parabolic ↗

$$P_L(t) = i_L(t) v_L(t) \text{ (W)}$$

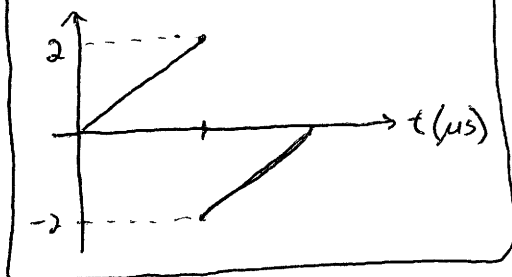

Power

← Multiply the $v(t)$ graph with the $i(t)$ graph.

#3

$$v_c(0) = 25V$$

$$v_c(t) = 50 - 25e^{-5000t}$$

$i_c = ?$

$P_c = ?$

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

$$= 10\mu F \frac{d}{dt} (50 - 25e^{-5000t})$$


$$= 10\mu F [125000 e^{-5000t}]$$

$$i_c(t) = 1.25 e^{-5000t} \text{ A}$$

$$P_c(t) = i_c(t)v_c(t) = [50 - 25e^{-5000t}] [1.25e^{-5000t}]$$

$$P_c(t) = 62.5 e^{-5000t} - 31.25 e^{-10000t}$$
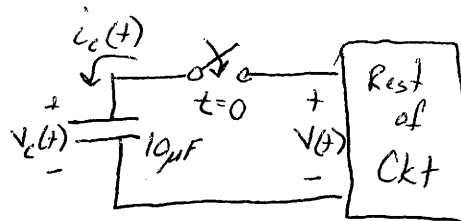
$$P_c(t) > 0 \text{ for } t > 0 \Rightarrow \text{Absorbing power}$$




#4

$$v_c(0) = 0$$

$$v_s(t) = 5 \sin \omega t \text{ u}(t)$$

KCL at V^-
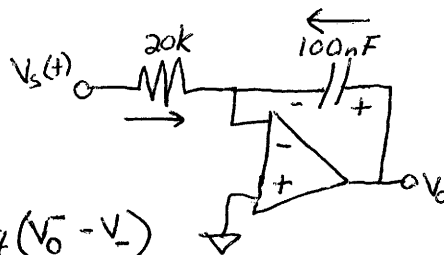
$$\frac{v_s(t) - V_-}{20k} = -i_c(t) = -C \frac{dv_c(t)}{dt} = -C \frac{d}{dt} (V_0 - V_-)$$



$$V_- = 0$$

$$\frac{v_s(t)}{20k} = -C \frac{dV_0}{dt}$$

$$V_0 = \frac{-1}{20k(100nF)} \int_0^t v_s(x) dx = \frac{-5}{20k(100nF)} \int_0^t \sin \omega t dt + V_c(0)$$

$$V_0(t) = \frac{-5}{20k(100nF)} \left[\frac{-1}{\omega} \cos \omega t \right]_0^t = \frac{-5}{20k(100nF)} \frac{1}{\omega} [-\cos \omega t + 1]$$

$$V_0(t) = \frac{-2500}{\omega} [1 - \cos(\omega t)]$$

OpAmp saturates at $\pm 15V$

$$-15 = \frac{-2500}{\omega} [1 - (-1)]$$


\leftarrow cos is max of ± 1

$$\omega = \frac{5000}{15} = 333 \frac{\text{rad}}{\text{s}}$$

when opamp enters saturation.
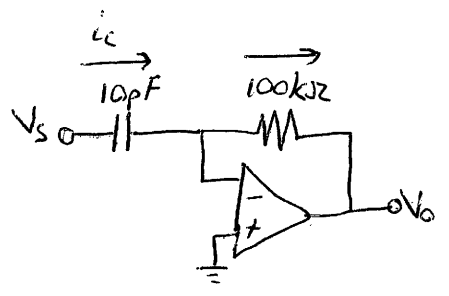
#5

$V_s(t) = 5 [e^{-\alpha t}] u(t)$ KCL at V^-
 $V^- = 0V$



$$10pF \frac{dV_s(t)}{dt} = \frac{-V_o}{100k}$$

$$V_o = -100k(10pF) \frac{dV_s(t)}{dt} = -1 \times 10^{-6} [-5\alpha e^{-\alpha t}] u(t)$$

$$V_o = 5 \times 10^{-6} \alpha e^{-\alpha t} u(t)$$

OpAmp saturates at $\pm 15V$

$15 = 5 \times 10^{-6} \alpha$ at $t=0$ exponential is a maximum (1)




$$\alpha = \frac{15}{5 \times 10^{-6}}$$

$$\alpha = 3 \times 10^6$$

When opamp enters saturation

#6

Capacitors in parallel add.

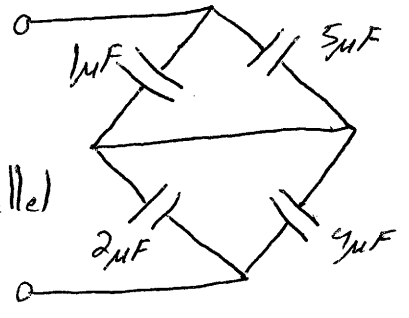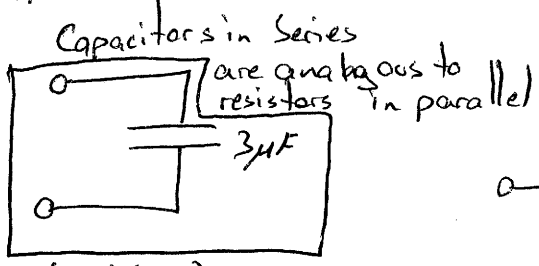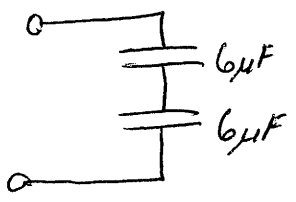

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow C_{eq} = \frac{(6\mu F)(6\mu F)}{6\mu F + 6\mu F} = 3\mu F$$

Inductors are reduced the same as resistors. [Series Add Parallel \rightarrow use formula]

