

#1 a)  $V_1 = 10 + j40$ ,  $\omega = 10$

change to polar form  $Ae^{j\theta}$

$$A = \sqrt{10^2 + 40^2} = 10\sqrt{17} = 41.23$$

$$\theta = \tan^{-1}\left(\frac{40}{10}\right) = 75.96^\circ$$

$$V_1 = 41.23 e^{j75.96^\circ}$$

$$\operatorname{Re}\{e^{j\theta}\} = \cos(\theta)$$

$$v_1(t) = \operatorname{Re}\{V_1 e^{j\omega t}\} = \boxed{41.23 \cos(10t + 75.96^\circ)}$$

b)  $V_2 = (8 - j3)5e^{-j60^\circ}$ ,  $\omega = 20$

change polar part ( $5e^{-j60^\circ}$ ) into rect ( $a + jb$ )

$$a = 5 \cos(-60^\circ) = 2.5$$

$$b = 5 \sin(-60^\circ) = -4.33$$

$$V_2 = (8 - j3)(2.5 - j4.33) = 7 - j42.14 = 42.7 e^{-j80.56^\circ}$$

$$v_2(t) = \operatorname{Re}\{V_2 e^{j\omega t}\} = \boxed{42.7 \cos(20t - 80.56^\circ)}$$

c)  $I_1 = 8 - j3 + \frac{3}{j}$ ,  $\omega = 300$

$$\frac{1}{j} = -j \quad I_1 = 8 - j3 - j3 = 8 - j6 \quad \text{put into polar form.}$$

$$I_1 = 10 e^{-j36.87^\circ}$$

$$i_1(t) = \operatorname{Re}\{I_1 e^{j\omega t}\} = \operatorname{Re}\{10 e^{-j36.87^\circ} e^{j300t}\} = \operatorname{Re}\{10 e^{j(300t - 36.87^\circ)}\}$$

$$\boxed{i_1(t) = 10 \cos(300t - 36.87^\circ)}$$

d)  $I_2 = \frac{3+j}{1-3j}$ ,  $\omega = 50$

We want this in the form  $a + jb$  so multiply top and bottom by complex conjugate of denominator.

$$I_2 = \frac{3+j}{1-3j} \frac{(1+3j)}{(1+3j)} = \frac{3+9j-3+j}{1+9} = j \rightarrow 1e^{j90^\circ}$$

$$i_2(t) = \operatorname{Re}\{I_2 e^{j\omega t}\} = \operatorname{Re}\{e^{j90^\circ} e^{j50t}\}$$

$$\boxed{i_2(t) = \cos(50t + 90^\circ) = -\sin(50t)}$$

#2  $v_1(t) = 50 \cos(\omega t - 45^\circ) = \text{Re} \{ 50 e^{j45^\circ} e^{j\omega t} \} \rightarrow V_1 = 50 e^{-j45^\circ}$   
 $v_2(t) = 25 \sin(\omega t) = 25 \cos(\omega t - 90^\circ) = \text{Re} \{ 25 e^{j90^\circ} e^{j\omega t} \} \rightarrow V_2 = 25 e^{-j90^\circ}$   
 $v_3(t) = ? \quad v_1 + v_2 + v_3 = 0$

Put  $v_1(t)$  and  $v_2(t)$  into Phasors,

$V_3 = -V_1 - V_2$  Phasors add (or subtract) as long as  $\omega$  is the same for each function.

$V_3 = -50 e^{-j45^\circ} - 25 e^{-j90^\circ}$   
 $= (-35.36 + j35.36) + (0 + j25)$

← You can do this in your calc, but hard to do by hand. To do by hand, put into rect. form.

$V_3 = (-35.36 + 60.36)$

← Add real parts and add imag. parts.

$V_3 = 69.95 e^{j120.36^\circ}$


← Put in Polar form

$v_3(t) = \text{Re} \{ V_3 e^{j\omega t} \}$

← Return the phasor to the time domain


$v_3(t) = 69.95 \cos(\omega t + 120.36^\circ)$

#3

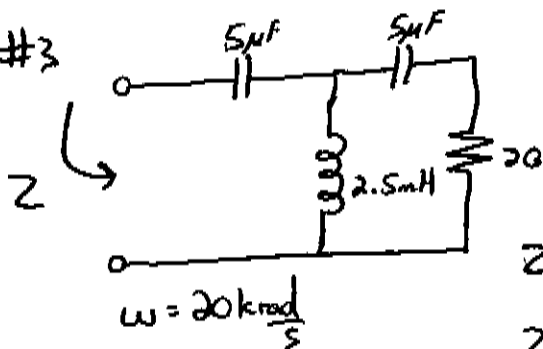

Make everything impedance

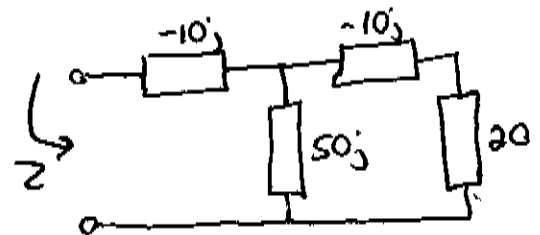$Z_C = \frac{1}{j\omega C} = -10j$   
 $Z_L = j\omega L = 50j$



Impedances act like resistors so combine the devices (series or parallel) as if they were resistors.


$Z = -10j + 50j \parallel (-10j + 20) = -10j + \frac{50j(20 + j(-10))}{50j + (20 - j10)} = -10j + \frac{500 + j1000(20 - 40)}{20 + 40j(20 - 40)}$   
 $= -10j + \frac{50000}{2000} = -10j + 25$   
 $Z = 25 - j10 \Omega$

$$\#4 \quad i(t) = 300 \cos(2000t) \text{ mA} \quad \omega = 2000$$


$$= 0.3 \cos(2000t) \text{ A}$$

$$I = 0.3 e^{j0} = 0.3 \text{ A} \leftarrow \text{phasor of input}$$

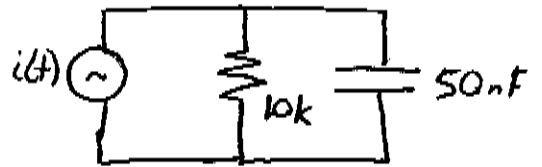Since impedance acts like resistors you can do a current divider to find  $i_R(t)$  and  $i_C(t)$



↓ change into impedance

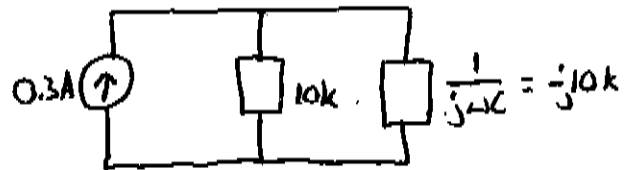

$$I_R = \frac{-j10k}{-j10k + 10k} (0.3) = (0.15 - j0.15) \text{ A}$$

$$= 0.212 e^{-j45^\circ} \text{ A}$$

phasor of  $i_R(t)$


$$i_R(t) = \text{Re} \{ I_R e^{j\omega t} \} = \boxed{0.212 \cos(2000t - 45^\circ) \text{ A}}$$


$$I_C = \frac{10k}{10k - j10k} (0.3) = (0.15 + j0.15) \text{ A} = 0.212 e^{j45^\circ} \text{ A}$$

$$i_C(t) = \text{Re} \{ I_C e^{j\omega t} \} = \boxed{0.212 \cos(2000t + 45^\circ) \text{ A}}$$

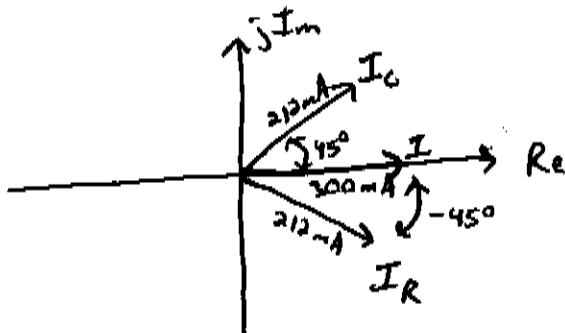
### Phasor Diagram

Plot  $I$ ,  $I_R$  and  $I_C$  on the complex plane



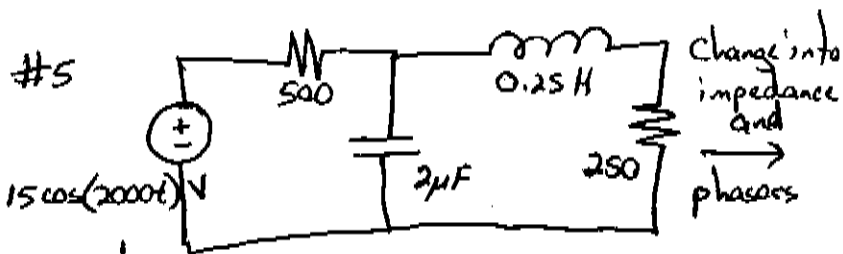

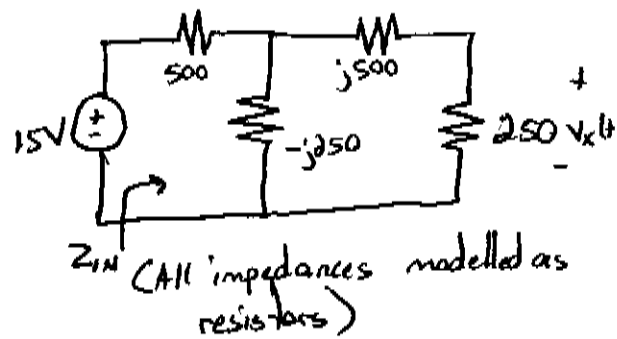$\omega = 2000$   
 $Z_C = \frac{1}{j\omega C} = -j250$   
 $Z_L = j\omega L = j500$




To find  $Z_{IN}$ , find the  $Z_{eq}$  of all ~~resistor~~ impedances.

$$Z_{IN} = 500 + (-j250) \parallel (250 + j500) = 500 + \frac{(-j250)(250 + j500)}{-j250 + (250 + j500)}$$

$Z_{IN} = 625 - j375 \Omega$

To find  $v_x(t)$  we first should find  $V_x$  (phasor)

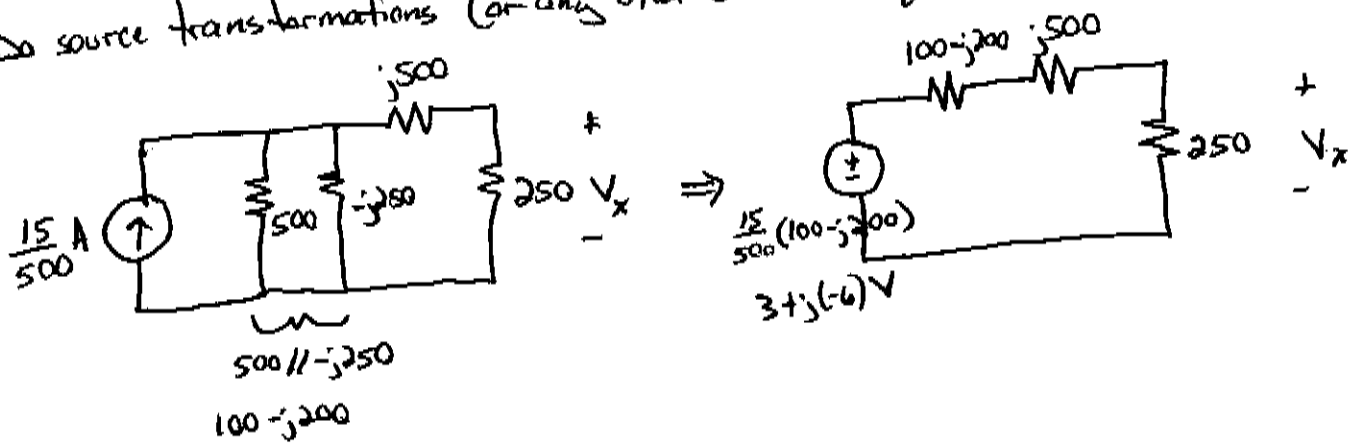Do source transformations (or any other ckt technique we've learned)




Use a Voltage Divider:

$$V_x = \frac{250}{250 + j500 + (100 - j200)} (3 - j6) = -0.88 - j3.53 \text{ V} = 3.64 e^{-j104^\circ} \text{ V}$$

$v_x(t) = \text{Re} \{ V_x e^{j\omega t} \} = 3.64 \cos(2000t - 104^\circ) \text{ V}$

Transform back into time domain

#6

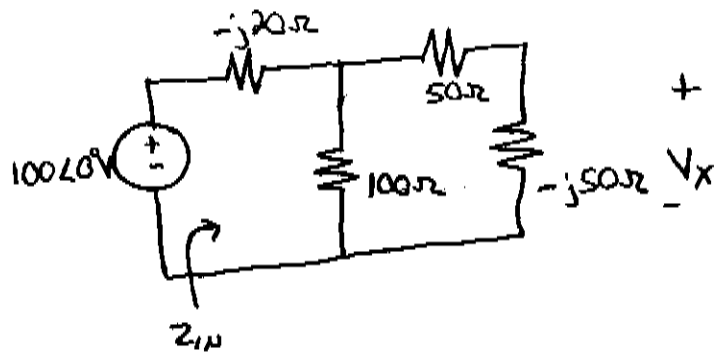


circuit is already in impedance and phasor form.

$$Z_{IN} = -j20 + 100 \parallel (50 - j50) = -j20 + \frac{100(50 - j50)}{100 + 50 - j50}$$

$$Z_{IN} = 40 - j40 \Omega$$

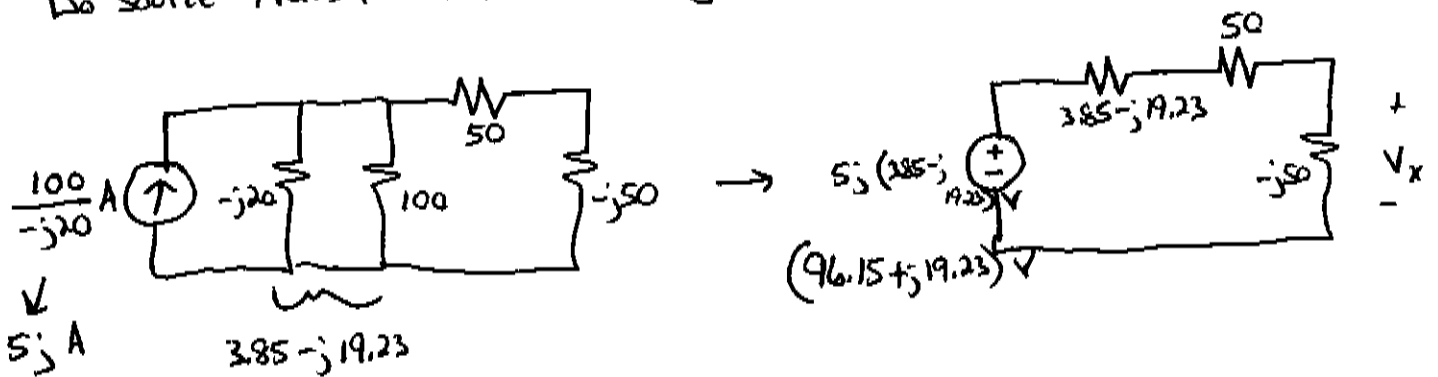Do Source Transformations and Voltage divider again.



$$V_x = \frac{-j50}{-j50 + 50 + (3.85 - j19.23)} (96.15 + j19.23) \text{ V}$$

$$V_x = 50 - j25 \text{ V} \quad \text{or} \quad 55.9 e^{-j26.6^\circ} \text{ V}$$