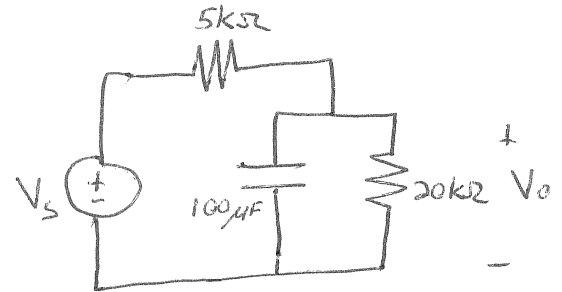


#1 a)  $T(j\omega) = \frac{V_o(j\omega)}{V_s(j\omega)} = ?$


Voltage Divider:  $V_o = V_s \frac{20k \parallel \frac{1}{j\omega(100\mu F)}}{\left[20k \parallel \frac{1}{j\omega(100\mu F)}\right] + 5k}$



$$T(j\omega) = \frac{\frac{20k}{1+j2\omega}}{\frac{20k}{1+j2\omega} + 5k} = \frac{20k}{25k + j(10k)\omega} = \frac{0.8}{1 + j\frac{\omega}{2.5}}$$

$$\boxed{\frac{0.8}{1 + j\frac{\omega}{2.5}}}$$

$x_{dB} = 20 \log x$

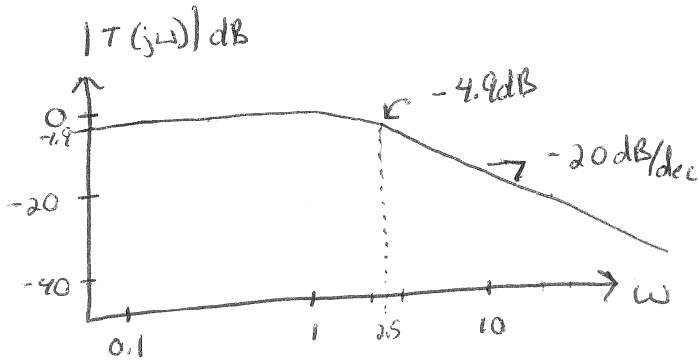


At  $\omega = 0$   $|T(j\omega)| = 0.8 \rightarrow -1.9 \text{ dB}$

$\omega_c = \frac{5}{2} \frac{\text{rad}}{\text{s}} = 2.5$  (when denom =  $1+j$ )
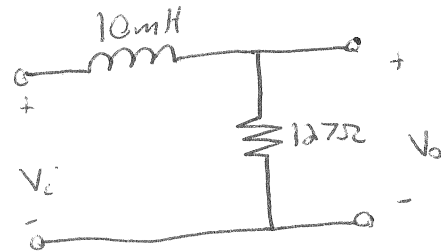
#2 Voltage Divider:

$$T(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{127}{127 + j\omega(10m)} = \boxed{\frac{1}{1 + j\omega(7.87 \times 10^{-5})}}$$



a)  $f_c = ? = \frac{\omega_c}{2\pi}$  ~~1 + j\omega\_c(7.87 \times 10^{-5}) = 1 + j~~

$\omega_c = \frac{1}{7.87 \times 10^{-5}} = 12.7k \frac{\text{rad}}{\text{s}}$

$f_c = 2021 \text{ Hz}$

Low-Pass

(when  $\omega = 0$   $|T(j\omega)| > 0$ ; when  $\omega \rightarrow \infty$   $|T(j\omega)| \rightarrow 0$ )

b)  $T(j(0.2\omega_c)) = (0.96 - j0.192) = 0.98 e^{-j11.3^\circ}$   
 $T(j\omega_c) = (0.5 - j0.5) = 0.707 e^{-j45^\circ}$   
 $T(j(5\omega_c)) = (0.038 - j0.192) = 0.196 e^{-j78.7^\circ}$

#2 cont...

e)  $v_i = 10 \cos(\omega t)$

$\omega = 0.2\omega_c$

$V_o = T(j\omega) v_i(j\omega) = 9.8 \cos(\omega t - 11.3^\circ)$

$\omega = \omega_c$

$V_o(t) = 7.07 \cos(\omega t - 45^\circ)$

$\omega = 5\omega_c$

$V_o(t) = 1.96 \cos(\omega t - 78.7^\circ)$

#3



$T(j\omega) = ?$

Inverting Amp:  $V_o = \frac{-Z_F}{Z_{in}} V_{in}$

$T(j\omega) = \frac{V_o}{V_i} = \frac{-(100k \parallel \frac{1}{j\omega 5n})}{10k} = \frac{-100k}{1 + j\omega (5 \times 10^{-4})}$

$T(j\omega) = \frac{-10}{1 + j\omega (5 \times 10^{-4})}$

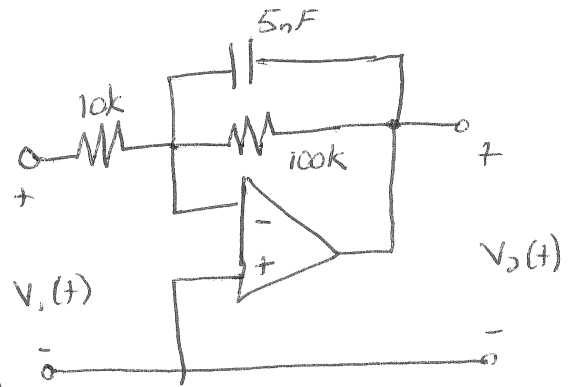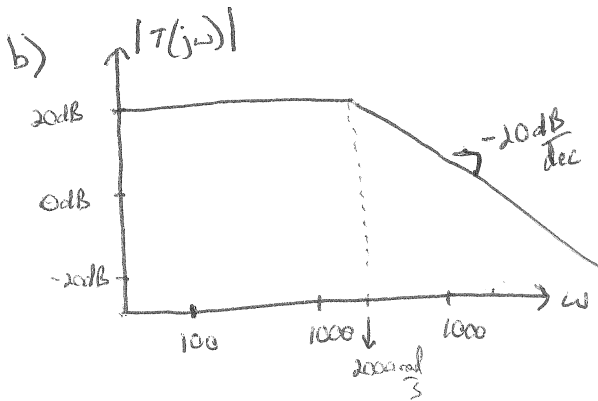a) DC gain:  $-10$  ( $\omega=0$ )  
 $\omega_c = 2000 \frac{\text{rad}}{\text{s}} = 318 \text{ Hz}$   
 Low pass



e)  $V_o = T(j\omega) V_i$

$\omega = 0.5\omega_c$

$V_{o, \text{Amp}} = 50$

$\omega = \omega_c$

$V_{o, \text{Amp}} = 50$


$\omega = 2\omega_c$

$V_{o, \text{Amp}} = 25$

#4 Find transfer function  $T(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$

$$T(j\omega) = \frac{V_o}{V_A} \cdot \frac{V_A}{V_i} = \frac{10k}{10k + \frac{1}{j\omega(0.1\mu)}} \cdot \left(1 + \frac{60k}{20k}\right)$$


Voltage Divider
Non-inverting Amp.

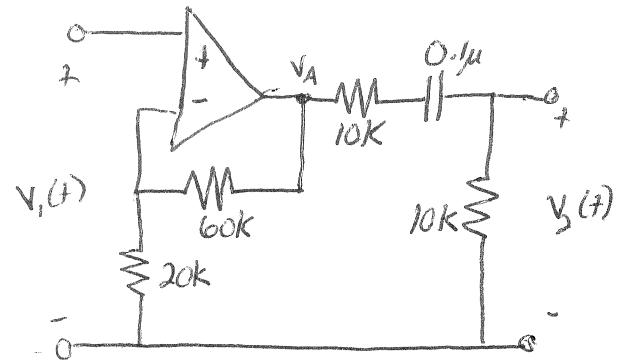

$$T(j\omega) = \frac{40k(j\omega(0.1\mu))}{1 + j\omega(10k)(0.1\mu)} = \frac{j\omega(2)}{j\omega + 500} = \frac{j\omega(4m)}{1 + j\omega(2m)}$$

- a) DC gain ( $\omega=0$ ): 0  
 $f_\infty$  gain: 2  
 $\omega_c: 500 \frac{\text{rad}}{\text{s}} = 79.6 \text{ Hz}$

b) High pass ( $|T(j\omega)| = 0$  @ low freq. and is flat at high freq.)

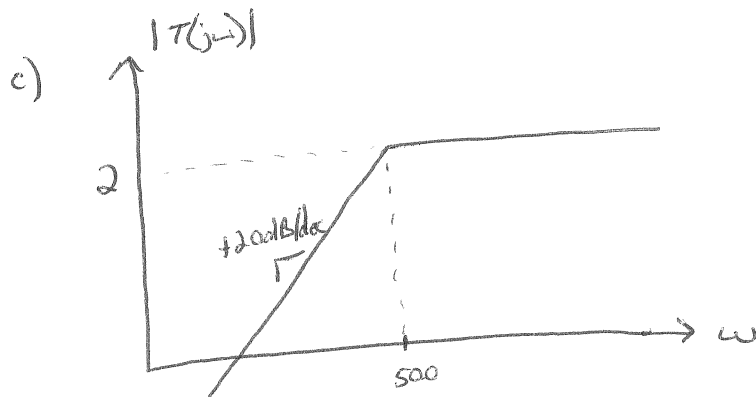


#5

$$T(j\omega) = \frac{10}{10^2 + \frac{j\omega}{20}} = \frac{\frac{1}{10}}{1 + \frac{j\omega}{2000}}$$

a) Low pass  
 $\omega_c = 2000 \frac{\text{rad}}{\text{s}} = 318 \text{ Hz}$   
Passband Gain:  $\frac{1}{10}$

$\omega = 0$  for low pass passband

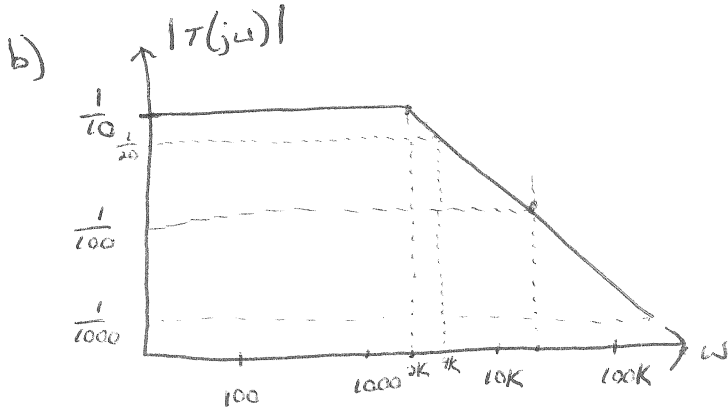

c)  $|T(j(0.5\omega_c))| = \frac{1}{10}$

$$|T(j\omega_c)| = \frac{1}{10}$$

$$|T(j(2\omega_c))| = \frac{1}{20}$$