

3-24Assume $V_0 = 1V$

$$i_0 = \frac{1V}{2k} = \frac{1}{2} \text{ mA}$$

$$i_0 = i_1 = \frac{1}{2} \text{ mA}$$

$$V_1 = i_1(1k) = \frac{1}{2} \text{ V}$$

$$V_2 = V_B = V_1 + V_0 = \frac{3}{2} \text{ V} \quad i_2 = \frac{V_B}{4k} = \frac{3/2 \text{ V}}{4k} = \frac{3}{8} \text{ mA}$$

$$\text{KCL @ B} \quad i_3 = i_2 + i_1 = \frac{3}{8} + \frac{1}{2} = \frac{7}{8} \text{ mA} \quad V_3 = \left(\frac{7}{8} \text{ mA}\right)(1k) = \frac{7}{8} \text{ V}$$

$$V_4 = V_3 + V_2 = \frac{7}{8} + \frac{3}{2} = \frac{19}{8} \text{ V} \quad i_4 = \frac{V_4}{8k} = \frac{19}{64} \text{ mA}$$


$$\text{KCL @ A} \quad i_5 = i_4 + i_3 = \frac{19}{64} + \frac{7}{8} = \frac{75}{64} \text{ mA} \quad V_5 = \left(\frac{75}{64} \text{ mA}\right)(1k) = \frac{75}{64} \text{ V}$$

$$V_{in} = V_5 + V_4 = \frac{75}{64} + \frac{19}{8} = \frac{227}{64} \text{ V}$$




$$K = \frac{V_0}{V_{in}} = \frac{1}{227/64} = 64/227$$

$$V_0 = \left(\frac{64}{227}\right) 10V = \frac{640}{227} \text{ V}$$

$$\boxed{V_0 = 2.82V} \quad 2$$

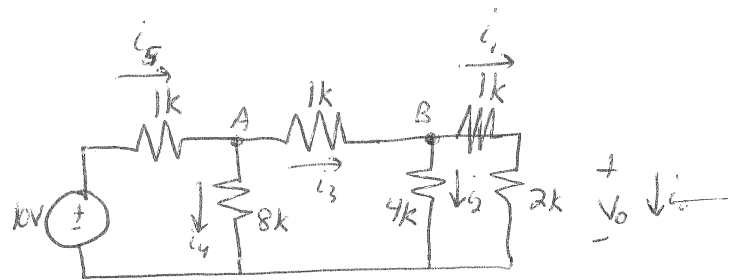


3-29 ① i_s ON

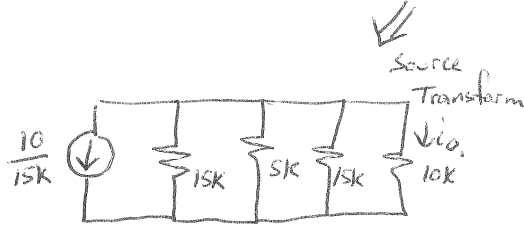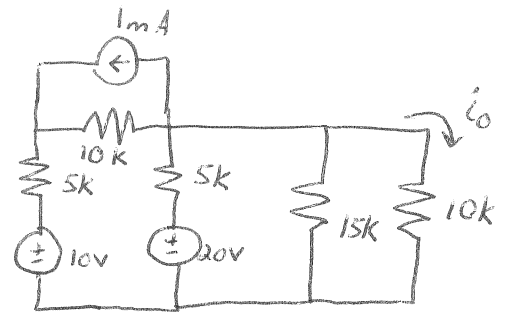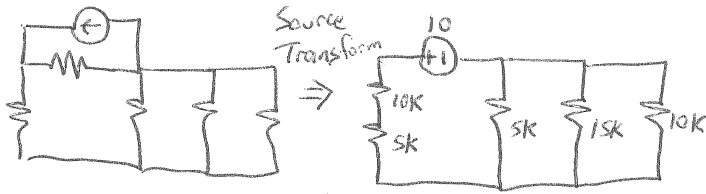

Current Divider

$$i_{0_1} = \frac{\frac{1}{10k}}{\frac{1}{10k} + \frac{1}{5k} + \frac{1}{5k} + \frac{1}{15k}} \left(\frac{-10}{15k} \right) = -0.1538 \text{ mA} \quad +1$$


② 10V source ON

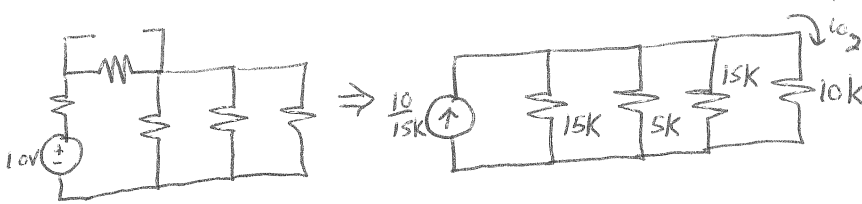

$$i_{0_2} = \frac{\frac{1}{10k}}{\frac{1}{10k} + \frac{1}{5k} + \frac{1}{5k} + \frac{1}{15k}} \left(\frac{10}{15k} \right) \quad +1$$

$$i_{0_2} = 0.1538 \text{ mA}$$

③ 20V source ON

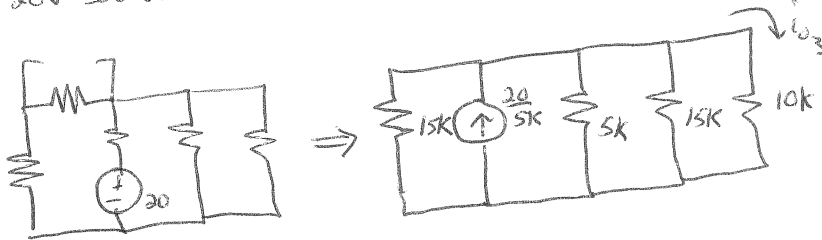


$$i_{0_3} = \frac{\frac{1}{10k}}{\frac{1}{10k} + \frac{1}{15k} + \frac{1}{5k} + \frac{1}{15k}} \left(\frac{20}{5k} \right) \quad +1$$

$$i_{0_3} = 0.923 \text{ mA}$$


$$i_0 = \sum i_{0_j} = i_{0_1} + i_{0_2} + i_{0_3} = i_{0_3} =$$

$$i_0 = 0.923 \text{ mA} \quad +2$$

3-31

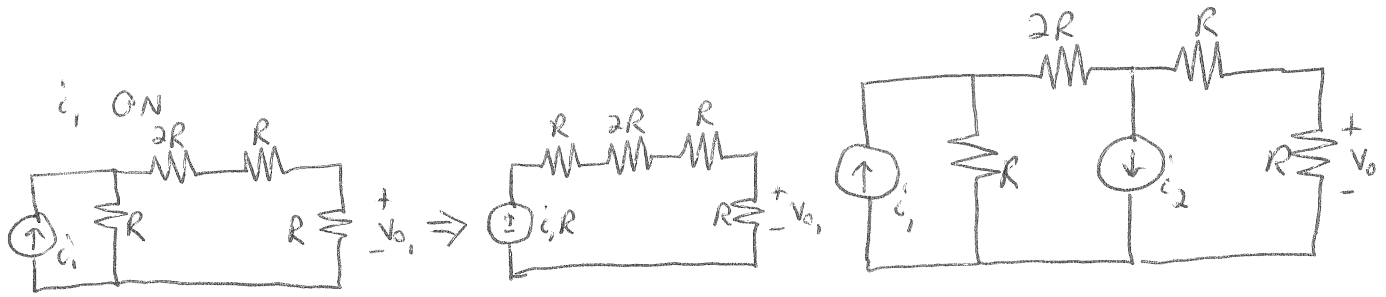
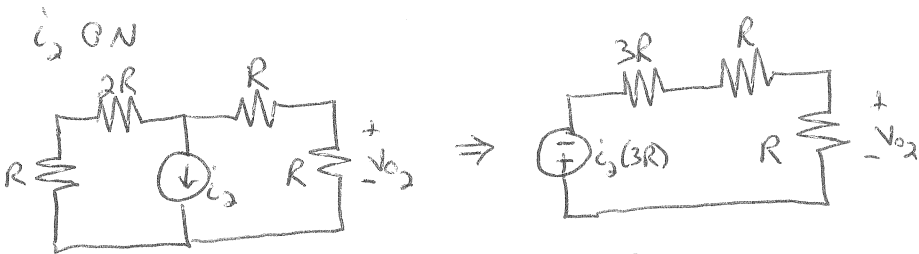
$$V_{0_1} = \frac{R}{R+R+2R+R} (i_1 R) = \frac{i_1 R}{5} + 2$$



$$V_{0_2} = \frac{R}{R+2R+R} (i_2 (3R)) = -\frac{3i_2 R}{5} + 2$$

$$V_0 = \sum V_{0_i} = V_{0_1} + V_{0_2} \quad \boxed{V_0 = \frac{i_1 R}{5} - \frac{3i_2 R}{5} + 1}$$

#4

Find V_{Th} , R_{Th}



and i_x

$$V_{oc} = V_T = ?$$

$$V_{oc} = V_A - V_B = \frac{10}{10+10} (20) - 10$$

$$V_{oc} = V_T = 0$$
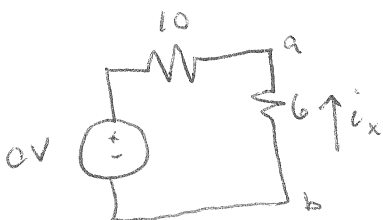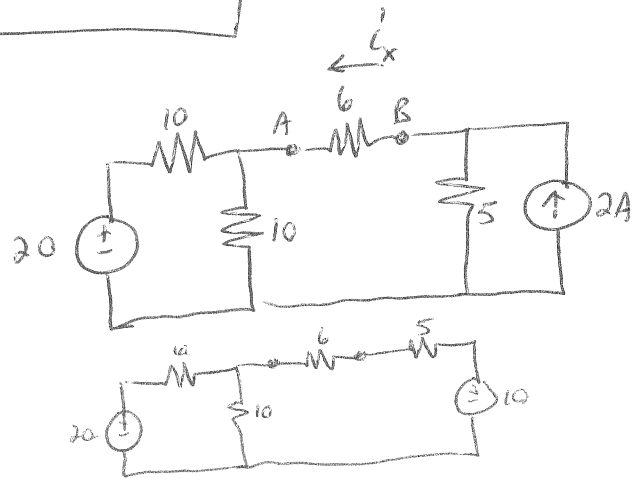
$$R_{LB} = 10//10 + 5 = 10 \Omega = R_T$$




$$\text{KVL } 0 + (-i_x)10 - i_x(6) = 0$$

$$\boxed{i_x = 0}$$

3 points for work

* This is a silly problem if you got that $V_T = 0$ and $i_x = 0$ then you will receive full credit

#5
Find i using Norton

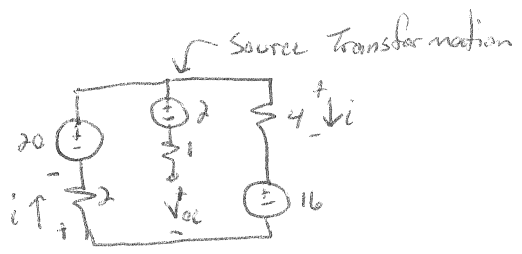

KVL around outside

$$2(i) - 20 + 4i + 16 = 0$$

$$6i = 4$$


$$i = 2/3$$

KVL around left loop

$$2i - 20 + 2 + V_{oc} = 0$$

$$V_{oc} = 18 - \frac{4}{3} = \frac{50}{3} = 16.67V$$

$R_{LB} = R_N = ?$ Turn off sources

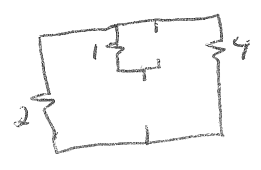


$$R_{LB} = 1 + 2 // 4$$

$$R_{LB} = 7/3 = 2.33\Omega$$

2 work
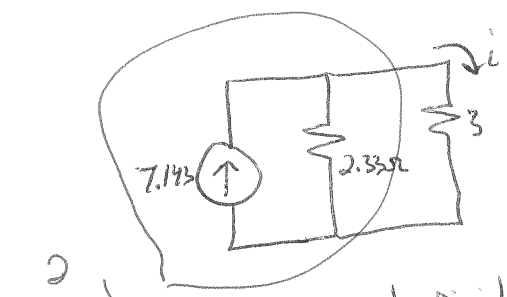
$$I_{sc} = \frac{V_{th}}{R_{LB}} = \frac{50/3}{7/3} = \frac{50}{7} = 7.143A$$




for Norton Equivalent



Current Divider

$$i = \frac{\frac{1}{3}}{\frac{1}{3} + \frac{1}{2.33}} (7.143)$$


$$i = 3.125A \quad +1$$

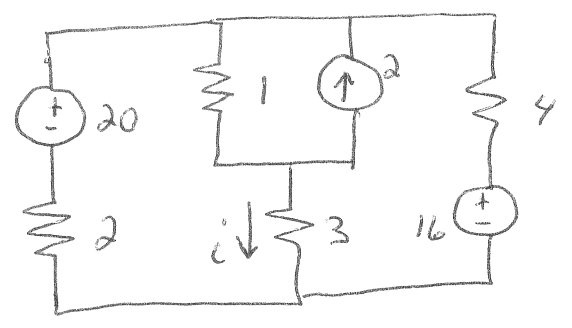


Another Way

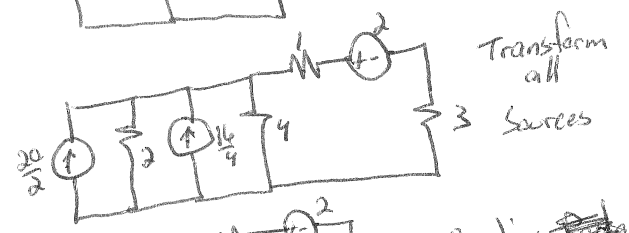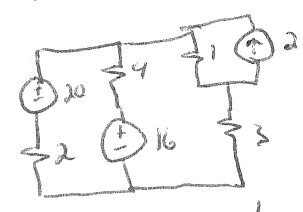

Transform all sources

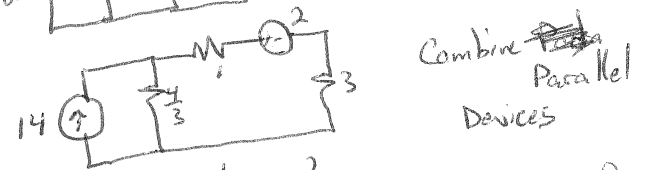


Combine Parallel Devices

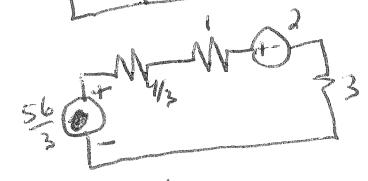

Source Transformation



Combine Series thevenin Equivalent

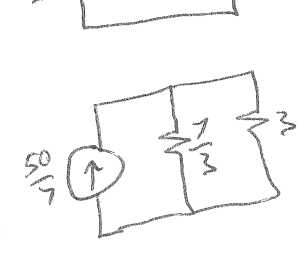



Source Transformation
← Norton Equiv.

Same. →
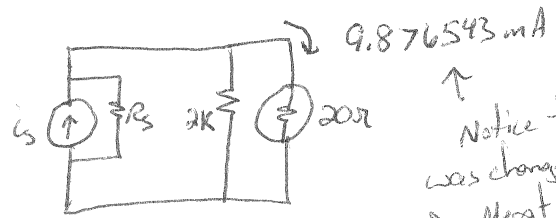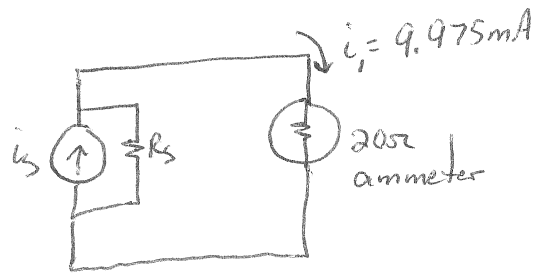
#6 Current Divider

① $\frac{\frac{1}{20}}{\frac{1}{20} + \frac{1}{R_s}} i_s = i_1 = 9.975 \text{ mA}$

② $\frac{\frac{1}{20}}{\frac{1}{20} + \frac{1}{2k} + \frac{1}{R_s}} i_s = 9.876543 \text{ mA}$



↑ Notice this was changed by Dr. Merat so the problem makes sense.

$\frac{R_s}{20 + R_s} i_s = 9.975 \text{ mA}$

1a) $i_s R_s = 199.5 \text{ mA} + 9.975 \text{ mA}(R_s)$

$\frac{2k R_s}{2k + R_s} i_s = 9.876543 \text{ mA}$
 $\frac{2k R}{2k + R} + 20$

2 work

$\frac{2k R_s i_s}{2k R_s + 40k + 20 R_s} = 9.876543 \text{ mA}$

2a) $2k R_s i_s = 19.753086 R_s + 395.06172 + 0.19753086 R_s = 395.06172 + 19.95061686 R_s$

Must keep lots of digits

1b) $2k R_s i_s = 399 + 19.95 R_s \quad (1a \times 2k)$

1b-2a) $0 = 3.93828 - 6.1686 \times 10^{-4} R_s$


$R_s = 6384 \Omega$

← This value can vary depending on how many digits were rounded above

$\frac{R_s}{20 + R_s} i_s = 9.975 \text{ mA}$
 $i_s = \frac{9.975 \text{ mA} (20 + 6384)}{6384}$

$i_s = 10 \text{ mA}$

part b

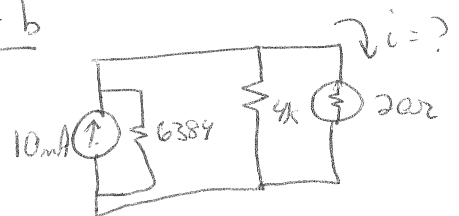

$i = \frac{\frac{1}{20}}{\frac{1}{20} + \frac{1}{4k} + \frac{1}{6384}} (10 \text{ mA})$

$i = 9.919 \text{ mA}$