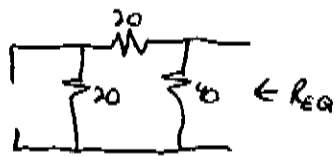


#1 a) Find  $R_L$  for max power

Max Power when  $R_L = R_N = R_T$


Find  $R_N$ :



$$R_N = 40 \parallel (20+20)$$

$$R_N = R_L = 20 \Omega$$


Find  $I_N$ :

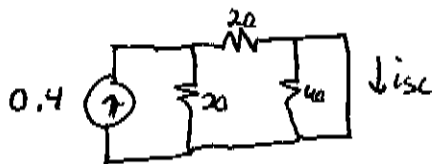

$$I_N = i_{sc} = \left( \frac{20}{20+20} \right) (0.4)$$


$$i_N = 0.2 \text{ A}$$

Find  $P_{max}$ :

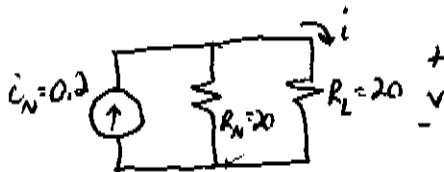

$$P = i v = i^2 R_L = \left[ \left( \frac{20}{20+20} \right) (0.2) \right]^2 (20)$$


$$P_{max} = 0.2 \text{ W}$$

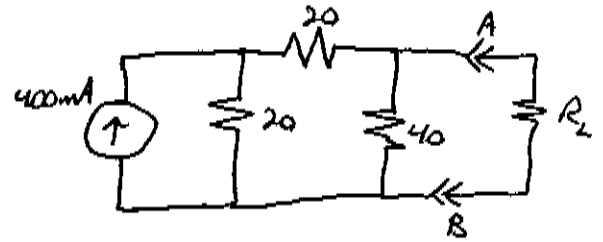

b) Find  $R_L$  for max voltage

Max Voltage when  $R_L = \text{Open ckt}$

$$R_L = \infty$$

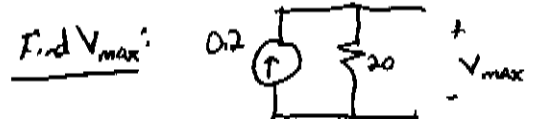


$$V_{max} = i_N R_N = (0.2)(20)$$

$$V_{max} = 4 \text{ V}$$

c) Find  $R_L$  for max current

Max Current when  $R_L = 0$  short ckt

$$R_L = 0 \Omega$$

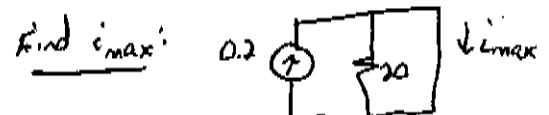


$$i_{max} = i_N = 0.2 \text{ A}$$

#2


To find  $R_L$  and  $P_{max}$ , first find Thevenin Eq.

$$R_T = R_{LB}$$

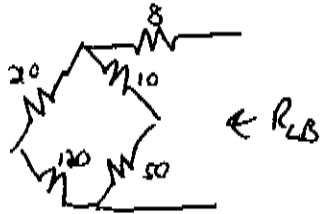

$$R_T = 8 + (140 // 60)$$
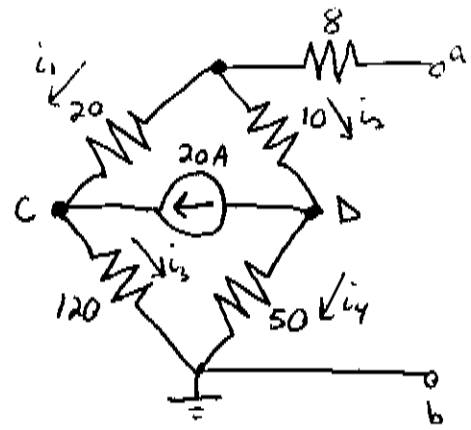
$$\boxed{R_T = 50 \Omega = R_L} \text{ for max power}$$



$V_T = V_{oc}$  Use Node Voltage (or some other technique)

$$V_a = V_{oc}$$

$$\textcircled{1} \frac{V_a - V_c}{20} + \frac{V_a - V_D}{10} = 0$$

$$\underline{3V_a - V_c - 2V_D = 0}$$

$$\textcircled{2} \frac{V_a - V_c}{20} + 20 = \frac{V_c}{120}$$

$$\underline{6V_a - 7V_c = -20(120)}$$

$$\textcircled{3} \frac{V_a - V_D}{10} = 20 + \frac{V_D}{50}$$

$$\underline{5V_a - 6V_D = 20(50)}$$

Put into calculator to solve


$$V_a = 20$$

$$V_c = 360$$

$$V_D = -150$$

$$\underline{V_{oc} = V_T = 20V}$$

Thevenin Equiv.

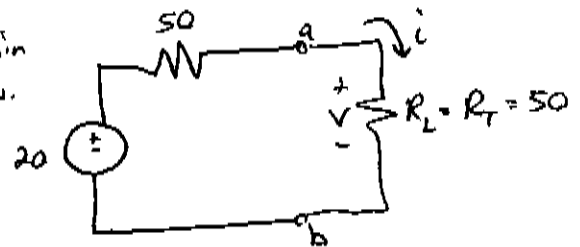



$$P_{max} = iV = \frac{V^2}{R} = \frac{\left(\frac{50}{50+50}\right)(20)^2}{50}$$

$$\boxed{P_{max} = 2W}$$


#3

$P_{max} = 1mW$

Reduce Ckt on left of interface

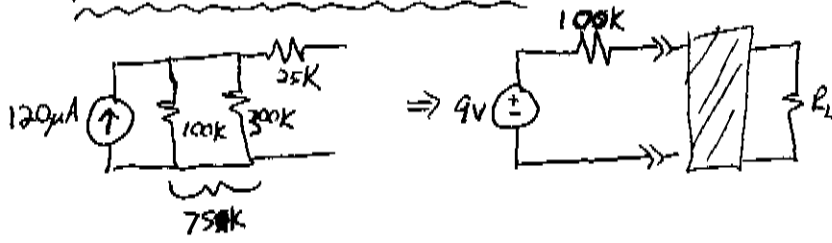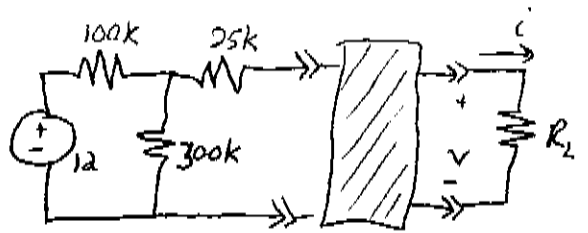

What is  $P_{max}$  from source?

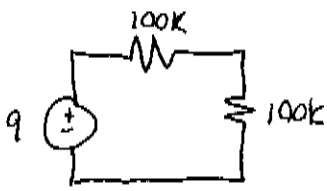

$$P_{max} = \frac{\left(\frac{9}{2}\right)^2}{100k} = 0.2025mW$$

Max Power is already less than 1mW

No interface ckt is necessary

Inserting an interface ckt and calculating values would show the same result.

#4

a)  $v_2 = ?$   $\frac{i_2}{i_1} = ?$   $V_s = 10mV$   $R_F = 10k\Omega$

KCL @ A  $\frac{V_s - V_x}{1k} = \frac{V_x - V_2}{R_F}$

$V_2 = -99V_x$

$\frac{V_s - V_x}{1k} = \frac{V_x - (-99V_x)}{R_F}$


$10V_s - 10V_x = 100V_x$

$V_x = \frac{10}{110} V_s = \frac{10}{110} (10mV) = 909\mu V$

$V_2 = -99V_x = -90mV$

$\frac{i_2}{i_1} = \frac{\frac{V_2}{1k}}{\frac{V_s - V_x}{1k}} = \frac{V_2}{V_s - V_x} = \frac{-90mV}{10mV - 909\mu V}$

$\frac{i_2}{i_1} = -9.9$

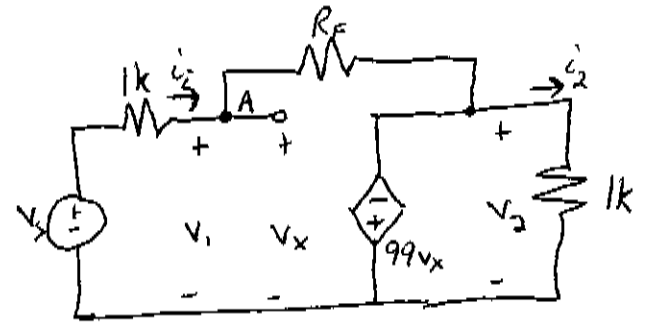

b)  $R_{in} = ? = V_1 / i_1$

$\frac{V_1}{i_1} = \frac{V_1}{\frac{V_s - V_1}{1k}} = \frac{V_x (1k)}{V_s - V_x}$

$R_{in} = \frac{(909\mu V)(1k)}{10mV - 909\mu V}$

$R_{in} = 100\Omega$

#5

$$i_o/i_s = ?$$


KCL @ A:  $i_s = \frac{V_o}{R_s} + i_x = \frac{i_o R_o}{R_s} + i_x$

$$r i_x = V_o = i_o R_o$$

$$i_x = \frac{i_o R_o}{r}$$

$$i_s = \frac{i_o R_o}{R_s} + \frac{i_o R_o}{r}$$
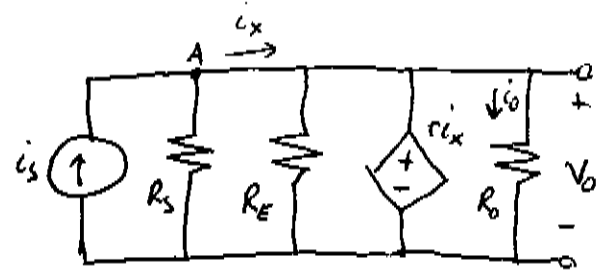
$$\frac{i_o}{i_s} = \frac{r R_s}{R_o(r + R_s)}$$



#6


a) Use Mesh Currents, find  $V_c$  and  $i_x$

$$i_1 - i_3 = 9A$$

$$2V_y = i_4 - i_3 = 4i_1 - 4i_2$$

$$i_4 = -i_x$$

$$V_y = 2(i_1 - i_2)$$

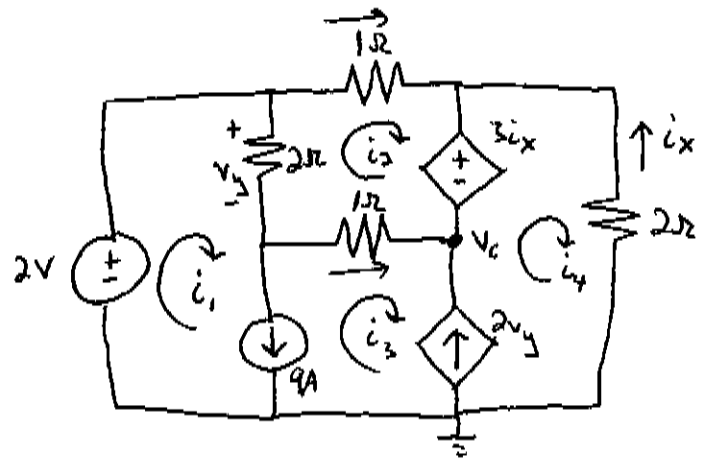

$$(i_2 - i_3)(1) + (2)(i_2 - i_1) + i_3(1) + 3i_x = 0 \quad \text{KVL around top middle loop}$$

$$-2 + (1)i_2 + 2i_4 = 0 \quad \text{KVL around outside loop}$$

①  $i_1 - i_3 = 9$

②  $4i_1 - 4i_2 + i_3 - i_4 = 0$

③  $-2i_1 + 4i_2 - i_3 - 3i_4 = 0$

④  $i_2 + 2i_4 = 2$

} Put into calculator to solve

$$i_1 = 2A$$

$$i_2 = 0$$

$$i_3 = -7$$

$$i_4 = 1$$

$$i_x = -i_4 = -1A$$

$$V_c = -3i_x - 2i_x \quad (\text{KVL around right loop})$$

$$V_c = 5V$$


#6

b) Use Node Voltage, to find  $V_c$  and  $i_x$

$$V_A = 2V$$

$$V_y = V_A - V_B$$

$$i_x = \frac{-V_D}{2}$$

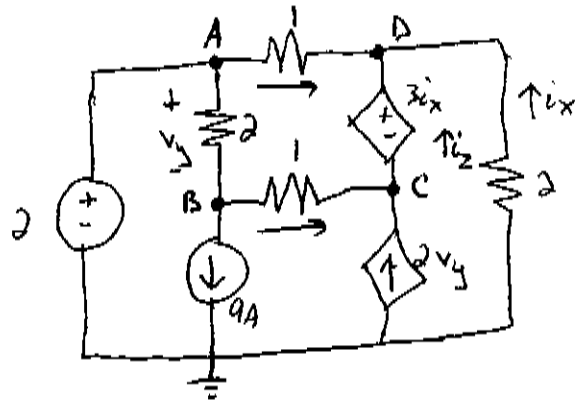

KCL @ B:  $\frac{V_A - V_B}{2} = 9 + \frac{V_B - V_C}{1} = \frac{2 - V_B}{2}$

KCL @ C:  $\frac{V_B - V_C}{1} + 2(V_A - V_B) = i_2$

KCL @ D:  $i_2 + \frac{V_A - V_D}{1} + i_x = 0$

$$i_2 = \frac{3V_D}{2} - V_A = \frac{3V_D}{2} - 2$$

KVL around right loop:  $V_C + 3i_x = V_D = V_C - \frac{2V_D}{2}$

$$V_C = \frac{5V_D}{2}$$

$$\textcircled{1} -\frac{3}{2}V_B + V_C = 8$$

$$\textcircled{2} -V_B - V_C - \frac{3}{2}V_D = -6$$

$$\textcircled{3} V_C - \frac{5}{2}V_D = 0$$

Put into calc to solve

$$\boxed{\begin{matrix} V_B = -2V \\ V_C = 5V \\ V_D = 2V \end{matrix}}$$

$$\boxed{i_x = \frac{-V_D}{2} = -1A}$$