

#1 Find Norton Equivalent

Find V_{oc} : $i = 0$

$$\text{KCL @ X} \quad \frac{1}{3} = \frac{V_1}{3}$$

$$\underline{V_1 = 1V}$$

Even though $i = 0$ there is current in the top loop.

$$i_2 = 2.5V_1 \quad V_x = (2.5V_1) \cdot 4 = 10V_1 = \underline{\underline{10V}}$$

$$V_{oc} = V_{ab} = V_a = V_1 - V_x = \underline{\underline{-9V}}$$

Find i_{sc} : $\text{KCL @ X} \quad \frac{1}{3} + 2.5V_1 = \frac{V_1}{3} + \frac{V_1 - V_y}{4}$

$$\text{KCL @ Y} \quad \frac{V_1 - V_y}{4} = 2.5V_1 + \frac{V_y}{5}$$

Remove Fractions: $4 + 30V_1 = 4V_1 + 3V_1 - 3V_y$

$$23V_1 + 3V_y = -4$$

$$5V_1 - 5V_y = 50V_1 + 4V_y$$




$$\underline{\underline{V_y = -5V_1}}$$

$$V_1 = -\frac{1}{2}$$

$$V_y = 2.5$$


$$i_{sc} = \frac{V_y}{5} = \frac{1}{2} = I_N$$
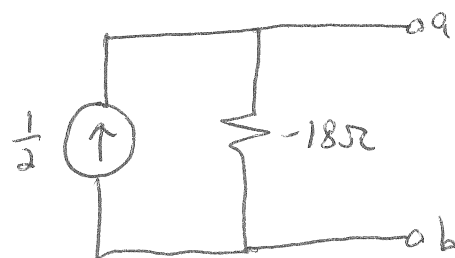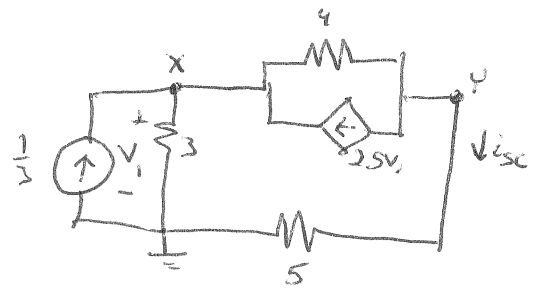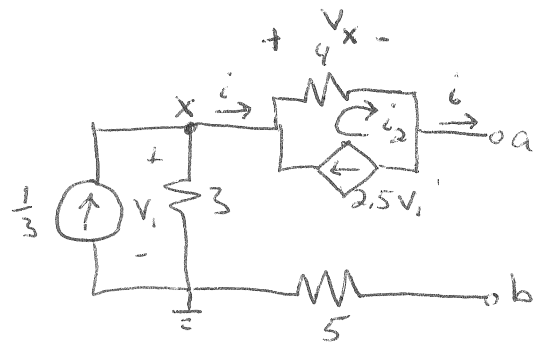
$$R_N = \frac{V_{oc}}{i_{sc}} = \frac{-9}{\frac{1}{2}} = -18\Omega$$



#2 a) Find Thevenin Equivalent

Find V_{oc} :

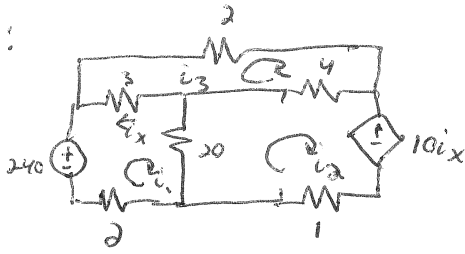

$$\text{KVL } i_1: -240 + (i_1 - i_2)3 + (i_1 - i_2)20 + i_1(2) = 0$$

$$i_2: (i_2 - i_1)20 + (i_2 - i_3)4 + 10i_x + i_2(1) = 0$$

$$i_3: (i_3 - i_1)3 + i_3(2) + (i_3 - i_2)4 = 0$$

$$i_3 - i_1 = i_x$$

$$\Rightarrow \left. \begin{aligned} 25i_1 - 20i_2 - 3i_3 &= 240 \\ -20i_1 + 25i_2 - 4i_3 + 10i_x &= 0 \\ -3i_1 - 4i_2 + 9i_3 &= 0 \\ -i_1 + i_3 - i_x &= 0 \end{aligned} \right\} \begin{array}{l} \text{Plug into} \\ \text{calculator} \\ \text{to solve} \end{array}$$

$$i_1 = 99.6$$

$$i_3 = 78$$


$$i_2 = 100.8$$

$$i_x = -21.6$$

$$V_{oc} = V_{20} = (i_1 - i_2)20$$

$$\boxed{V_{oc} = -24V}$$

Find i_{sc} :

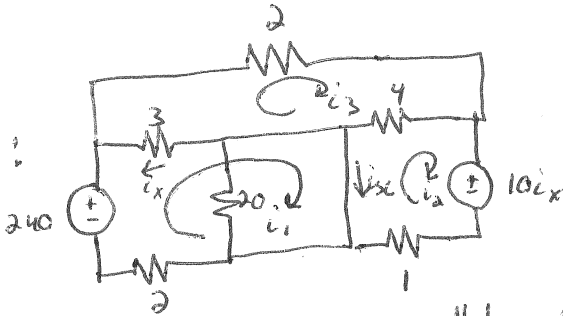

neglect 20Ω because it's in parallel w/ a short circuit

$$20 \parallel 0 = 0$$

$$\text{KVL } i_1: -240 + (i_1 - i_3)3 + 2i_1 = 0$$

$$i_2: (i_2 - i_3)4 + 10i_x + i_2 = 0$$


$$i_3: (i_3 - i_1)3 + 2i_3 + (i_3 - i_2)4 = 0$$

$$i_3 - i_1 = i_x$$

$$\Rightarrow \left. \begin{aligned} 5i_1 - 3i_3 &= 240 \\ 5i_2 - 4i_3 + 10i_x &= 0 \\ -3i_1 - 4i_2 + 9i_3 &= 0 \\ -i_1 + i_3 - i_x &= 0 \end{aligned} \right\} \begin{array}{l} i_1 = 92 \\ i_2 = 96 \\ i_3 = 73.33 \\ i_4 = -18.67 \end{array}$$

$$\boxed{i_{sc} = i_1 - i_2 = -4A}$$
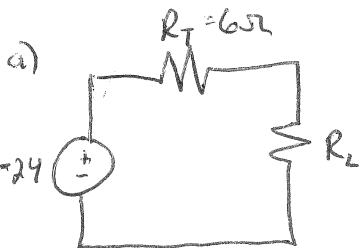
$$\Rightarrow R_T = \frac{V_{oc}}{i_{sc}} = 6\Omega$$




b) max power when $R_L = R_T$

$$\boxed{R_L = 6\Omega}$$

c) $P_{max} = \frac{V_T^2}{4R_L} = \frac{(-24)^2}{4(6)}$

$$\boxed{P_{max} = 24W}$$
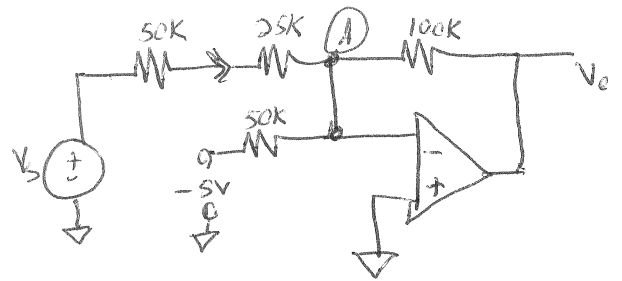
#3 For OpAmp $V_p = V_n$
 $i_p = i_n = 0$
 $V_p = 0 = V_n$




KCL @ A: $\frac{V_s - V_A}{75K} = \frac{V_A - (-5)}{50K} + \frac{V_A - V_o}{100K}$

$V_A = V_n = 0$

$V_o = -100K \left(\frac{V_s}{75K} - \frac{5}{50K} \right)$

$V_o = 10 - \frac{4}{3} V_s$
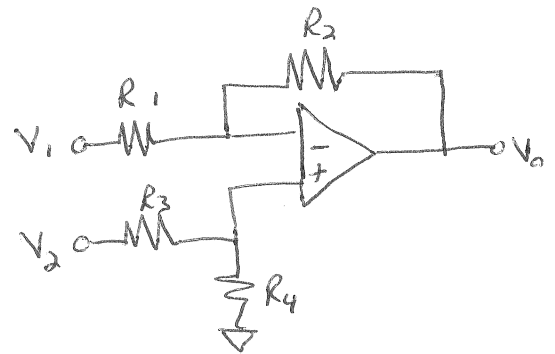
#4 a) Show $V_o = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{R_3}{R_4}} V_2 - \frac{R_2}{R_1} V_1$



$V_p = V_n = V_2 \frac{R_4}{R_3 + R_4}$

$\frac{V_1 - V_p}{R_1} = \frac{V_p - V_o}{R_2} = \frac{V_1 - V_2 \frac{R_4}{R_3 + R_4}}{R_1} = \frac{V_2 \frac{R_4}{R_3 + R_4} - V_o}{R_2}$

$-V_o = \frac{R_2}{R_1} V_1 - \frac{R_2}{R_1} \frac{R_4}{R_3 + R_4} V_2 - \frac{R_4}{R_3 + R_4} V_2$ } Factor out $\frac{R_4}{R_3 + R_4}$

$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_2 - \frac{R_2}{R_1} V_1$

$V_o = \frac{\left(1 + \frac{R_2}{R_1}\right)}{\left(1 + \frac{R_3}{R_4}\right)} V_2 - \frac{R_2}{R_1} V_1$

} divide top and bottom of $\frac{R_4}{R_3 + R_4}$ by R_4
 $= \frac{1}{\frac{R_3}{R_4} + 1}$

b) $V_o = 4V_2 - 11V_1$

$\frac{R_2}{R_1} = 11$

$\frac{1 + 11}{1 + \frac{R_3}{R_4}} = 4$

$\frac{R_3}{R_4} = 2$

One Design: (Many Possible)

$R_1 = 1k\Omega, R_2 = 11k\Omega, R_4 = 1k\Omega, R_3 = 2k\Omega$

#5 a) $i_p = i_n = 0$ so $\underline{V_p = V_s = V_n}$

$V_n = V_o \frac{10k}{10k + 20k}$ Voltage Divider

$V_o \left(\frac{1}{3} \right) = V_s$

$V_o = 3V_s$

b) $V_s = 1.5V$

$V_o = 4.5V$

$i_o = \frac{V_o}{5k} = \frac{4.5V}{5k} = 900\mu A$

