


#1 $V_{P1} = V_{N1} = 0$ $V_{P2} = V_{N2} = 0$

KCL @ V_{N1} : $\frac{V_{S1}}{R_1} = \frac{-V_x}{R_2} \Rightarrow V_x = -\frac{R_2}{R_1} V_{S1}$

KCL @ V_{N2} : $\frac{V_x}{R_3} + \frac{V_{S2}}{R_4} = \frac{-V_o}{R_5}$

$V_o = -\frac{R_5}{R_3} \left(-\frac{R_2}{R_1} \right) V_{S1} - \frac{R_5}{R_4} V_{S2}$

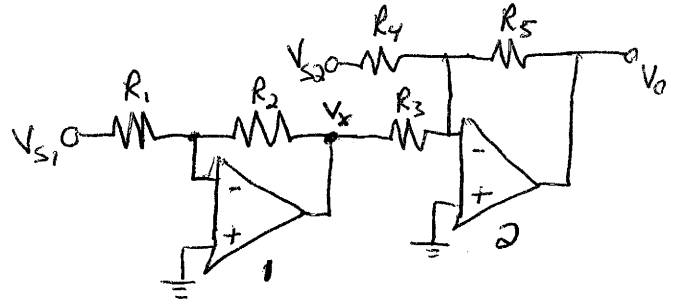$V_o = \frac{R_2}{R_1} \frac{R_5}{R_3} V_{S1} - \frac{R_5}{R_4} V_{S2}$




#2 $V_{P1} = \frac{10k}{10k+10k} V_x = \frac{V_x}{2} = V_{N1} = V_1$

$V_{N2} = V_{P2} = 0$

KCL @ V_{N2} : $\frac{V_x}{10k} + \frac{V_1}{10k} + \frac{V_1+5}{10k} = \frac{-V_o}{20k}$

$V_o = -2V_x - 2V_1 - 2V_1 - 5(2) = V_2$
 $= -2(2V_1) - 2V_1 - 2V_1 - 10$

$V_o = -8V_1 - 10$


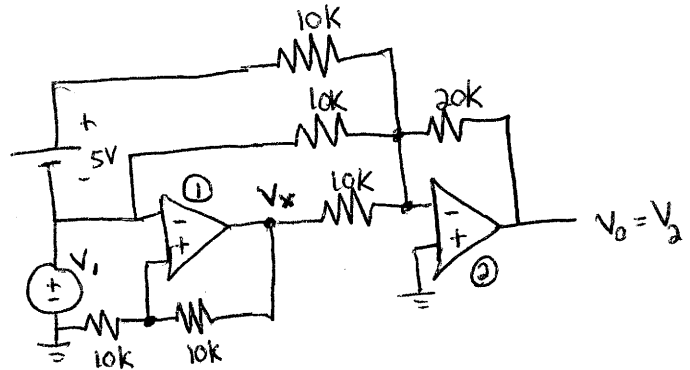


#3 $V_o = K_2 V_2 + K_1 V_1$

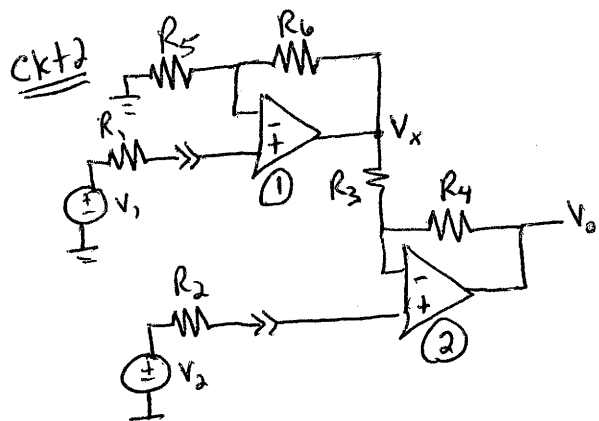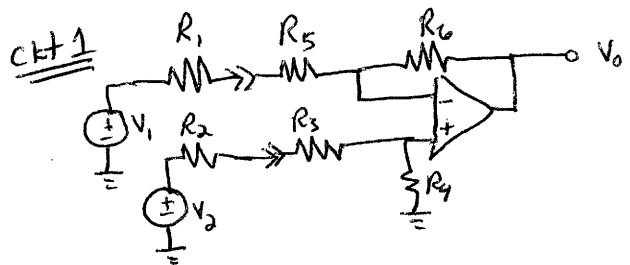(a) Same Ckt as on last HW

$V_o = \left(1 + \frac{R_6}{R_5+R_1} \right) V_2 - \left(\frac{R_4}{R_5+R_1} \right) V_1$

$K_2 = \frac{\left(1 + \frac{R_6}{R_5+R_1} \right)}{\left(1 + \frac{R_2+R_3}{R_4} \right)}$ $K_1 = -\left(\frac{R_4}{R_5+R_1} \right)$



#3 cont...

(a) cont... $V_{P_1} = V_{N_1} = V_1$

$V_{P_2} = V_{N_2} = V_2$

KCL @ V_{N_1} : $\frac{0 - V_1}{R_5} = \frac{V_1 - V_X}{R_6}$

KCL @ V_{N_2} : $\frac{V_X - V_2}{R_3} = \frac{V_2 - V_0}{R_4}$

$V_X = V_1 \left(1 + \frac{R_6}{R_5}\right)$

$V_0 = R_4 \left(\frac{V_2}{R_4} + \frac{V_2}{R_3} - \frac{V_X}{R_3}\right)$

$V_0 = V_2 \left(1 + \frac{R_4}{R_3}\right) - \left(\frac{R_4}{R_3}\right) \left(1 + \frac{R_6}{R_5}\right) V_1$

$K_2 = \left(1 + \frac{R_4}{R_3}\right) \quad K_1 = -\left(\frac{R_4}{R_3}\right) \left(1 + \frac{R_6}{R_5}\right)$

(b) $R_1 = R_2 = 1k \quad R_3 = R_5 = 10k$

(c)

$V_0 = 5(V_2 - V_1)$

ckt 1

$K_1 = -5 = -\left(\frac{R_6}{R_5 + R_1}\right) \Rightarrow R_6 = 5(10k + 1k)$

$R_6 = 55k$

$K_2 = \frac{(1+5)}{1 + \frac{R_2 + R_3}{R_4}} = 5$

$6 = 5 + \frac{5(R_2 + R_3)}{R_4}$

$\frac{1}{5} = \frac{R_2 + R_3}{R_4} \Rightarrow R_4 = 5(10k + 1k)$

$R_4 = 55k$

ckt 2

$K_1 = -5 = -\left(\frac{R_4}{R_3}\right) \left(1 + \frac{R_6}{R_5}\right)$

$K_2 = 5 = \left(1 + \frac{R_4}{R_3}\right)$

$R_4 = 4R_3 = 40k$

$5 = \left(\frac{40k}{10k}\right) \left(1 + \frac{R_6}{10k}\right) = 4 + \frac{4R_6}{10k}$

$R_6 = \frac{10k}{4} = 2.5k$



(d) + ckt 1 only uses one opamp versus two for ckt 2 however, sources v_1 and v_2 are loaded by R_5 and R_3 respectively in ckt 1.

+ These tradeoffs would have to be considered if placing these subtractor circuits into a design.

#4 $V_{OH} = 15V$ $V_{OL} = 0$

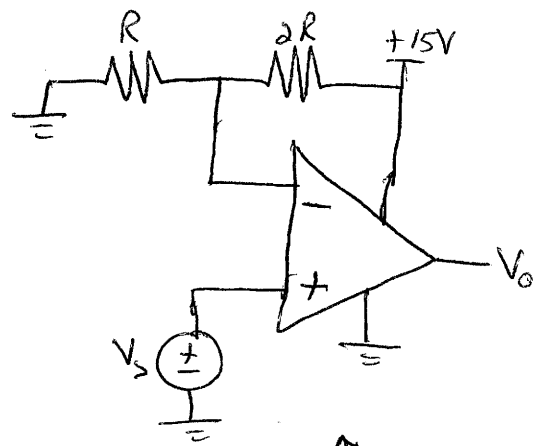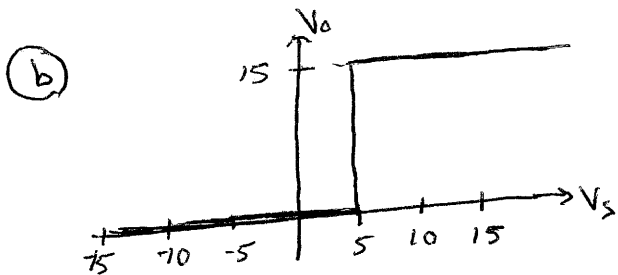a) $V_- = \frac{R}{R+2R} (15) = 5$

$V_o = V_{OH}$ if $V_s > 5V$
 $V_o = V_{OL}$ if $V_s < 5V$



↑
 Open Loop Comparator
 No Feedback so $V_+ \neq V_-$
 ↓


#5 $V_{OH} = 10V$ $V_{OL} = 0V$

a) if $V_p > V_n \Rightarrow V_{OH}$

$V_s > -2$ $V_o = V_{OH}$

if $V_p < V_n \Rightarrow V_{OL}$

$V_s < -2$ $V_o = V_{OL}$

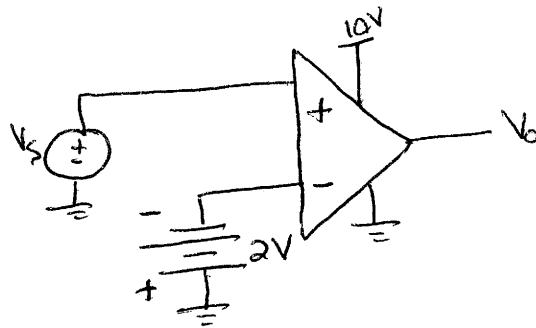

b)

