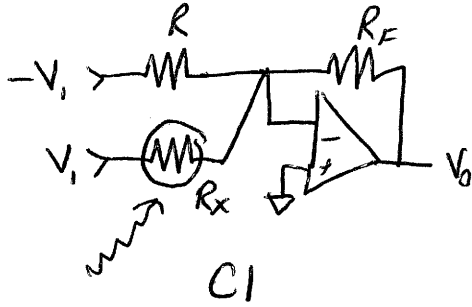


#1



$$V_o = K V_i$$

Darkness  $R_x = 10 \text{ k}\Omega$ Sunlight  $R_x = 2 \text{ k}\Omega$ 


a) What is K for C1 and C2

C1 KCL at -terminal

$$-\frac{V_i}{R} + \frac{V_i}{R_x} = -\frac{V_o}{R_F}$$

$$V_o = V_i \left( \frac{R_F}{R} - \frac{R_F}{R_x} \right)$$

$$K = \frac{R_F}{R} - \frac{R_F}{R_x}$$

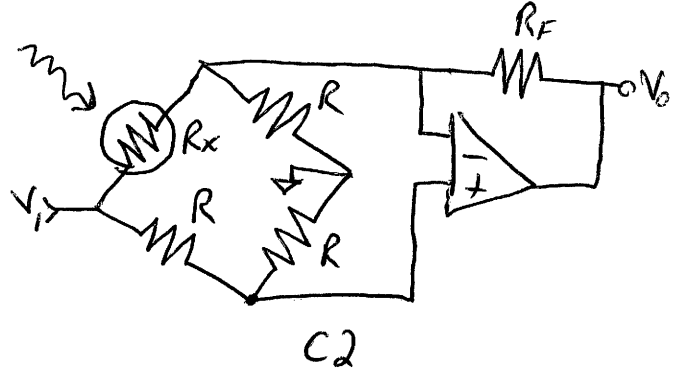C2  $V_+ = \frac{V_i R}{R+R} = \frac{V_i}{2}$  Voltage DividerKCL @  $V_-$ 

$$\frac{V_i - V_i/2}{R_x} = \frac{V_i/2}{R} + \frac{V_i/2 - V_o}{R_F}$$

$$K = \frac{1}{2} \left( 1 + \frac{R_F}{R} - \frac{R_F}{R_x} \right)$$

b)  $V_i = 15 \text{ V}$   $R, R_F = ?$  $V_o = -10$  sunlight $V_o = +10$  darkness

$$\textcircled{1} 10 = 15 \left( \frac{R_F}{R} - \frac{R_F}{10\text{k}} \right)$$

$$\textcircled{2} -10 = 15 \left( \frac{R_F}{R} - \frac{R_F}{2\text{k}} \right)$$

Subtract equations

$$\frac{20}{15} = -\frac{R_F}{10\text{k}} - \frac{R_F}{2\text{k}}$$

$$\boxed{R_F = \frac{10\text{k}}{3} = 3.3\text{k}\Omega} \Rightarrow \boxed{R = \frac{10\text{k}}{3} = 3.3\text{k}\Omega}$$

c) Repeat b) for C2

$$-\frac{20}{15} = 1 + \frac{R_F}{R} - \frac{R_F}{2\text{k}}$$

$$\frac{20}{15} = 1 + \frac{R_F}{R} - \frac{R_F}{10\text{k}}$$

subtract equations

$$\frac{40}{15} = -\frac{R_F}{10\text{k}} + \frac{R_F}{2\text{k}}$$

$$\boxed{R_F = \frac{100\text{k}}{15} = 6.67\text{k}\Omega}$$

$$\boxed{R = 6.67\text{k}\Omega}$$

#1 d) C1 uses 2 fewer resistors compared to C2

Power is power through each resistor summed together (assuming opamp power is equal)

If  $R_x = 2k$

$$P_{C1} = \frac{15^2}{3.3k} + \frac{15^2}{2k} + \frac{10^2}{3.3k} = \underline{\underline{210mW}}$$

$$P_{C2} = \frac{(\frac{15}{2})^2}{2k} + \frac{(\frac{15}{2})^2}{6.67k} + 2 \cdot \frac{(\frac{15}{2})^2}{6.67k} + \frac{(\frac{15}{2} - 10)^2}{6.67k} = \underline{\underline{99mW}}$$

Similar calculation when  $R_x = 10k$

$$P_{C1} = 121mW$$

$$P_{C2} = 32mW$$

So, C2 uses less power but uses more components.

#2

$$V_p = V_n \quad i_p = i_n = 0$$

KCL @ (A)

$$\frac{5-3}{500} + \frac{V_{o2}-3}{3k} = \frac{3-1}{1k}$$

$$12 + V_{o2} - 3 = 6$$


$$\boxed{V_{o2} = -3V}$$

KCL @ (B)

$$\frac{V_{o1}-5}{4k} = \frac{5-3}{2k} + \frac{5-3}{500}$$

$$V_{o1} - 5 = 16 + 16$$



$$\boxed{V_{o1} = 37V}$$

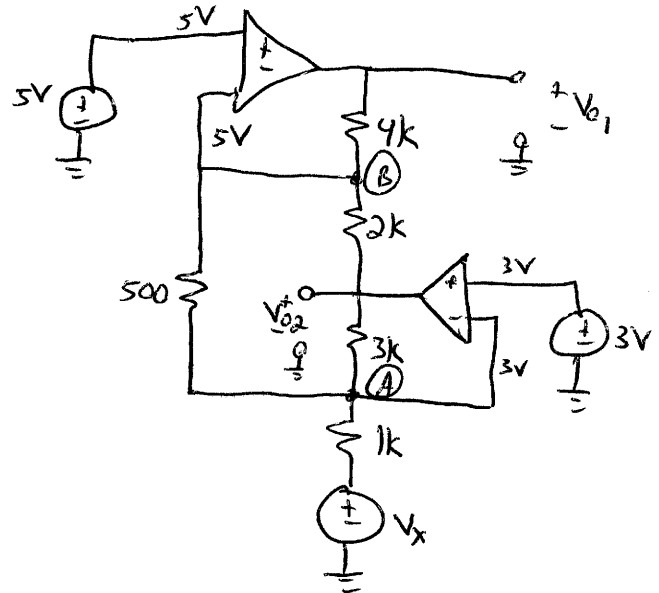

#3 Find  $V_{oc}$  and  $R_T$

$$V_{oc} = V_{ab} = V_a$$

Source transformation on current source

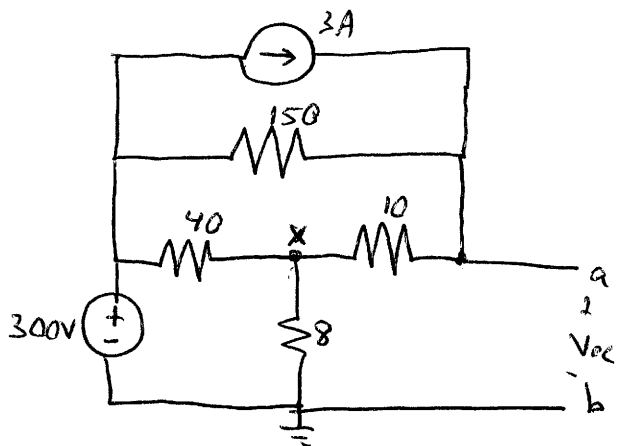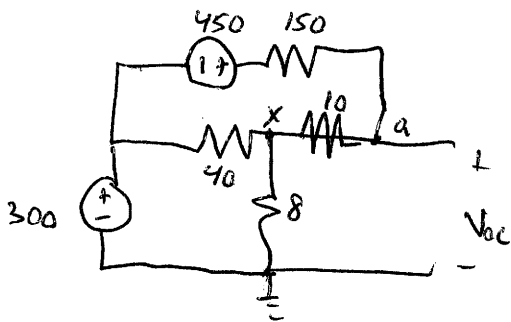

KCL @ x

$$\frac{300 - V_x}{40} = \frac{V_x}{8} + \frac{V_x - V_a}{10}$$

KCL @ a

$$\frac{V_x - V_a}{10} + \frac{750 - V_a}{150} = 0$$

$$15V_x - 15V_a = -750 + V_a$$

$$V_x = \frac{-750 + 16V_a}{15} \quad \text{Plug into KCL @ x eqn.}$$

$$\frac{300}{40} - \frac{(-750 + 16V_a)}{15(40)} = \frac{-750 + 16V_x}{15(8)} + \frac{-750 + 16V_a}{15(10)}$$


$$-\frac{V_a}{10}$$

$$4500 + 750 + 16V_a = -3750 + 80V_a = 3000 + 64V_a$$


$$-60V_a$$

$$V_{oc} = V_a = 120V$$

Find  $R_T$ : Turn off all sources

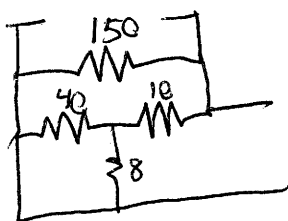

$\Rightarrow$

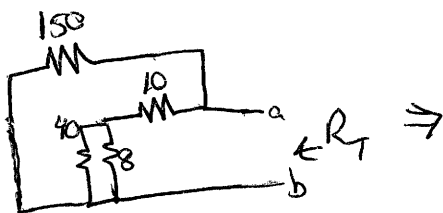

$$\frac{40(8)}{48} = 6.67$$


$$R_T = 50 \parallel (10 + 6.67)$$

$$= \frac{50(16.67)}{66.67}$$

$$R_T = 15 \Omega$$
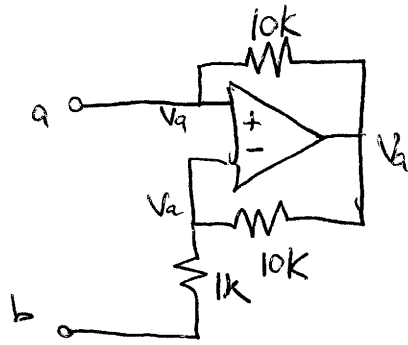
#4  $V_a = V_p = V_n$

$\frac{V_p - V_o}{10k} = 0$  (Not current flows into opamp or through open ckt)




$V_p = V_o = V_n$  ← So no current through the other 10k  
 ↳ No current through 1k by KCL @  $V_n$

$V_b = V_a \Rightarrow V_{oc} = 0V = V_T$

to find  $R_T$  apply a "test" voltage source and determine test current.

$i_{test} = \frac{V_{test} - V_o}{10k}$       Voltage Divider  
 $V_{test} = V_p = V_n = \frac{1k}{1k+10k} V_o$

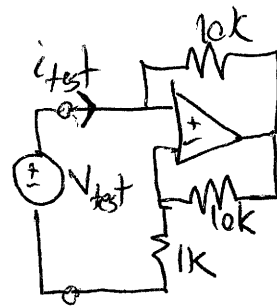$V_o = \frac{11k}{1k} V_{test} = 11V_{test}$



$i_{test} = \frac{V_{test} - 11V_{test}}{10k}$

$\frac{V_{test}}{i_{test}} = R_T = \frac{10k}{-10} = -1k$



# #5 Node Voltage

KCL @ super node

$$\frac{0 - V_A}{20} + \frac{V_B - V_B}{2} = \frac{V_D - V_C}{4} + \frac{V_D}{80} + 3.125 V_D$$

$$V_D = V_B - V_C$$

$$-4V_A + 40V_B - 40V_A = 20V_D - 20V_C + V_D + 35V_B - 25V_C$$

$$\underline{-44V_A - 210V_B + 270V_C - 21V_D = 0 \quad \text{Equation 1}}$$

KCL @ C

$$\frac{V_B - V_C}{1} = \frac{V_C}{40} + \frac{V_C - V_D}{4} \Rightarrow \underline{40V_B - 51V_C + 10V_D = 0 \quad \text{Equation 2}}$$

$$\underline{V_B = 20 \quad \text{Equation 3}}$$

$$V_A = V_D + 35i_\beta \quad i_\beta = \frac{V_C}{40}$$

$$\underline{40V_A - 35V_C - 40V_D = 0 \quad \text{Equation 4}}$$

Put into calculator to solve.

$$V_A = -20.25V$$

$$V_B = 20$$

$$V_C = 10$$

$$V_D = -29$$

KCL @ B

$$\frac{V_A - V_B}{2} + \frac{V_C - V_B}{1} = i_{20V} = -30.125A$$

$$P = IV = (-30.125A)(20V)$$

$$\boxed{P = -602.5W}$$

↑  
minus sign means the 20V source is delivering power.

