

Department of Electrical Engineering and Computer Science  
**ENGR 210. Introduction to Circuits and Instruments (4)**

Quiz No. 11

4/8/05

**PUT ANSWERS IN THE SPACE PROVIDED AND, IF APPROPRIATE, SHOW YOUR WORK. BE SURE TO STATE ANY ASSUMPTIONS**

**Problem 1 Elementary phasors, (10 points)**

Use phasors to combine the following sinusoidal functions into a single trigonometric expression. Your answer should be expressed as a real function.

$$y = 40\cos(\omega t + 60^\circ) + 80\sin(\omega t + 135^\circ) - 100\cos(\omega t + 270^\circ);$$

①  $y = 40\cos(\omega t + 60^\circ) + 80\cos(\omega t + 45^\circ) - 100\cos(\omega t + 270^\circ)$   
 cosine conversion

③  $y = 40e^{j60} + 80e^{j45} - 100e^{j270}$   
 polar conversion

③  $y = 40\cos(60) + j40\sin(60) + 80\cos(45) + j80\sin(45) - 100\cos(270) - j100\sin(270)$

③  $y = 40(1/2) + j40(\sqrt{3}/2) + 80(\sqrt{2}/2) + j80(\sqrt{2}/2) - 100(0) - j100(-1)$   
 math

$$y = 20 + j20\sqrt{3} + 40\sqrt{2} + j40\sqrt{2} + j100$$


conversion to polar  
 $y = (20 + 40\sqrt{2}) + j(20\sqrt{3} + 40\sqrt{2} + 100)$

②  $y = 26.57 + j(191.21)$   
 $y = 206.0 e^{68.2j}$

①  $y = 206\cos(\omega t + 68^\circ)$   
 answer

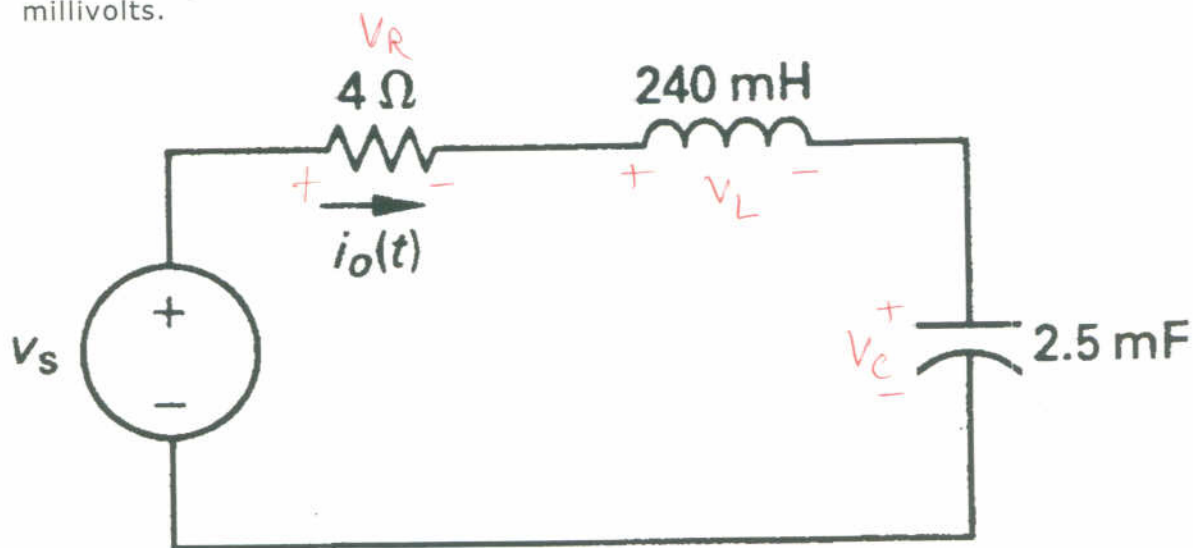**Problem 2 Phasor circuits, (10 points)**

Find the steady state expression for  $i_o(t)$  in the circuit below if  $v_s(t) = 100\sin(50t)$  millivolts.



$$v_s(t) = 0.1 \sin(50t)$$

conversion ← ①

$$v_s(t) = 0.1 \cos(50t - 90^\circ)$$

$$v_s(t) = 0.1 e^{-j90}$$

math and conversions ← ③

$$V_R = 4 + j0$$

$$V_L = j\omega L = j(50)(0.240\text{H}) = j12 = 0 + j12$$

$$V_C = \frac{1}{j\omega C} = \frac{1}{j(50)(2.5 \times 10^{-3}\text{F})} = j8 = 0 - j8$$

$$Z_{eq} = V_R + V_L + V_C$$

$$Z_{eq} = 4 + j12 - j8$$

$$Z_{eq} = 4 + j4$$

$$V = IZ$$

$$I = \frac{V}{Z} = \frac{0.1 e^{-j90}}{4 + j4} = \frac{0.1 (\cos(-90) + j \sin(-90))}{4 + j4} =$$

$$I = \frac{-0.1j(4 - j4)}{4 + j4(4 - j4)} = \frac{-0.4j - 0.4}{16 + 16} = \frac{-0.4(j+1)}{32}$$

$$I = -0.0125 - 0.0125j = 0.0177 e^{-j135}$$

answer ← ①

$$I_o(t) = 0.0177 \cos(50t - 135^\circ) \text{ A}$$

ALTERNATE WAY (EASIER)

$$\frac{0.1 e^{-j90}}{4\sqrt{2} e^{j45}} = 0.0177 e^{-j135}$$

$$I_o(t) = 0.0177 \cos(50t - 135^\circ) \text{ A}$$

③ → same as other way