

Department of Electrical Engineering and Computer Science  
**ENGR 210. Introduction to Circuits and Instruments (4)**

Quiz No. 12

4/15/05

**PUT ANSWERS IN THE SPACE PROVIDED AND, IF APPROPRIATE, SHOW YOUR WORK. BE SURE TO STATE ANY ASSUMPTIONS**

**Problem 1 Transfer functions (10 points)**

(a) Determine the transfer function  $T_v(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)}$  of the following circuit. Be sure to put the denominator of your transfer function in standard form.


$T_v(j\omega) = \frac{j\omega/2000}{1+j\omega/2000}$  OR  $\frac{j\omega}{2000+j\omega}$

(b) What is the cutoff frequency  $\omega_c$  for this filter?  $\omega_c = 2000 \text{ rad/s} \approx 318 \text{ Hz}$

(c) What is  $T_v(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)}$  for  $\omega = 2\omega_c$ ?  
 $T_v(j2\omega_c) = \frac{j2\omega_c}{2000+j2\omega_c} = \frac{j4000}{2000+j4000} = \frac{j2}{1+j2}$

(d) If  $v_i(t) = 10 \cos(\omega t)$  write the steady state expression for  $v_o(t)$  when  $\omega = 2\omega_c$ .  
 $v_o(t) = 8.94 \cos(\omega t + 26.6^\circ)$

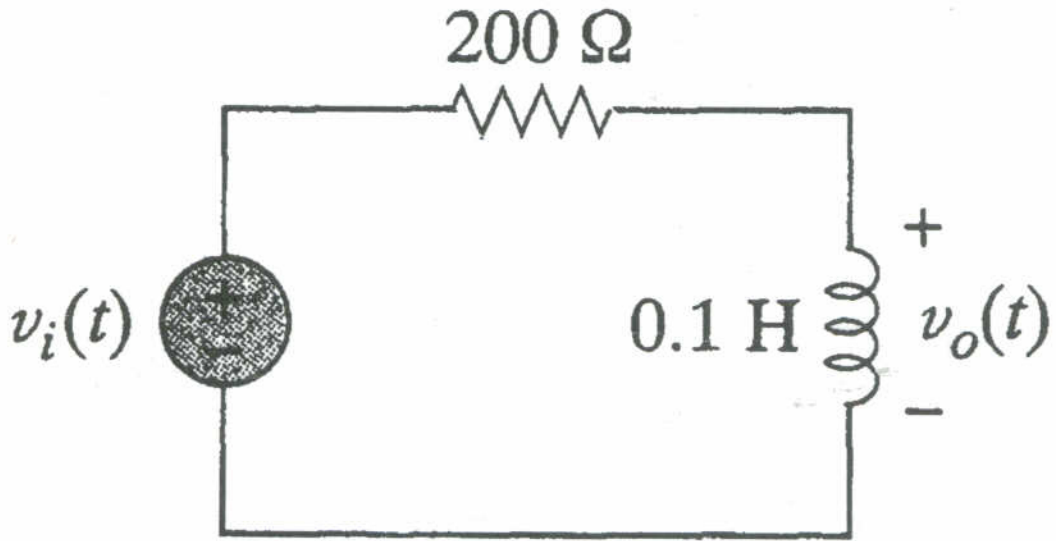(e) What kind of filter is this? High-pass, low-pass, band-pass, band-reject, notch, something else?  
 Type = high pass



$$T_v(j4000 \text{ rad/s}) = \frac{j2(1-j2)}{1+j2(1-j2)}$$

$$= \frac{j2+4}{1+4} = \frac{j2+4}{5}$$

$$= 0.8 + 0.4j \equiv 0.894 \cos(\omega t + 26.6^\circ)$$

$$= 8.94 \cos(\omega t + 26.6^\circ)$$

*apt. setting up phasor analysis pt for ohm's law*  
*know it or not*  
*same as (b)*  
*for math*  
*for answer*  
*same as (b)*

**Problem 2 Frequency dependent transfer functions (10 points)**

2 for math  
1 for answer

(a) What is the cutoff frequency  $\omega_c$  for the filter described by

$$T_v(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)} = \frac{4}{2 + j\omega 10} \quad \omega_c = \underline{0.2 \text{ rad/s}}$$

(b) Using the chart below plot the frequency dependence of this filter. Be sure to label your axes.

(c) What is the passband gain of this filter in decibels.

same as (a) Passband gain = 6 dB

1 pt for axis  
1 pt for points  
2 pts for line

(A)  $\frac{4}{2 + j\omega 10} = \frac{0.4}{0.2 + j\omega} \quad \boxed{\omega_c = 0.2 \text{ rad/s}}$

(C)  $20 \log_{10} |2| = \boxed{6 \text{ dB}}$

