

CASE WESTERN RESERVE UNIVERSITY

Case School of Engineering

Department of Electrical Engineering and Computer Science

ENGR 210. Introduction to Circuits and Instruments (4)


Quiz No. X2

1/28/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE

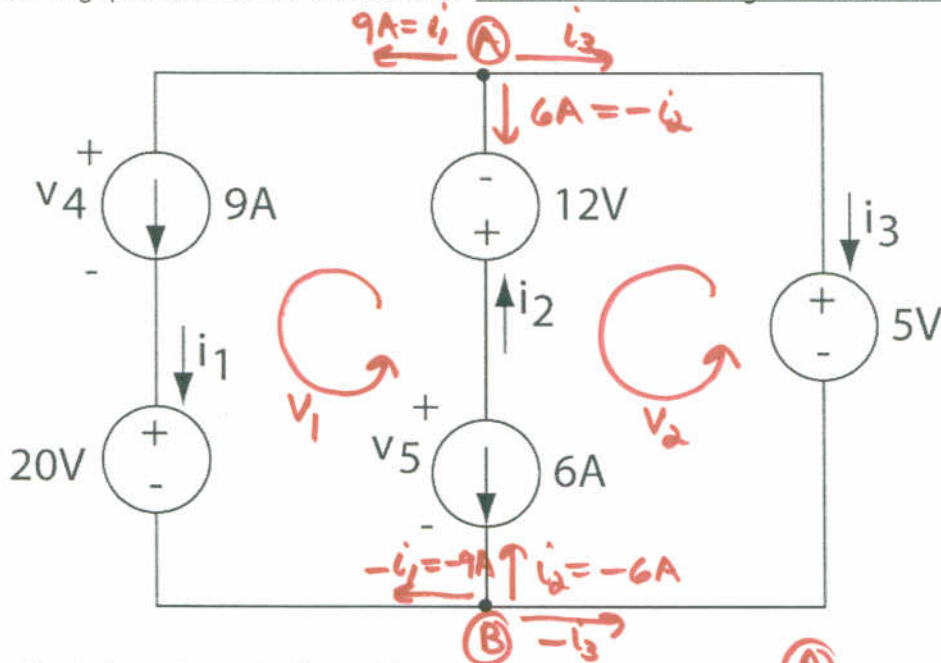Problem 1 (10 points) – CONNECTION CONSTRAINTS

Answer the following questions for the circuit below. Be sure to follow the sign conventions indicated.



(a) Determine the indicated currents through the voltage sources.

$i_1 =$ 9 amperes

$i_2 =$ -6 amperes

(b) What is the current through the 5 volt voltage source.

$i_3 =$ -15 amperes

(c) What is the voltage across each current source?

$V_4 =$ -15 volts

$V_5 =$ 17 volts

② < 1 for good work
< 1 for answer

② - same as I1

② - same as I1

② - same as I1

② - same as I1

$V_1: V_4 + 20V - V_5 + 12V = 0$

$V_2: -12V + V_5 - 5V = 0$

$V_5 = 17V$

$V_4 = -15V$

①
 $i_1 = 9A$
 $-i_2 = 6A$
 $i_3 = ?$


$i_1 - i_2 + i_3 = 0$

$9A + 6A = -i_3$

$i_3 = -15A$

② not needed. Use to check!

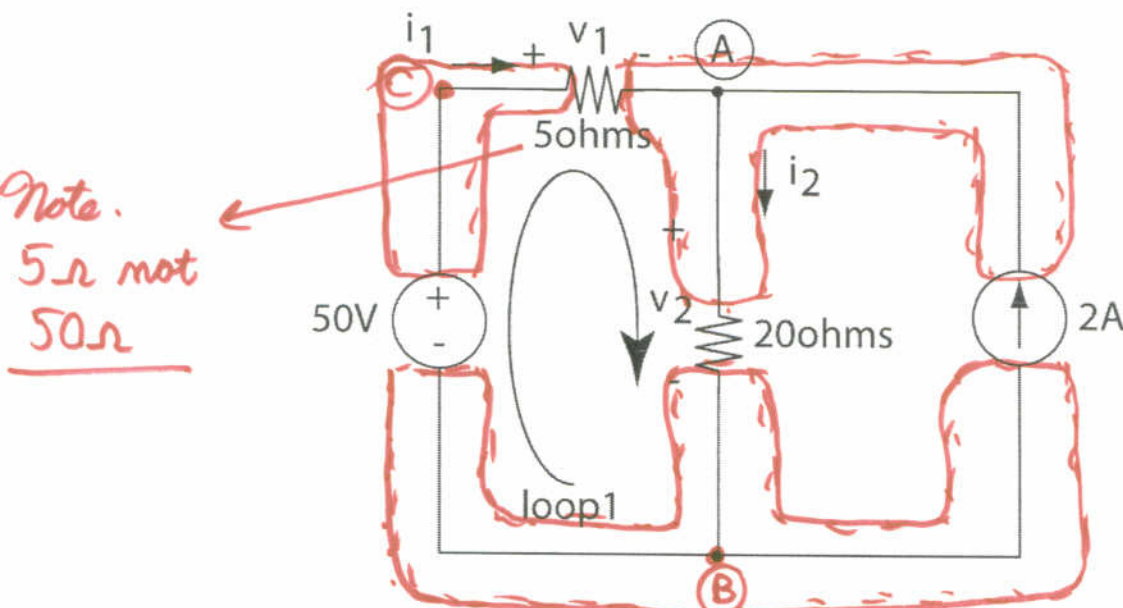Problem 2 (10 points) COMBINED CONSTRAINTS



(a) How many nodes are in the above circuit? # nodes = 3 (2) - 2 for answer

(b) Write the Kirchoff's Current Law equation for all the currents at node A. Your answer should be in terms of given circuit parameters, i.e., i_1 , i_2 , etc.

$$i_1 - i_2 + 2A = 0 \quad (2) - 2 \text{ for equation}$$

(c) Write the Kirchoff's Voltage Law equation for loop 1. Your answer should be in terms of given circuit parameters, i.e., i_1 , i_2 , etc.

$$V_1 + V_2 - 50V = 0 \quad (2) - 2 \text{ for equation}$$

(d) What are the values of i_1 and i_2 ?

$i_1 =$ 0.4 amperes

$i_2 =$ 2.4 amperes

Handwritten calculations:

$$V_1 = (5\Omega)(i_1)$$

$$V_2 = (20\Omega)(i_2) = (20\Omega)(i_1 + 2A) = 20\Omega \cdot i_1 + 40V$$

$$50V = V_1 + V_2 = 5\Omega \cdot i_1 + 20\Omega \cdot i_1 + 40V$$

$$10V = 25\Omega \cdot i_1 \quad i_1 = 0.4A$$

$$i_2 = 0.4A + 2A = 2.4A$$

Additional notes: "1 for correct", "2 for good work", "same as I1".