

CASE WESTERN RESERVE UNIVERSITY
 Case School of Engineering
 Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)


Quiz No. 5

2/20/04

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS

LINEARITY - SUPERPOSITION

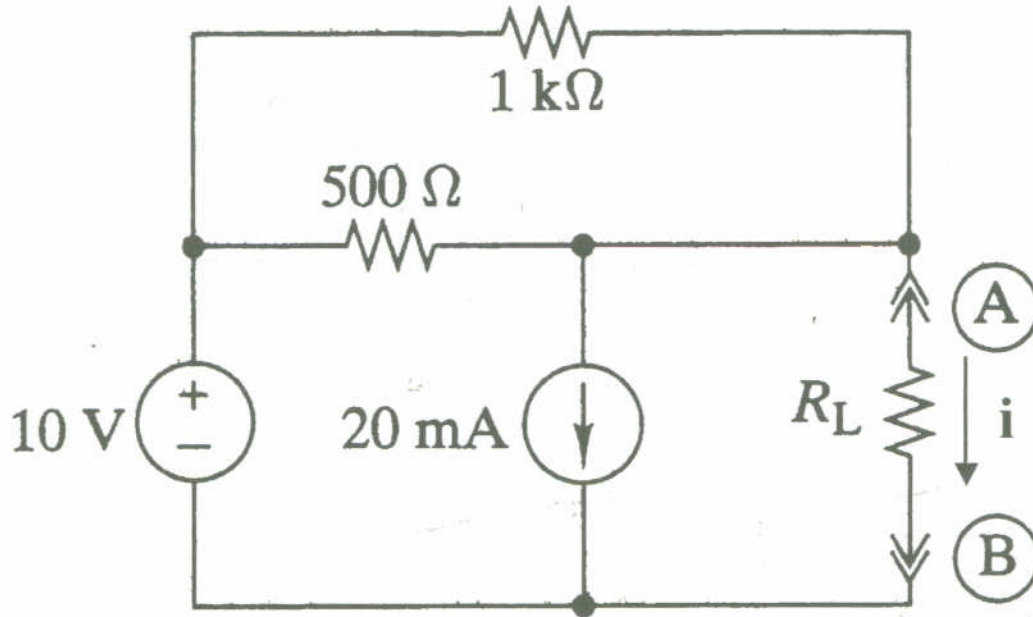1. (10 points) Assume $R_L = 500\Omega$. Using superposition determine



- (a) the current i_1 through R_L from the 10 volts source. $i_1 = \underline{0.012A}$ (5) *correctly redrawn circuit (2) equations (2) answer (1)*
- (b) the current i_2 through R_L from the 20 milliampere source. $i_2 = \underline{-0.008A}$ (5) *same as above*

$R_L = 500\Omega$ $V = IR$

turn off current source → open

$i_1 = 0.012A$ (1)

current divider

$= \frac{333.3}{(333.3 + 500)} (20mA)$

$= -0.008A$

$i_2 = -0.008A$ (1)


turn off voltage source → short

$\frac{(1000 \times 500)}{1000 + 500} = 333.3\Omega$

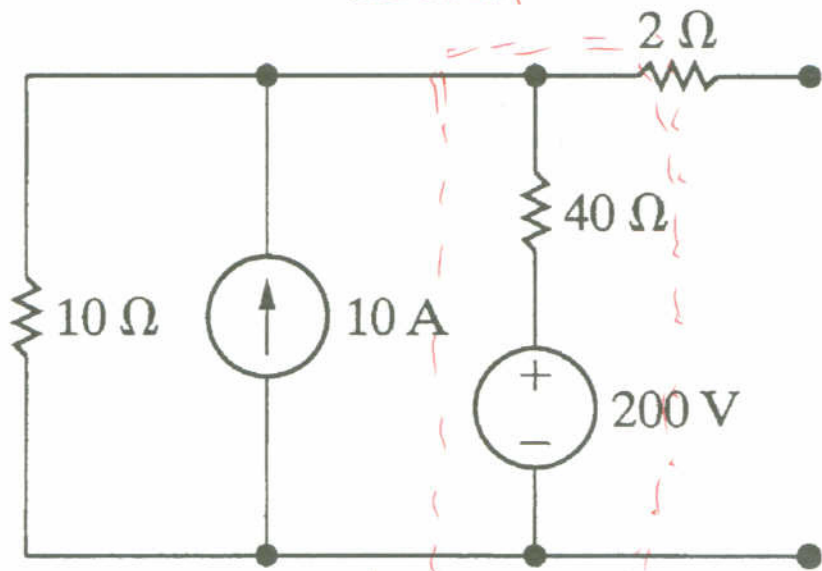2. (10 points) What is the Thevenin equivalent of the circuit shown below.


$V_T =$ 120V 5 $R_T =$ 10Ω 5

1 point for redrawn circuits
3 points for correct equivalent circuit
1 point for answer



same as R_T


$V = IR$

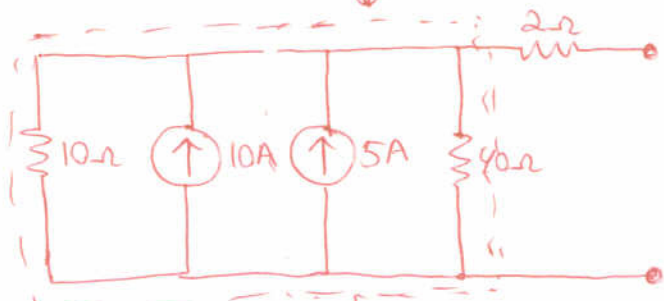

$\frac{200V}{40\Omega} = 5A$


③

①

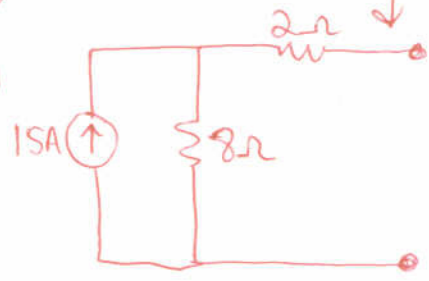

$10A + 5A = 15A$

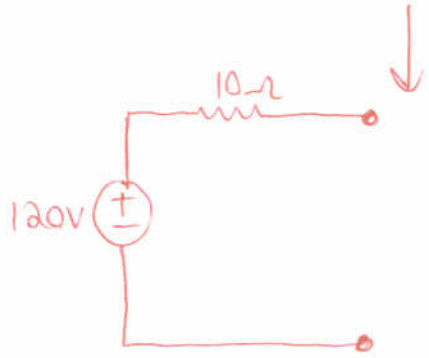$\frac{(40 \times 10)}{(40 + 10)} = 8\Omega$



$(15A)(8\Omega) = 120V$

$8\Omega + 2\Omega = 10\Omega$

$V_T = 120V$

$R_T = 10\Omega$

①