

CASE WESTERN RESERVE UNIVERSITY
 Case School of Engineering
 Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 6

2/25/05


PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS

MAXIMUM SIGNAL TRANSFER

Problem 1 (10 points)

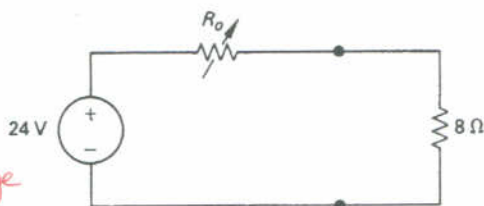- (4) (a) Find the value of the variable resistor R_0 in the circuit below that will result in maximum power dissipation in the $8\text{-}\Omega$ load resistor.

*either you got it or you didn't
 2 points for 8Ω*



*for max power
 $R_0 = 8\Omega$
 $R_0 = 8\Omega$*

*two points for correct voltage
 two points for correct power*

- (4) (b) What is the maximum power that can be delivered to the $8\text{-}\Omega$ load resistor. $P = 72\text{W}$

- (2) (c) If R_0 increases from 10Ω to 25Ω , the power dissipated by the 8Ω load will (circle one)

- (i) increase
- (ii) remain the same
- (iii) decrease.

same as part A

(B)
$$P = \frac{V^2}{R} = \frac{(24V)^2}{8\Omega} = \frac{576V}{8\Omega} = 72W$$
 $P = 72W$


(C) Decrease; P_{max} occurs when $R_0 = 8\Omega$, therefore going from 10Ω to 25Ω will decrease the power.

* Note, if you wrote down 8Ω for part A, and subsequently got $18V$ for part B, you were given 6 points out of 8. Most people did this.

LINEAR DEPENDENT SOURCES

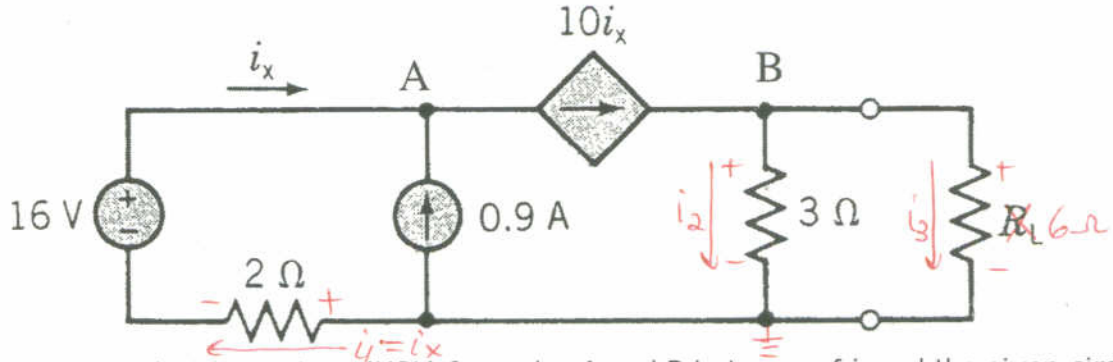Problem 2 (10 points)

Consider this active circuit with a dependent source. Assume $R_L = 6\Omega$



a) Write node analysis equations (KCL) for nodes A and B in terms of i_x and the given circuit parameters. These are the connection equations. Do not write i_x in terms of other circuit variables for this part of your answer.

Node	Node-Voltage Equation					
A	$-\frac{1}{2}$	$\cdot V_A$	+	0	$\cdot V_B$	$= -8.9 + 10i_x$
B	0	$\cdot V_A$	+	$\frac{1}{2}$	$\cdot V_B$	$= 10i_x$

b) Now write an expression for i_x in terms of V_A , V_B and the given circuit parameters. (This is a constraint equation.)

two points for correct substitution
one point for answer

$$-\frac{1}{2}V_A = -8.9 + 10i_x \rightarrow -\frac{1}{2}V_A = -8.9 - 10\left(\frac{V_A - 16 - 0}{2}\right) \rightarrow \frac{1}{2}V_A = 8.9 + 5V - 80$$

$$\frac{1}{2}V_B = 10i_x \rightarrow \frac{1}{2}V_B = 10\left(\frac{V_A - 16 - 0}{2}\right) \rightarrow \frac{1}{2}V_B = 5V_A - 80$$

$$4.5V_A = 71.1$$

$$5V_A - \frac{1}{2}V_B = 80$$

c) Using your equations from parts (a) and (b) determine the node voltages for the above circuit values.

note: if one answer is correct

V_A	15.8V	V_B	2.0V
-------	-------	-------	------

Node A $-\left(\frac{V_A - 16 - 0}{2}\right) + 0.9 - 10i_x = 0 \quad \underline{\underline{-\frac{V_A}{2} = -8.9 + 10i_x}}$

Node B $10i_x - \frac{V_B - 0}{3} - \frac{V_B - 0}{6} = 0 \quad \underline{\underline{\frac{V_B}{2} = 10i_x}}$

4.5V_A = 71.1 $V_A = 15.8V$ $5V_A - \frac{1}{2}V_B = 80 \quad 5(15.8) - \frac{1}{2}V_B = 80$

$1 = \frac{1}{2}V_B \quad \underline{\underline{V_B = 2V}}$