

CASE WESTERN RESERVE UNIVERSITY

Case School of Engineering

Department of Electrical Engineering and Computer Science

ENGR 210. Introduction to Circuits and Instruments (4)


Quiz No. 7

3/4/05

PUT ANSWERS IN THE SPACE PROVIDED AND, IF APPROPRIATE, SHOW YOUR WORK. BE SURE TO STATE ANY ASSUMPTIONS

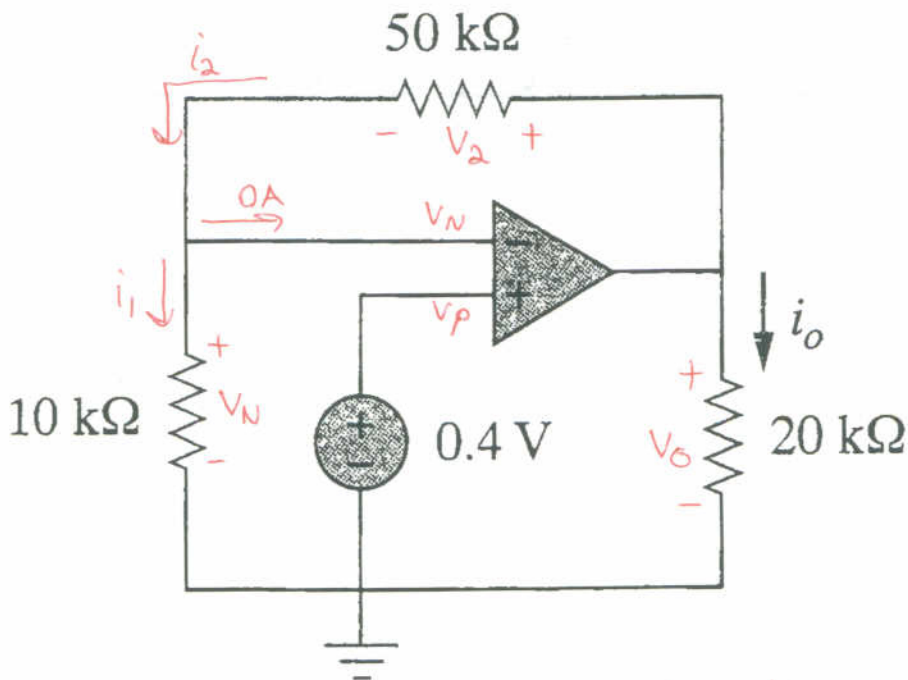Problem 1 (10 points)

Determine i_o in the circuit below. $i_o = \underline{0.12\text{mA}}$ → point structure below



$$\begin{aligned} \textcircled{3} \quad & V_n = V_p = 0.4\text{V} \\ \textcircled{3} \quad & i_2 = i_1 = \frac{0.4\text{V}}{10\text{k}\Omega} = 0.04\text{mA} \\ \textcircled{3} \quad & V_2 = i_2 (50\text{k}\Omega) = 2\text{V} \end{aligned}$$

$$i_o = \frac{V_o}{20\text{k}\Omega}$$

$$V_o = V_1 + V_2 = 2.4\text{V}$$


$$i_o = \frac{2.4\text{V}}{20\text{k}\Omega}$$

$$i_o = 0.12\text{mA} \quad \text{--- } \textcircled{1}$$


* Note, you did not have to show all the work above, but you had to show some work beyond the answers

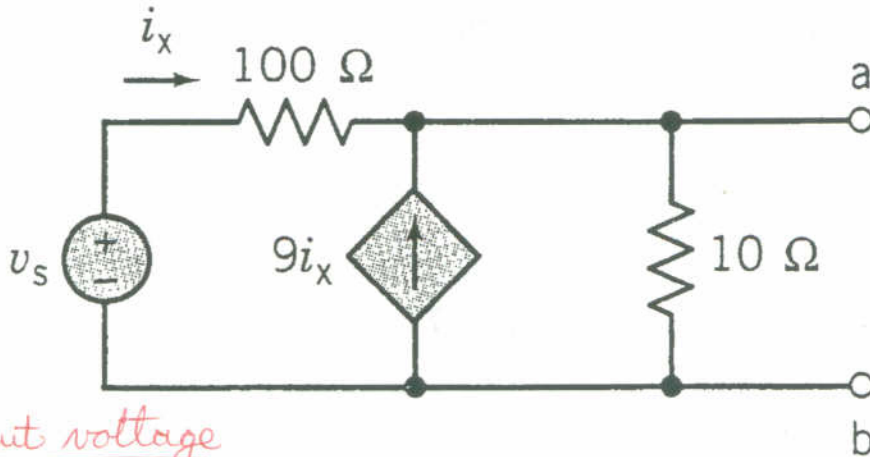Problem 2 (10 points)

Determine the Thevenin equivalent circuit for the circuit shown below at the output terminals a-b.



open circuit voltage

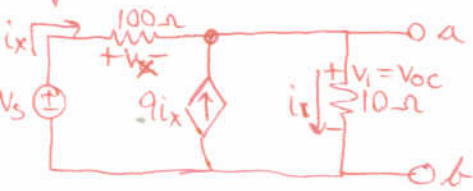

$$V_{oc} = i_1 (10\Omega)$$

$$i_1 = i_x + 9i_x = 10i_x$$

$$i_x = \frac{V_x}{100\Omega}$$

$$V_x = V_s - V_{oc}$$


$$i_x = \frac{V_s}{100\Omega} - \frac{V_{oc}}{100\Omega}$$

$$i_1 = \frac{V_s}{10\Omega} - \frac{V_{oc}}{10\Omega}$$


$$V_{oc} = V_s - V_{oc}$$

$$2V_{oc} = V_s$$

$$\underline{V_{oc} = \frac{1}{2}V_s}$$

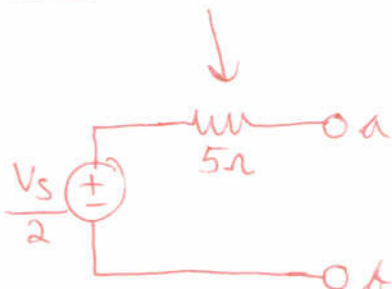

short circuit current

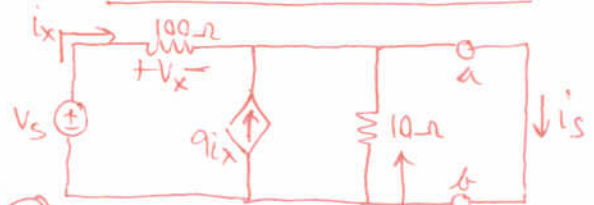

$$i_{sc} = i_x + 9i_x - 0$$

$$= 10i_x$$

$$i_x = \frac{V_x}{100}$$

$$V_x = V_s - 0$$

$$i_x = \frac{V_s}{100\Omega}$$

$$i_{sc} = \frac{V_s}{10\Omega}$$

$$R_T = \frac{V_{oc}}{I_{sc}} = \frac{V_s/2}{V_s/10\Omega} = 5\Omega$$

$$\underline{R_T = 5\Omega}$$

* Note - equivalent R (can NOT look back on a dependent source!)

④ - method
⑤ - answer

same as above ⑤

Note: in parallel w/ short, no current through 10 ohm resistor