

# Microwave Engineering - Take Home Quiz, May 1972

Name FRANCIS L. MGRAT

1. 9

2. 9

3. 9


27/30

1. Two lossless two-ports are connected in cascade as shown. They are characterized by scattering matrices with parameters  $S_{11}, S_{22}, S_{12}$  and  $S'_{11}, S'_{22}, S'_{12}$  respectively where

$$S_{11} = S_{22} = j/4, \quad S'_{11} = 1/2, \quad S'_{22} = -1/2. \quad \text{Find}$$

the scattering matrix parameters for the overall network.

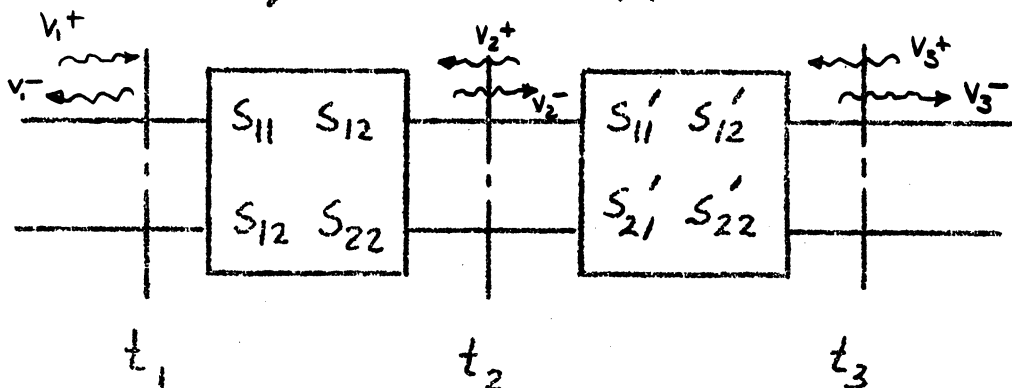Hint: With a matched load connected at  $t_3$  the first two-port sees a termination at  $t_2$  with a reflection coefficient  $S'_{11}$ .



$$V_1^- = \frac{j}{4} V_1^+ + S_{12} V_2^+$$

$$V_2^- = S_{22} V_1^+ + \frac{j}{4} V_2^+$$

$$V_2^+ = \frac{1}{2} V_2^- + S'_{12} V_3^+$$

$$V_3^- = S'_{22} V_2^- + \frac{1}{2} V_3^+$$

$$S_{11} = \frac{2j+4}{8-j} \frac{8+j}{8+j} = \frac{16j+32-2+4j}{65} = \frac{20j+30}{65} = \frac{4j+6}{13}$$

$$S_{22} = \frac{2j-4}{8-j} \frac{8+j}{8+j} = \frac{16j-32+2+4j}{65} = \frac{20j-30}{65} = \frac{4j-6}{13}$$

$S_{12} = S_{21}$  for a lossless junction

$$\frac{-34+12j}{65}$$

$$|S_{11}| = \frac{16+36}{169} = \frac{52}{169}$$

$$|S_{22}| = \frac{16+36}{169} = \frac{52}{169}$$

$$\angle S_{11} = \text{Arctan}\left(\frac{4}{6}\right) = \text{Arctan}\left(\frac{2}{3}\right)$$

$$\angle S_{22} = \text{Arctan}\left(-\frac{2}{3}\right) = -\text{Arctan}\left(\frac{2}{3}\right)$$


$$\text{thus } \angle S_{12} = \frac{\angle S_{11} + \angle S_{22}}{2} + \frac{\pi}{2} + n\pi = \frac{\pi}{2} + n\pi$$

$$e^{j\frac{\pi}{2}} e^{\mp jn\pi} = j e^{\mp jn\pi} = \pm j$$

$$|S_{12}|^2 = 1 - |S_{11}|^2 = 1 - \frac{52}{169} = \frac{117}{169}$$


$$S_{12} = S_{21} = \pm j \frac{117}{169}$$

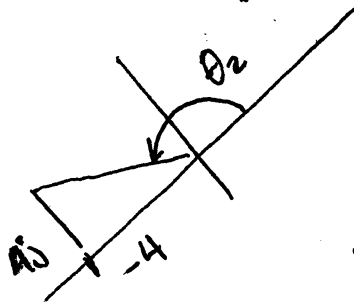$\angle S_{22}$  is  $\pi$ -arctan  $\frac{2}{3}$  for your value of  $S_{22}$



Procedure OK

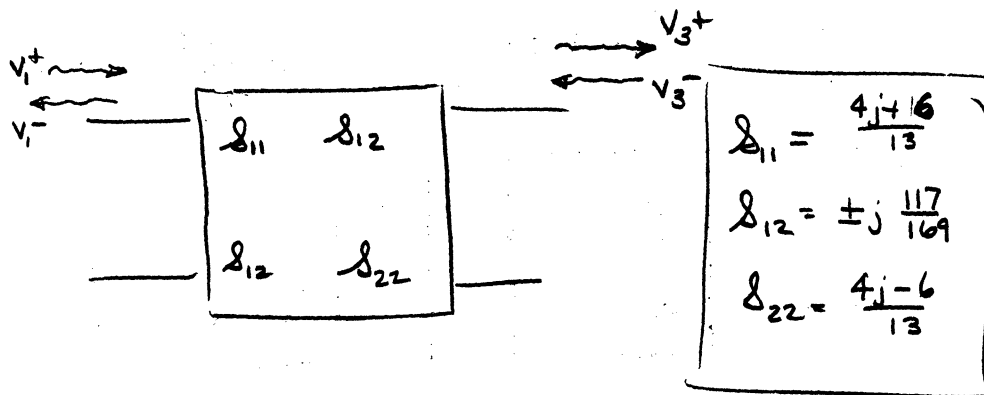\*sign error above makes results for  $S_{12}$  wrong



assume a matched load at  $t_3$  then  $V_3^+ \equiv 0$  if  $V_1^- = S_{11} V_1^+ + S_{12} V_3^+ = S_{11} V_1^+ + j V_3^+ \equiv 0$   
 where  $S_{11}$  &  $S_{12}$  are elements of the scattering matrix for the overall network

then  $S_{11} = \frac{V_1^-}{V_1^+}$

$V_1^- = \frac{1}{4} V_1^+ + S_{12} V_3^+$

$\frac{1}{S_{12}} (V_1^- - \frac{1}{4} V_1^+) = V_3^+ \therefore S_{12} V_1^+ = -(\frac{1}{4} V_3^+ - V_3^-) = -(\frac{1}{4} V_3^+ - 2V_3^+) = -\frac{j-8}{4} V_3^+$

$\therefore V_3^+ = -\frac{4}{j-8} V_3^+$

$\frac{1}{S_{12}} (V_1^- - \frac{1}{4} V_1^+) = -\frac{4}{j-8} S_{12} V_1^+$

$S_{11} - \frac{1}{4} = -\frac{4 S_{12}^2}{j-8}$

$S_{11} = \frac{j}{4} - \frac{4 S_{12}^2}{j-8}$

$S_{12}^2 = |S_{12}|^2 e^{j2\phi}$

where  $\phi = \frac{\theta_1 + \theta_2}{2} + \frac{\pi}{2} \pm n\pi$

$S_{11} = |S_{11}| e^{j\theta_1} \therefore S_{11} = \frac{1}{4} e^{j\frac{\pi}{2}}$   
 $S_{22} = |S_{22}| e^{j\theta_2} \therefore S_{22} = \frac{1}{4} e^{j\frac{\pi}{2}}$

$= \frac{\frac{\pi}{2} + \frac{\pi}{2}}{2} + \frac{\pi}{2} \pm n\pi = \pi \pm n\pi = (1 \pm n)\pi$

$e^{j2(1 \pm n)\pi} = 1$

$|S_{12}|^2 = 1 - |S_{11}|^2 = 1 - \frac{1}{16} = \frac{15}{16}$

$S_{11} = \frac{j}{4} - \frac{4(\frac{15}{16})}{j-8} = \frac{-1-8j-15}{4(j-8)} = -\frac{8j+16}{4(j-8)} = \frac{2j+4}{8-j}$  ✓

assume a matched load at  $t_1$  then  $V_1^+ \equiv 0$   $V_3^- = S_{12} V_1^+ + S_{22} V_3^+ \therefore S_{22} = \frac{V_3^-}{V_3^+}$

$V_2^+ = \frac{1}{2} V_2^- + S_{12}' V_3^+ \therefore (V_2^+ - \frac{1}{2} V_2^-) = S_{12}' V_3^+$

$V_3^- = S_{12}' V_2^- - \frac{1}{2} V_3^+ \therefore S_{12}' V_2^- = V_3^- + \frac{1}{2} V_3^+$

as  $V_1^+ = 0$   $V_1^- = S_{11}' V_2^+ \text{ \& } V_2^- = \frac{1}{4} V_2^+$

$V_2^+ - \frac{1}{2}(\frac{1}{4})V_2^+ = S_{12}' V_3^+ \quad S_{12}' \frac{1}{4} V_2^+ = V_3^- + \frac{1}{2} V_3^+$

$V_2^+ (1 - \frac{1}{8}) = S_{12}' V_3^+ \quad V_2^+ (\frac{1}{4} S_{12}') = V_3^- + \frac{1}{2} V_3^+$

$\therefore \frac{S_{12}' V_3^+}{\frac{8-j}{8}} \cdot \frac{1}{4} S_{12}' = V_3^- + \frac{1}{2} V_3^+ \therefore \left[ \frac{1}{4} S_{12}'^2 V_3^+ = (\frac{8-j}{8}) V_3^- + (\frac{8-j}{16}) V_3^+ \right] \cdot 16$

$4j S_{12}'^2 = 2(8-j) S_{22} + (8-j) \therefore S_{22} = \frac{4j S_{12}'^2 - (8-j)}{2(8-j)} = \frac{4j S_{12}'^2 + j - 8}{2(8-j)}$


again  $S_{11}' = \frac{1}{2} \therefore$  identify  $\theta_1' = 0$   $\theta_2' = \pi$   $\phi' = \pi \mp n\pi$   
 $S_{22}' = \frac{1}{2} e^{j\pi}$   
 $\Rightarrow S_{12}'^2 = |S_{12}'|^2 = \frac{1}{4}$

as  $S_{12}'^2 = |S_{12}'|^2 = 1 - |S_{11}'|^2 = 1 - \frac{1}{4} = \frac{3}{4}$

$S_{22} = \frac{4j(\frac{3}{4}) + j - 8}{2(8-j)} = \frac{4j - 8}{2(8-j)} = \frac{2j - 4}{8-j}$  ✓

note that  $|S_{11}| = |S_{22}|$  as expected for a lossless junction

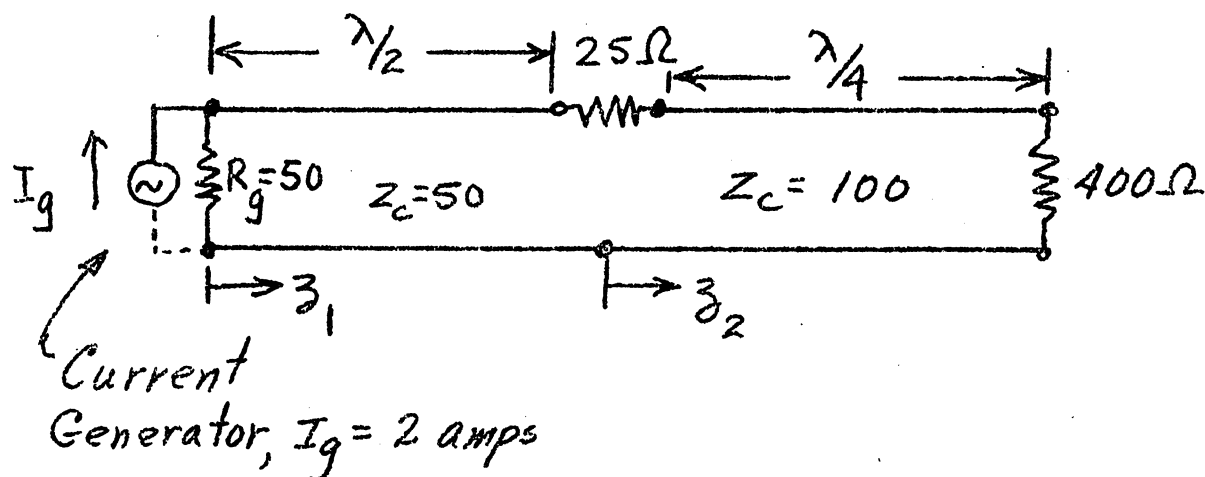2. For the illustrated transmission line circuit find the total voltage and current at all points on each line section. Find the power delivered to the  $25\Omega$  and  $400\Omega$  resistors.




$$Z_{in} = Z_c \frac{Z_L + jZ_c \tan \beta l}{Z_c + jZ_L \tan \beta l}$$

$$Z_{in}(z_2 = 0) = Z_c \frac{jZ_c}{jZ_L} = \frac{Z_c^2}{Z_L} = \frac{(100)^2}{400} = 25\Omega$$

$$Z_{in}(z_1 = \frac{\lambda}{2}) = 25\Omega + Z_{in}(z_2 = 0) = 25 + 25 = 50\Omega$$

$$Z_{in}(z_1 = 0) = 50\Omega$$

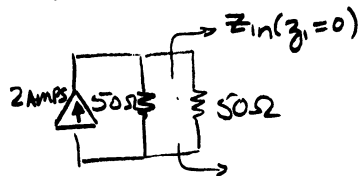

$$V = IZ = (2 \text{ amps})(25\Omega) = 50 \text{ volts.}$$

on the first section

$$V = V^+ e^{-j\beta z} + V^- e^{+j\beta z}$$

$$I = \frac{V^+}{Z_c} e^{-j\beta z} - \frac{V^-}{Z_c} e^{+j\beta z}$$

$$\text{at } z_1 = \frac{\lambda}{2} \quad \Gamma = \frac{Z_L - Z_c}{Z_L + Z_c} = 0 \quad \text{but } \Gamma = \frac{V_1^- e^{+j\beta \frac{\lambda}{2}}}{V_1^+ e^{-j\beta \frac{\lambda}{2}}} = \frac{V_1^-}{V_1^+}$$

$$\Rightarrow V_1^- = 0$$

$$\text{at } z_1 = 0 \quad V = V_1^- + V_1^+ = 50 \quad \therefore V_1^+ = 50 \quad \checkmark$$

and  $V = 50 e^{-j\beta z_1}$   $I = e^{-j\beta z_1}$   
 across the 25Ω resistor  $\text{at } z_1 = \frac{\lambda}{2}, V = 50 e^{-j\beta \frac{\lambda}{2}} = -50$   
 $I = -1$

$V_{\text{drop}} = IR = (1)(25) = 25 \text{ volts}$

$P_R = \frac{1}{2} |I|^2 R = \frac{1}{2} |1|^2 25 = 12.5 \text{ watts}$  ✓

at  $z_2 = \frac{\lambda}{4}$   $P = \frac{400 - 100}{400 + 100} = \frac{3}{5}$  &  $P = \frac{V^-}{V^+} e^{2j\beta z_2} = \frac{V^-}{V^+} e^{j\beta \frac{\lambda}{2}} = -\frac{V^-}{V^+}$   
 $\therefore \frac{3}{5} = -\frac{V^-}{V^+} \Rightarrow V^+ = -\frac{3}{5} V^-$

at  $z_2 = 0$   $25 = V^- + V^+$   
 $25 = -\frac{3}{5} V^+ + V^+$   
 $V^+ = \frac{125}{2} \text{ VOLTS}$

*sign error*

$V^- = -\frac{3}{5} \left(\frac{125}{2}\right) = -\frac{75}{2} \text{ VOLTS}$

$V = \frac{125}{2} e^{-j\beta z_2} - \frac{75}{2} e^{+j\beta z_2}$

$I = \frac{5}{8} e^{-j\beta z_2} + \frac{3}{8} e^{+j\beta z_2}$   $\left[ \frac{125}{2} \frac{1}{100} = \frac{5}{8}, \text{ etc} \right]$

at  $z_2 = \frac{\lambda}{4}$   $I = -\frac{5}{8} - \frac{3}{8} = -1 \text{ amp}$   
 $V = -\frac{25}{2} \text{ volt}$

$P_L = \frac{1}{2} I V^* = \frac{1}{2} (-1) \left(-\frac{25}{2}\right) = 12.5 \text{ watts}$

To summarize: at the generator  $I = 2 \text{ amps}$   $V = 50 \text{ volts}$   
 $0 \leq z_1 \leq \frac{\lambda}{2}$   $I = e^{-j\beta z_1}$   $V = 50 e^{-j\beta z_1}$

voltage drop across 25Ω resistor is 25 volts  
 power delivered to it is 12.5 watts

$0 \leq z_2 \leq \frac{\lambda}{4}$   $-I = \frac{5}{8} e^{-j\beta z_2} + \frac{3}{8} e^{+j\beta z_2}$


$-V = \frac{125}{2} e^{-j\beta z_2} - \frac{75}{2} e^{+j\beta z_2}$

at the load

$I = -1 \text{ amp}$   $V = -\frac{25}{2} \text{ volt}$

Power delivered to load (400Ω resistor) is 12.5 watts

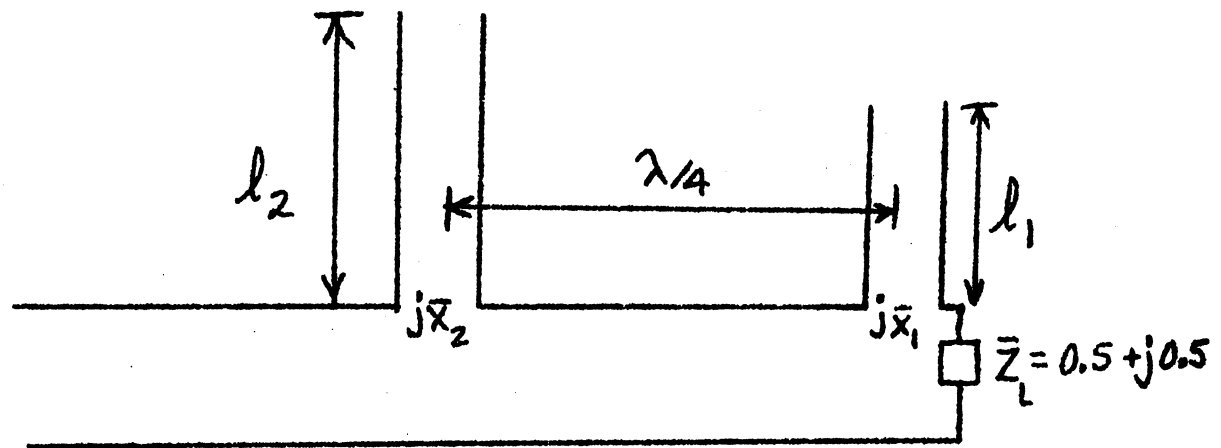3. A normalized load  $\bar{Z}_L = 0.5 + j0.5$  is to be matched by means of two open-circuited series stubs spaced  $\lambda/4$  apart. Use a Smith chart to find the required stub reactances and their lengths  $l_1$  and  $l_2$ .




$$\bar{x}_1 = ? \quad \bar{x}_2 = ? \quad l_1 = ? \quad l_2 = ?$$

$$2\beta d = 2 \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \pi$$

as  $\bar{Z}_L$  lies on the displaced  $\bar{Z} = 1$  circle  $\bar{x}_1 = 0$  ✓

from the chart  $l_1 = 0.25\lambda$


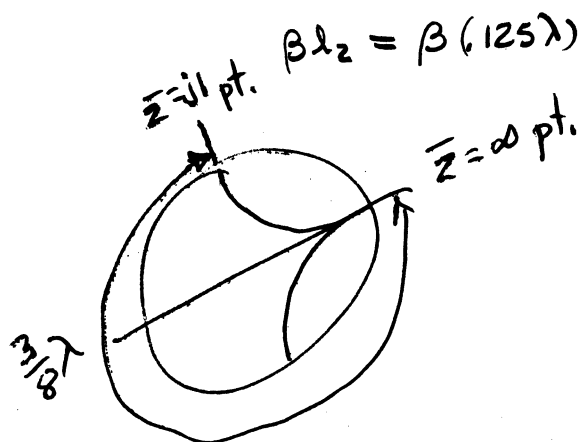
$\bar{x}_2 = 1$  so that  $\bar{Z} + j\bar{x}_2 = (1-j) + j = 1$  indicating a match



$$\beta l_2 = \beta (0.125\lambda) \Rightarrow l_2 = 0.125\lambda$$

$$\frac{3}{8}\lambda$$


### IMPEDANCE OR ADMITTANCE COORDINATES

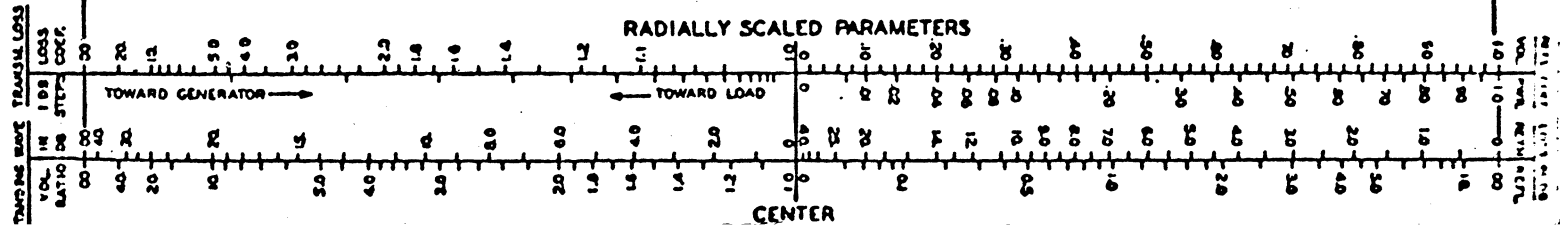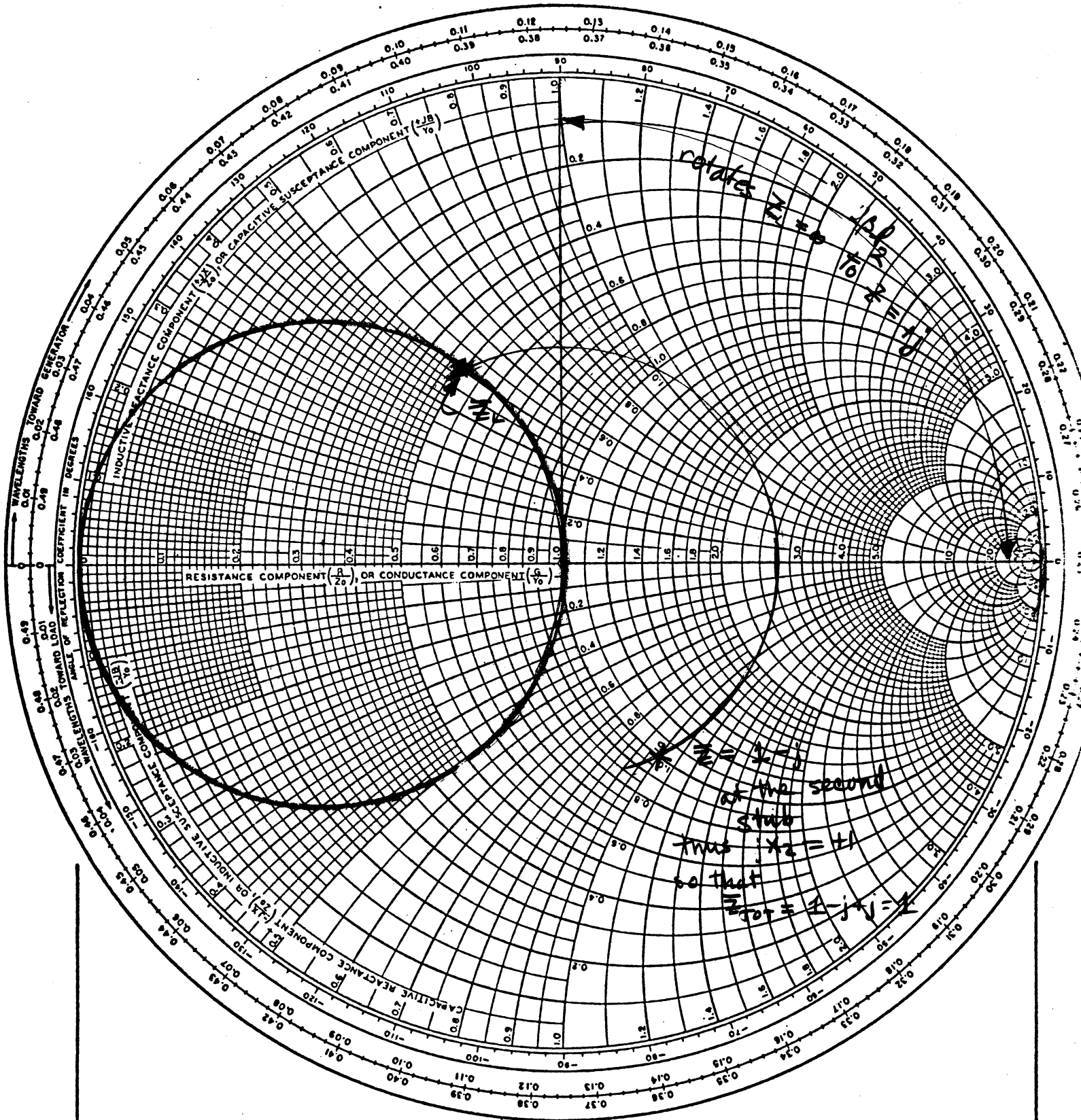

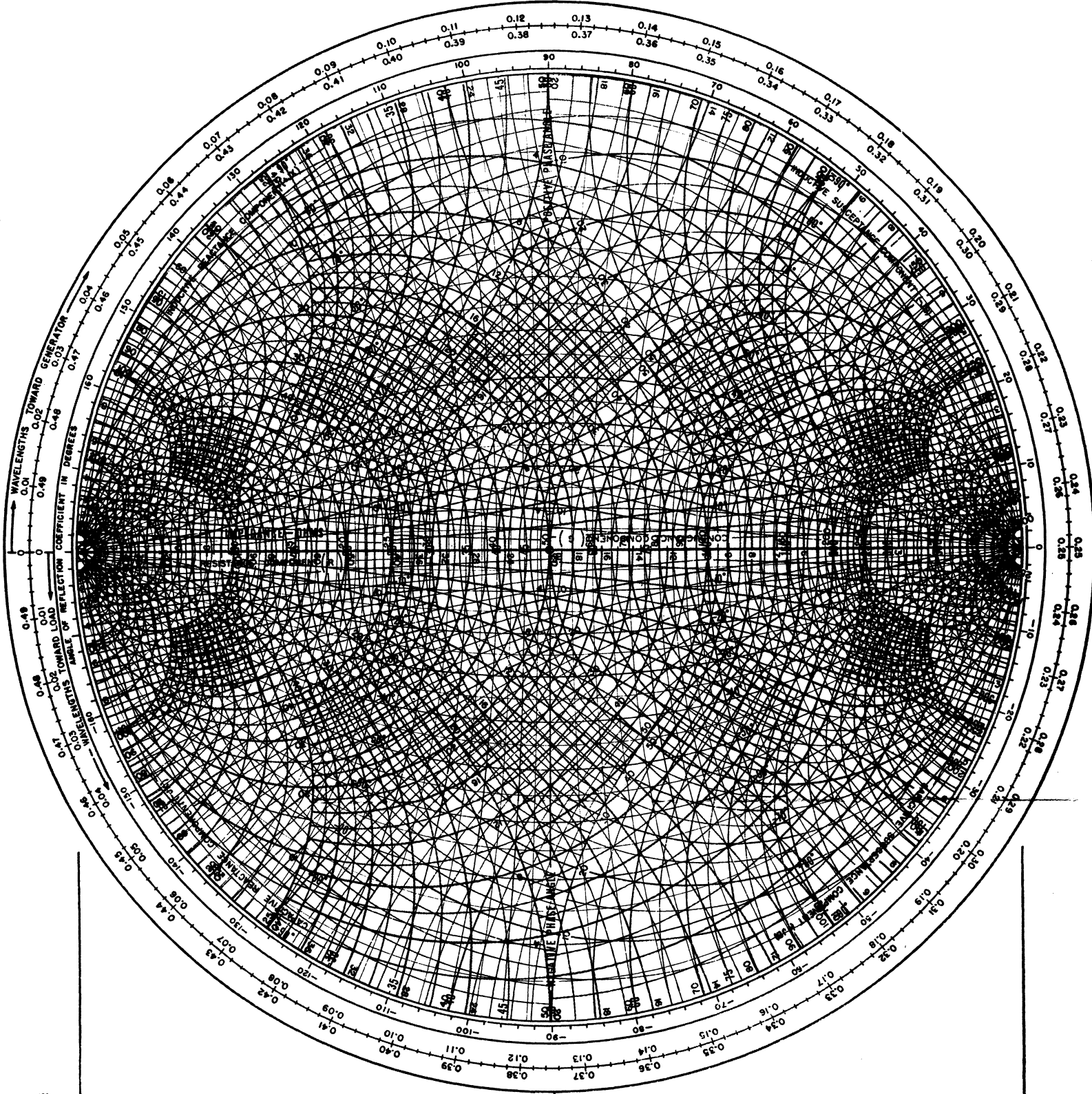
# IMMITTANCE CHART

IMPEDANCE COORDINATES — 50 OHM CHARACTERISTIC IMPEDANCE

ADMITTANCE COORDINATES — 20 MILLIMHO CHARACTERISTIC ADMITTANCE



### RADIALLY SCALED PARAMETERS

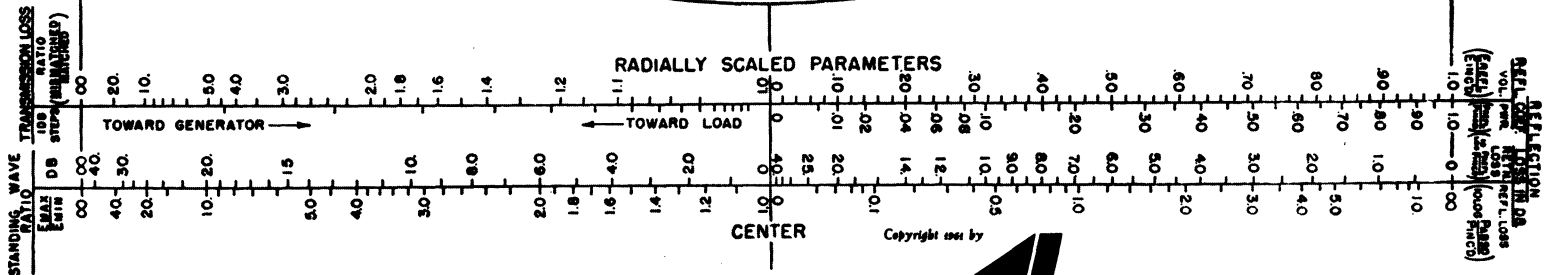




# Microwave Engineering Exam, April 1972


Name FRANCIS L. MERAT

1. 9
2. 8
3. 10

27/30

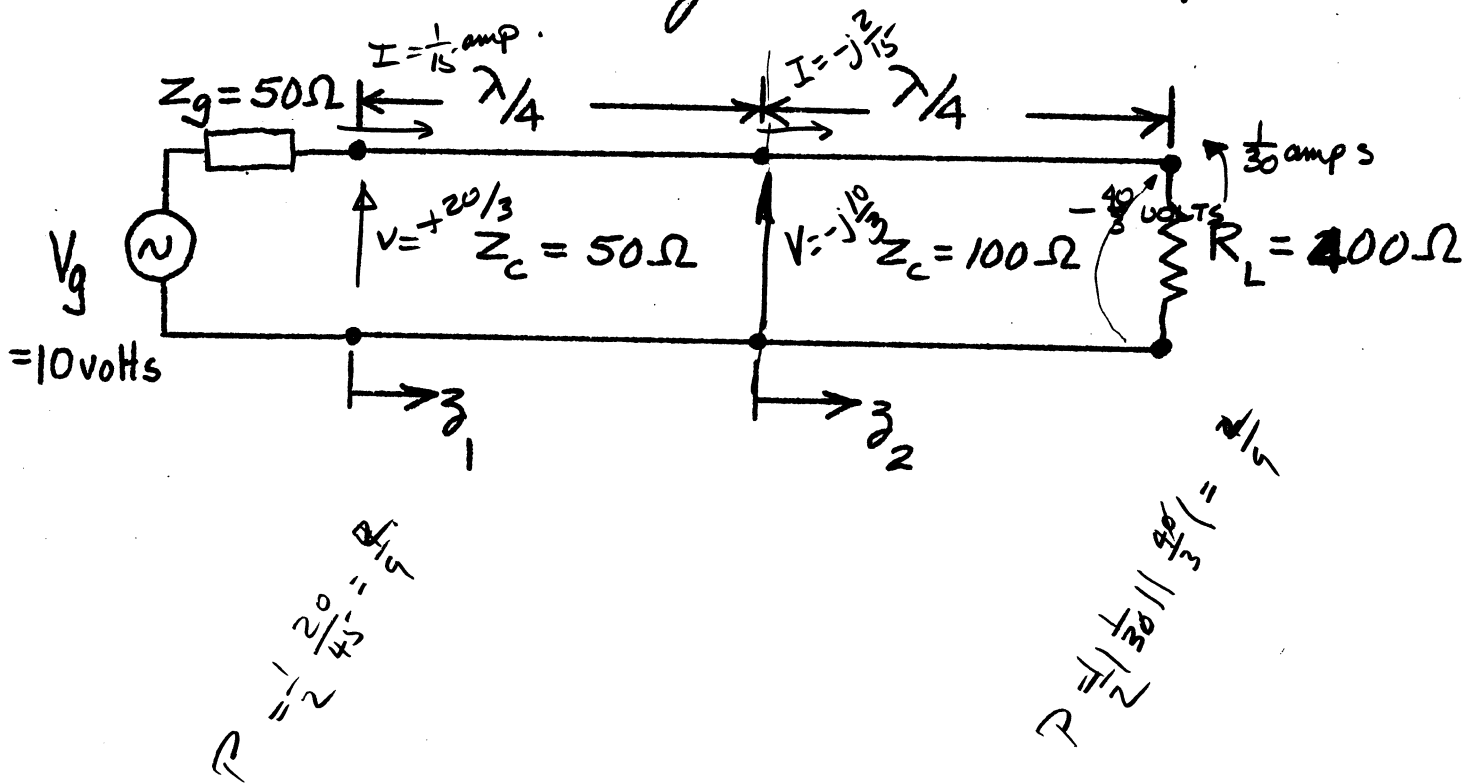1. For the illustrated transmission line circuit find the total voltage and current at all points on both line sections. Find the power delivered to the load.  $z_1$  and  $z_2$  measure distances along the two sections.




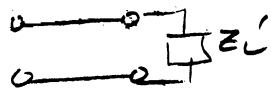


$$\begin{aligned}
 Z_L'' &= Z_g \frac{Z_L' + jZ_c \tan \beta l}{Z_c + jZ_L' \tan \beta l} \\
 &= 50 \frac{25 + j50 \tan \frac{\pi}{2}}{50 + j25 \tan \frac{\pi}{2}} \\
 &= 50 \cdot 2 = 100
 \end{aligned}$$


$$I_L'' = \frac{V_g}{Z_L'' + Z_g} = \frac{10}{100 + 50} = \frac{10}{150} = \boxed{\frac{1}{15} \text{ amp}}$$
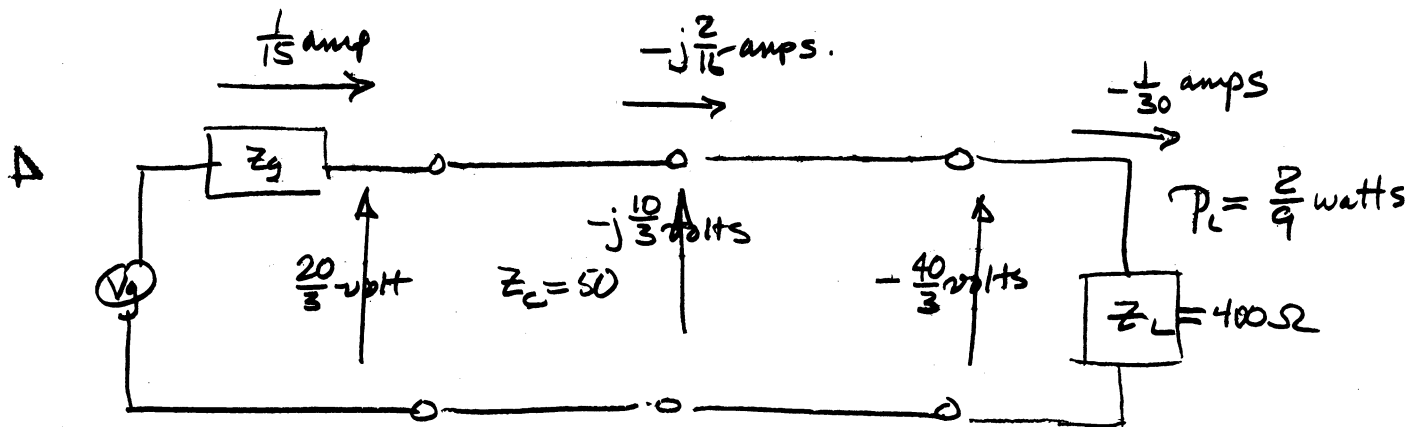
$$V_L'' = V_g \frac{Z_L''}{Z_L'' + Z_g} = 10 \frac{100}{100 + 50} = 10 \frac{10}{15} = \boxed{\frac{20}{3} \text{ volts}}$$



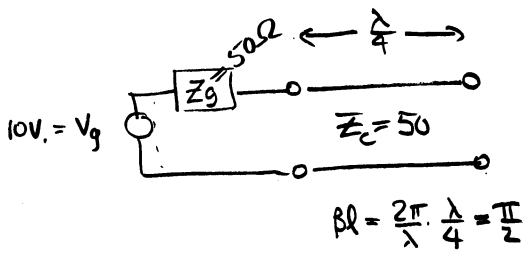

THEVENIZE THIS SECTION TO

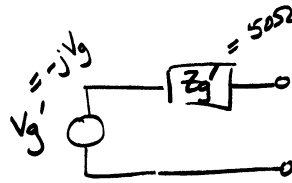

Hard way to do this problem

$$Z_g' = Z_c \frac{Z_g + jZ_c \tan \beta L}{Z_c + jZ_g \tan \beta L}$$

$$= 50 \frac{50 + j50 \tan \frac{\pi}{2}}{50 + j50 \tan \frac{\pi}{2}}$$

$$= 50$$

from text p. 167 eq. 4.49

$$V_{oc} = \frac{2V_g e^{-j\beta L}}{(1 + Y_c Z_g) + (1 - Y_c Z_g) e^{-2j\beta L}}$$

$$e^{-j\beta L} = e^{-j\frac{\pi}{2}} = \cos \frac{\pi}{2} - j \sin \frac{\pi}{2} = -j$$


$$e^{-2j\beta L} = e^{-j\pi} = \cos \pi - j \sin \pi = -1$$

$$1 + Y_c Z_g = 1 + \frac{1}{50} \cdot 50 = 2$$

$$1 - Y_c Z_g = 0$$

$$\Rightarrow V_{oc} = \frac{2V_g (-j)}{2} = -jV_g \checkmark$$

thevenize again:

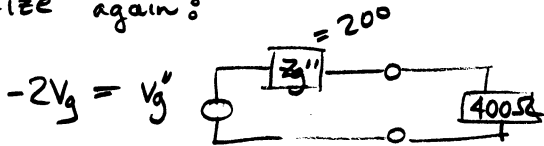

$$Z_g'' = Z_c \frac{Z_g' + jZ_c \tan \beta L}{Z_c + jZ_g' \tan \beta L} = 100 \frac{50 + j100 \tan \frac{\pi}{2}}{100 + j50 \tan \frac{\pi}{2}}$$

$$= 100 \frac{j100}{j50} = 200 \checkmark$$

$$V_{oc} = \frac{2V_g' e^{-j\beta L}}{(1 + Y_c Z_g) + (1 - Y_c Z_g) e^{-2j\beta L}} = \frac{2(-j)V_g'}{\frac{3}{2} + \frac{1}{2}(-1)} = \frac{2(-j)V_g'}{\frac{3}{2} - \frac{1}{2}} = \frac{2(-j)V_g'}{1}$$

$$= -2jV_g'$$

$$= -2j(-jV_g)$$

$$= -2V_g \checkmark$$

9

$$1 + Y_c Z_g = 1 + \frac{1}{100} \cdot 50 = 1 + \frac{1}{2} = \frac{3}{2}$$

$$1 - Y_c Z_g = 1 - \frac{1}{100} \cdot 50 = 1 - \frac{1}{2} = \frac{1}{2}$$

at load

$$I_L = \frac{V_g''}{Z_g'' + 400} = \frac{-2V_g}{200 + 400} = -\frac{2}{600} V_g = -\frac{1}{300} (10) = \boxed{-\frac{1}{30} \text{ amps}}$$

$$V_L = V_g'' \frac{400}{Z_g'' + 400} = -2V_g \frac{400}{600} = -\frac{4}{3} (10) = \boxed{-\frac{40}{3} \text{ VOLTS}}$$

$$P = \frac{1}{2} |I_L|^2 Z_L = \frac{1}{2} \left| -\frac{1}{30} \right|^2 400 = \frac{200}{900} = \boxed{\frac{2}{9} \text{ WATTS}} \checkmark$$


at junction between waveguide sections

$$Z_L' = Z_c \frac{Z_L + jZ_c \tan \beta L}{Z_c + jZ_L \tan \beta L} = 100 \frac{400 + j100 \tan \frac{\pi}{2}}{100 + j400 \tan \frac{\pi}{2}} = 25$$

$$I_L' = \frac{V_g'}{Z_g' + Z_L'} = \frac{-jV_g}{50 + 25} = -\frac{j}{75} 10 = \boxed{-\frac{j2}{15}}$$

$$V_L' = V_g' \frac{Z_L'}{Z_g' + Z_L'} = -j10 \frac{25}{75} = \boxed{-\frac{j10}{3}}$$

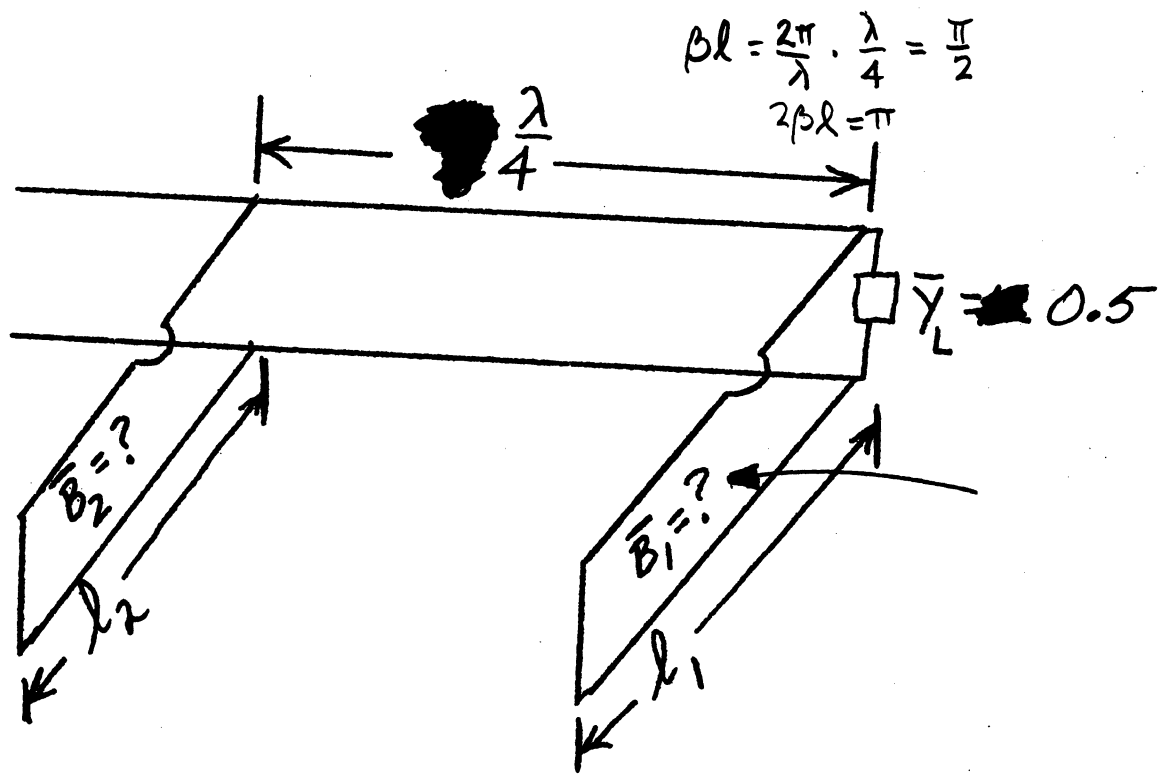2. For the illustrated double stub tuner find the lengths and susceptances that each stub must have to match the load admittance  $\bar{Y}_L = \mathbf{0.5}$  to the main line. Show all constructions on the attached Smith chart.





NAME  
SMITH CHART FORM 756-N

TITLE  
GENERAL RADIO COMPANY, WEST CONCORD, MASSACHUSETTS

DWG. NO.  
DATE

IMPEDANCE OR ADMITTANCE COORDINATES

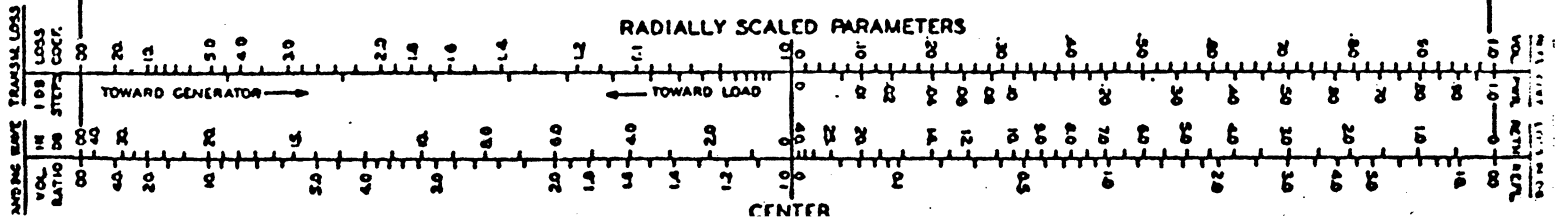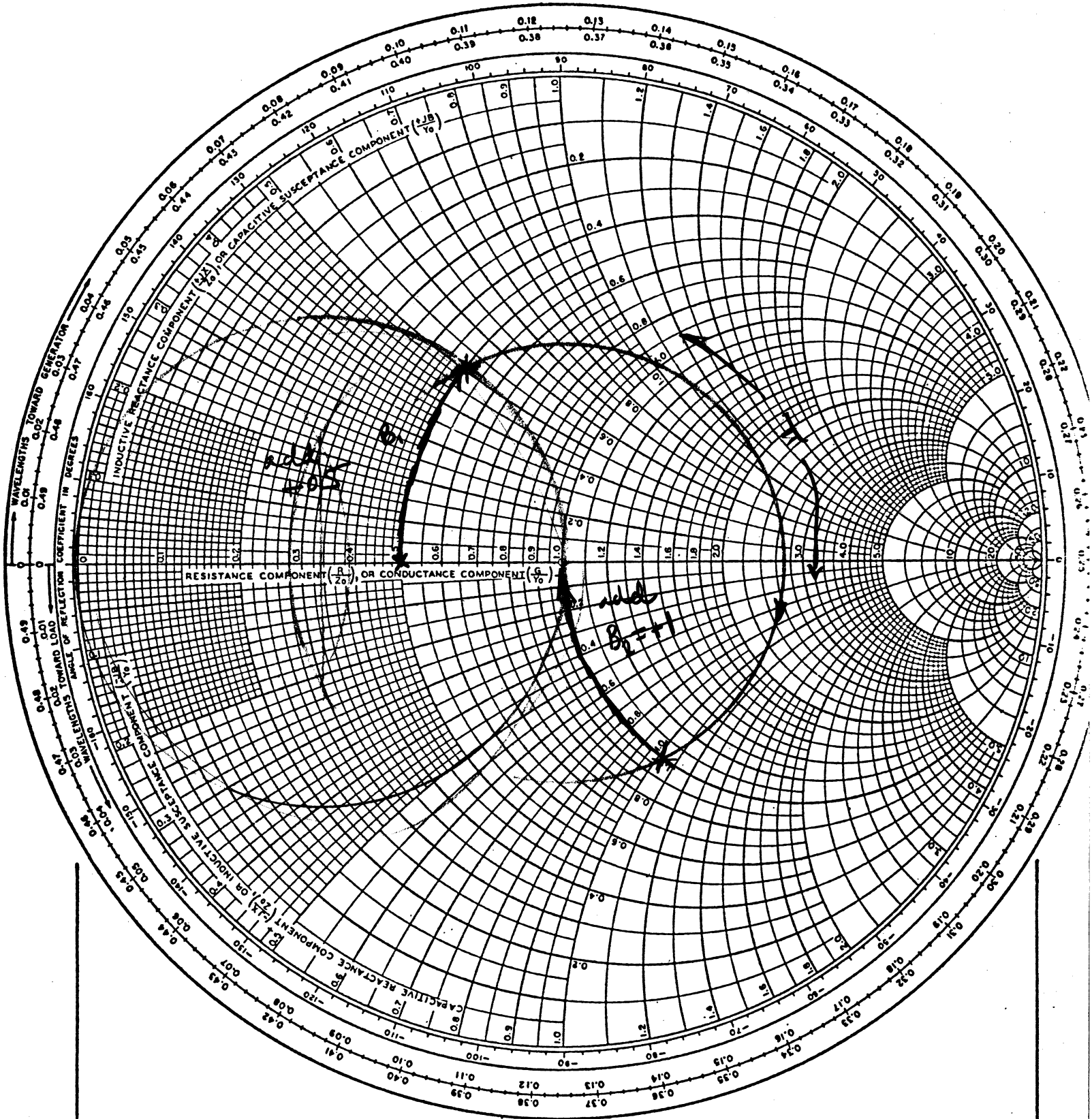

from chart

$$\boxed{B_1 = +0.5}$$

$$\text{want } \bar{\Gamma}_L' = \bar{\Gamma}_L + j\bar{B}_1 = 0.5 + j0.5$$

want  $B_2$  to be  $-1$

$$\boxed{B_2 = +1.0}$$

$$Y(x) = -j \cot \beta l$$

$$j\frac{1}{2} = -j \cot \beta l_1$$

$$\boxed{-\frac{1}{2} = \cot \beta l_1} \text{ look up in table}$$

Use chart  
to find  $l_1, l_2$


$$j1 = -j \cot \beta l_2$$

$$-1 = \cot \beta l_2$$

$$\boxed{\beta l_2 = \frac{3\pi}{8}}$$

8

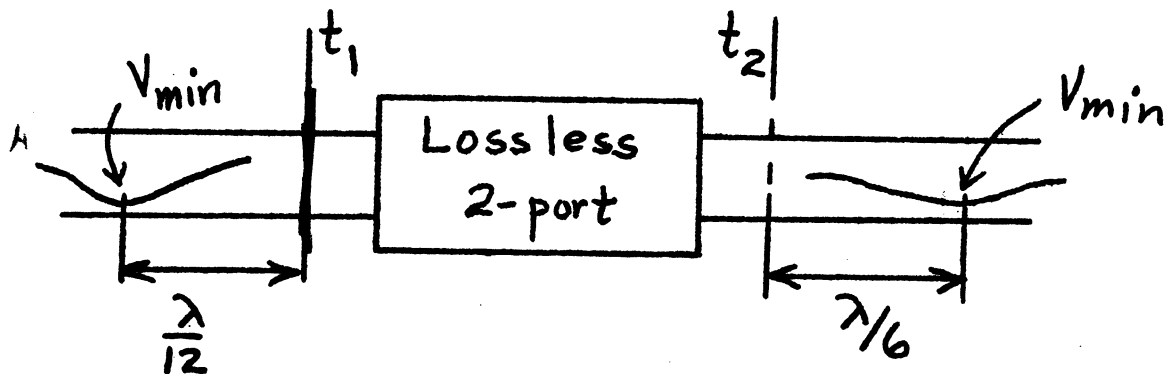3. Consider the illustrated lossless 2-port junction. With the output terminated in a matched load the VSWR on the input line was 3 and a voltage minimum occurred at  $\lambda/12$  from reference plane  $t_1$ . With the input side terminated in a matched load it was found that a voltage minimum occurred at  $\lambda/6$  from the reference plane  $t_2$  on the output line. In terms of this data find the scattering matrix parameters  $S_{11}$ ,  $S_{12}$  and  $S_{22}$  for the junction between reference planes  $t_1$  and  $t_2$ .



$$S_{12} = |S_{12}| e^{j\theta}$$

$$|S_{12}| = \sqrt{1 - |S_{11}|^2} = \sqrt{1 - \left(\frac{1}{2}\right)\left(\frac{1}{2}\right)} = \frac{\sqrt{3}}{2} \checkmark$$

$$S_{11} S_{12}^* + S_{22} S_{12}^* = 0$$

$$-\frac{1}{2} e^{j\frac{\pi}{3}} \frac{\sqrt{3}}{2} e^{-j\theta} + \frac{\sqrt{3}}{2} e^{+j\theta} \left(-\frac{1}{2}\right) e^{-j\frac{2\pi}{3}} = 0$$

$$e^{j\left(\frac{\pi}{3} - \theta\right)} + e^{j\left(\theta - \frac{2\pi}{3}\right)} = 0$$

$$e^{j\left(\frac{\pi}{3} - \theta\right)} = -e^{j\left(\theta - \frac{2\pi}{3}\right)}$$

$$= e^{-j\pi} e^{j\left(\theta - \frac{2\pi}{3}\right)}$$

$$\tan e^{-j\pi} = -1$$

$$e^{j\left(\frac{\pi}{3} - \theta\right)} = e^{j\left(\theta + \frac{5\pi}{3}\right)}$$

$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$\frac{\pi}{3} = \frac{180}{\pi} = 60^\circ$$

$$e^{j\frac{\pi}{3}} = \cos\frac{\pi}{3} + j\sin\frac{\pi}{3}$$

$$= \frac{1}{2} + j\frac{\sqrt{3}}{2}$$

$$\frac{2\pi}{3} = \frac{180}{\pi} = 120^\circ = -60^\circ$$

$$\frac{\pi}{3} - \theta = \theta - \frac{5\pi}{3}$$

$$\frac{\pi}{3} + \frac{5\pi}{3} = 2\theta$$

$$2\pi = 2\theta$$

$$\pi = \theta$$

$$\rightarrow S_{12} = \frac{\sqrt{3}}{2} e^{j\pi} = -\frac{\sqrt{3}}{2}$$

$$S_{11} = -\frac{1}{4} - j\frac{\sqrt{3}}{4}$$

$$S_{12} = -\frac{\sqrt{3}}{2} \checkmark$$

$$S_{22} = -\frac{1}{4} + j\frac{\sqrt{3}}{4}$$

$$S_{12} = |S_{12}| e^{j\theta}$$

$$S_{ii} = |S_{ii}| e^{j\theta_i}$$

$$\phi = \frac{\theta_1 + \theta_2 + \frac{\pi}{2} \pm n\pi}{2}$$

$$= \frac{4\frac{\pi}{3} + 5\frac{\pi}{3} + \frac{\pi}{2} \pm n\pi}{2}$$

$$= \frac{3\pi + \frac{\pi}{2} \pm n\pi}{2}$$

or zero phase is OK



output terminated in matched load

$$V_1^- = S_{11} V_1^+ + S_{12} V_2^+$$



$$S_{11} = \frac{V_1^-}{V_1^+} = \Gamma \text{ at plane } t_1$$

$$V_{SWR} = 3 \quad \frac{\lambda}{12} \text{ from } t_1$$

$$\text{but } Y_{in} = \frac{1-\Gamma}{1+\Gamma} = \frac{1+\rho}{1-\rho} = 3 \quad \text{at voltage minimum}$$

$$1-\Gamma = 3(1+\Gamma)$$


$$1-\Gamma = 3+3\Gamma$$

$$-2 = 4\Gamma$$

$$\Gamma = -\frac{1}{2} \text{ at } \frac{\lambda}{12} \text{ from } t_1$$

$$2\beta l = 60^\circ$$
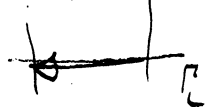
$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{12} = \frac{\pi}{6} = 30^\circ$$




transform

$$\Gamma(z) = \Gamma_L e^{-2j\beta z}$$

$$-\frac{1}{2} = \Gamma_L e^{-2j\beta l} = \Gamma_L e^{-j\frac{\pi}{3}}$$
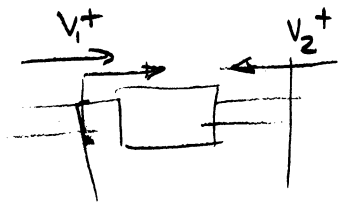
$$-\frac{1}{2} e^{+j\frac{\pi}{3}} = \Gamma_L = S_{11}$$



$$S_{11} = -\frac{1}{2} e^{+j\frac{\pi}{3}}$$

$$= \frac{1}{2} e^{j\frac{4\pi}{3}}$$

$$V_2^- = S_{21} V_1^+ + S_{22} V_2^+$$

If input is matched  $V_1^+ \rightarrow 0$

lossless junction

$$|S_{11}| e^{j\theta} = \frac{V_2^-}{V_2^+} = S_{22}$$

$$-\frac{1}{2} e^{j\theta} = S_{22} = \Gamma_L$$

$$2\beta l = 2 \cdot \frac{2\pi}{\lambda} \cdot \frac{\lambda}{6} = \frac{2\pi}{3}$$

$$e^{j\theta} = \cos\theta + j\sin\theta$$

at 0

but  $\Gamma(z) = \Gamma_L e^{-2j\beta z}$

$$\Gamma\left(\frac{\lambda}{6}\right) = -\frac{1}{2} e^{j\theta} e^{-j\frac{2\pi}{3}} = -\frac{1}{2} e^{j(\theta - \frac{2\pi}{3})}$$

at a voltage minimum  
 $\Rightarrow$  pick first time  
 i.e. pick  $n=0$

$\Gamma$  is negative and real  
 $\theta - \frac{2\pi}{3} = n\pi$   
 $\theta - \frac{2\pi}{3} = 0$   
 $\theta = \frac{2\pi}{3}$

$$S_{22} = -\frac{1}{2} e^{+j\frac{2\pi}{3}}$$

$$= \frac{1}{2} e^{j\frac{5\pi}{3}}$$

$$e^{j\pi} = \cos\pi + j\sin\pi$$

$$\frac{\pi/2 - \pi/4}{\pi} = 300^\circ = -60^\circ$$

$$\text{let } S_{12} = A e^{jB}$$

~~$$S_{11} S_{12}^* + S_{12} S_{22}^* = 0$$

$$-\frac{1}{2} e^{j\frac{\pi}{3}} A e^{-jB} + A e^{jB} \left(-\frac{1}{2}\right) e^{-j\frac{5\pi}{3}} = 0$$

$$e^{-j(\frac{\pi}{3}-B)} + e^{j(B-\frac{5\pi}{3})} = 0$$~~

$$S_{12} = A + jB$$

$$S_{11} = -\frac{1}{2} e^{j60^\circ} = -\frac{1}{2} \cos 60 - \frac{1}{2} j \sin 60 = -\frac{1}{4} - \frac{1}{4} j \sqrt{3}$$

$$S_{22} = -\frac{1}{2} e^{-j60^\circ} = -\frac{1}{4} + \frac{1}{4} j \sqrt{3}$$

$$S_{11} S_{12}^* + S_{12} S_{22}^* = 0$$

~~$$\left(-\frac{1}{4} - \frac{1}{4} j \sqrt{3}\right) (A - jB) + (A + jB) \left(-\frac{1}{4} + \frac{1}{4} j \sqrt{3}\right) = 0$$~~

$$A - jB + A + jB = 0$$

$$2A = 0$$

$$|S_{21}| = \sqrt{1 - |S_{11}|^2} = \sqrt{1 - \left(-\frac{1}{4} - \frac{1}{4} j \sqrt{3}\right)^2} = \sqrt{1 - \frac{1}{4}} = \sqrt{\frac{3}{4}} = \frac{1}{2} \sqrt{3}$$

$$S_{12} = A + jB$$

$$|S_{12}| = \sqrt{A^2 + B^2} \quad \text{but } A=0$$

$$= \sqrt{B^2} = B$$

$$\Rightarrow B = \frac{1}{2} \sqrt{3}$$

$$S_{11} = -\frac{1}{4} - \frac{1}{4} j \sqrt{3}$$

$$S_{12} = j \frac{1}{2} \sqrt{3}$$

$$S_{22} = -\frac{1}{4} + \frac{1}{4} j \sqrt{3}$$